

VLSI Testing



Lecture 25

18-322 Fall 2003

Announcement



- Homework 9 is due next Thursday (11/20)
- Exam II is on Tuesday (11/18) in class
- Review Session:
 - ☒ When: Next Monday (11/17) afternoon, 4pm – 6pm
 - ☒ Where: B131, HH

Outline



■ Defects and Faults

- ☒ Reasons for IC malfunctioning

■ Fault Modeling

- ☒ Types of faults (Stuck-At, bridge, Stuck Open)

- ☒ Automatic Test Pattern Generation

- ☒ Path Delay Fault

■ Design for Testability

Why Testing?

■ Manufacturing is imperfect

$$\boxed{\wedge} Y = \frac{\text{No. of good chips on wafer}}{\text{Total no. of chips}}$$

$\boxed{\wedge}$ Yield (Y) depends on technology, chip area and layout

$\boxed{\times}$ Y decreases as the area of chip is increased

$\boxed{\times}$ Defect density (D)

- Modern technologies yield a value of 1-5 defects/cm²

$\boxed{\wedge}$ Yield starts out low (~10%) moves up (95%)

■ High quality expectation


$\boxed{\wedge}$ The earlier you detect a fault, the cheaper it is to fix

Reasons for IC Malfunction - Contamination, Defects and Faults




- Contamination / Instabilities - Process induced impurities and random fluctuations of process conditions
- Defects - Permanent deformation in IC layer which may but does not have to result in fault
- Faults - Functional misbehaviors i.e. IC malfunctions


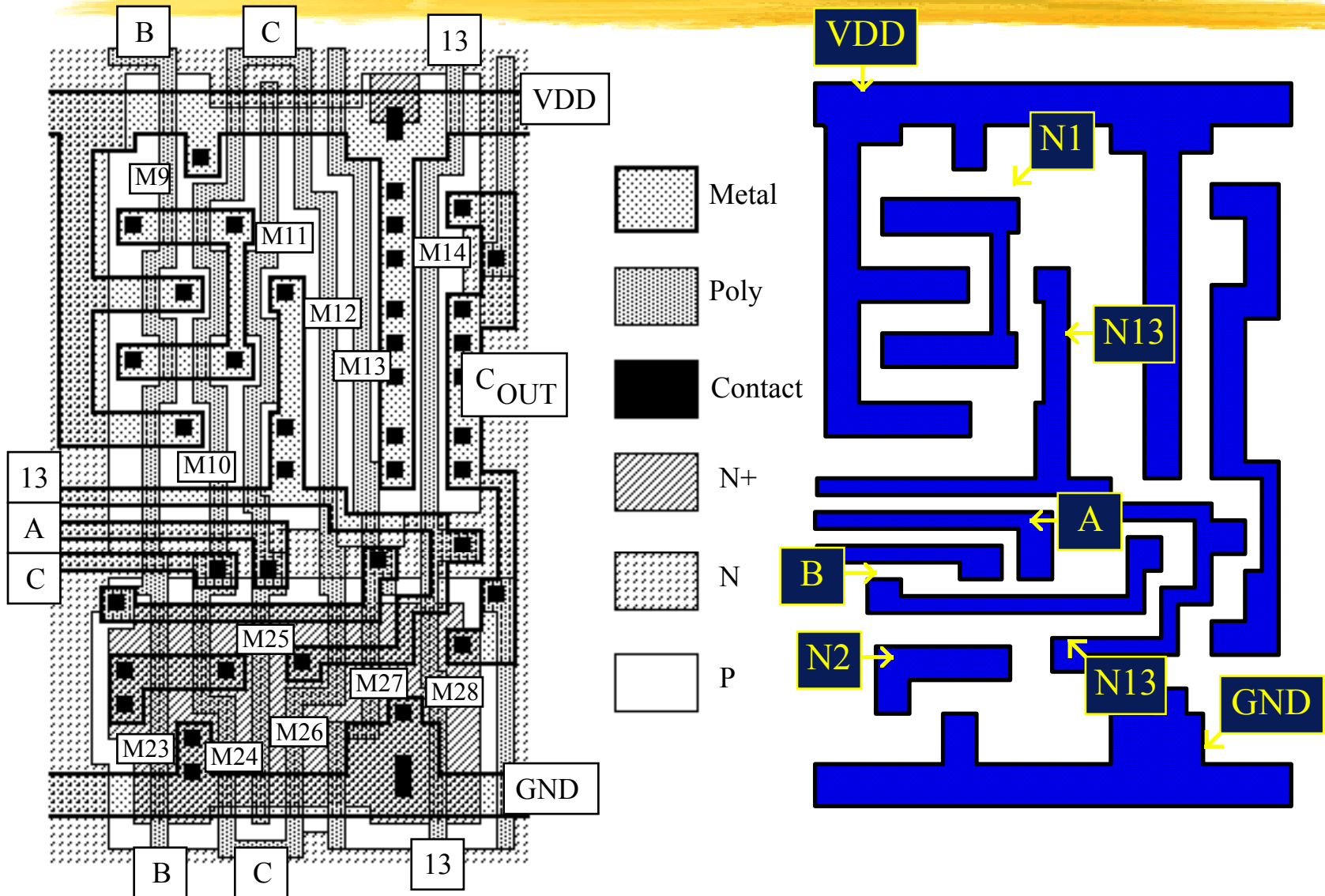
Reasons for IC Malfunction - Defects and Faults



 
Reasons for IC Malfunction - Defects and Faults



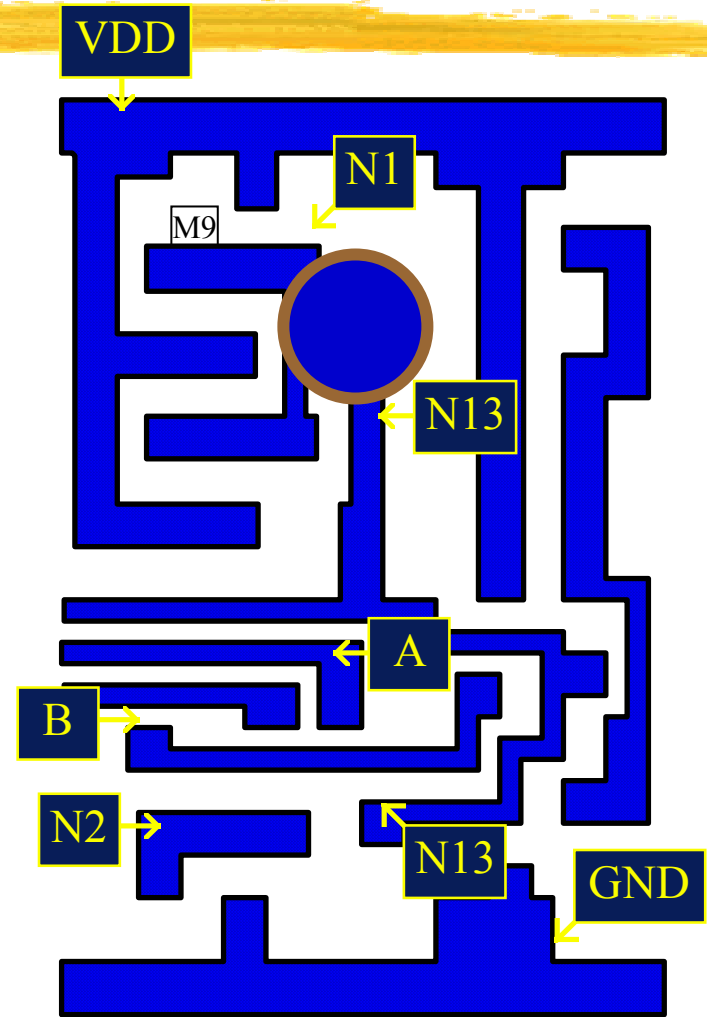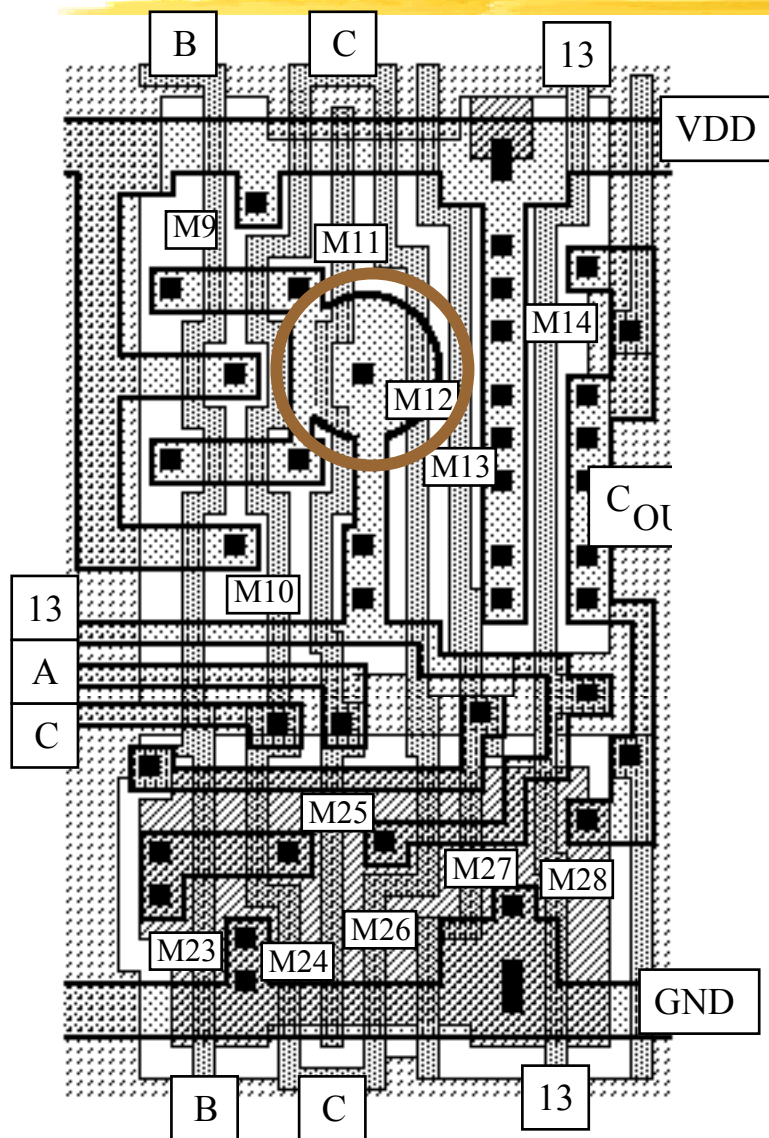Reasons for IC Malfunction - Defects and Faults



 Reasons for IC Malfunction - Defects and Faults



C_{out}

A	B	C	Defect	
			no	yes
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

N1 - N13 short

Outline



✓ Defects and Faults

- ☒ Reasons for IC malfunctioning

■ Fault Modeling


- ☒ Types of faults (Stuck-At, bridge, Stuck Open)

- ☒ Automatic Test Pattern Generation

- ☒ Path Delay Fault

■ Design for Testability

Test Complexity

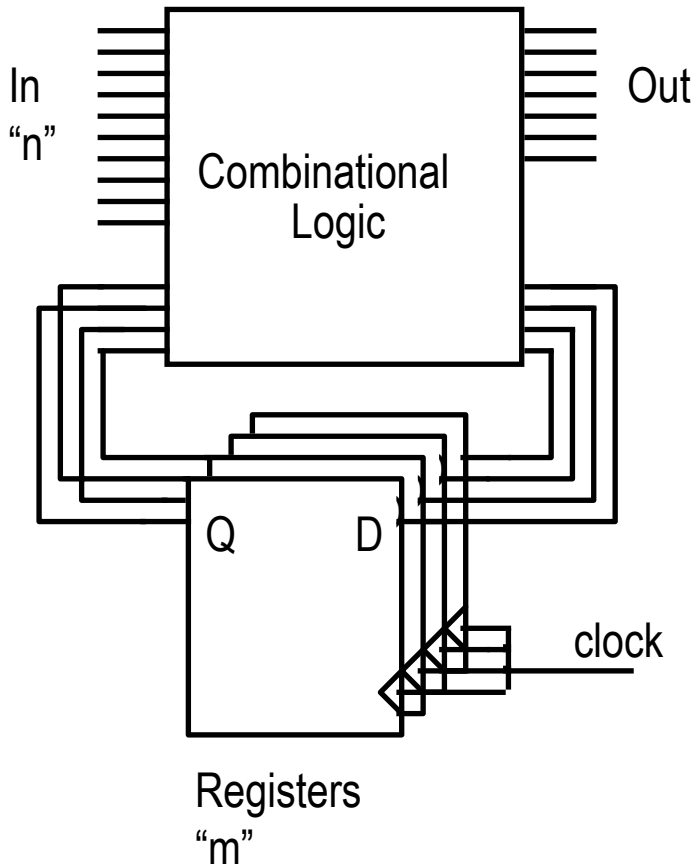

Exhaustive test 2^{n+m}

Circuit with $n = 25$ and $m = 50$

$1\mu\text{sec}/\text{test}$

Exhaustive test time is over 1 billion years!

(Registers make life harder!)

Testing Strategies



- Functional Test: (go/no go)

- ☒ Does the part work?
- ☒ Do this fast & cheap

- Diagnostic Test:

- ☒ What in the chip is broken?

- Parametric Test:


- ☒ What is:
 - ☒ max clock frequency
 - ☒ min supply voltage
 - ☒ max operating temp

Test Implementation

- Runs Test Vectors/Programs on Device Under Test (DUT)
 - ☒ Goal: Find a SMALL set of test vectors that has a BIG fault coverage
- Testers
 - ☒ Clock rate in the range of GHz
 - ☒ Resolutions measured in psec
 - ☒ Large very fast memory
 - ☒ Cost 1 - 5 million dollars


Fault Models

 - Modeling physical faults is complex
- **Need models** that simplify the behavior of faults




Stuck-At Fault



Stuck-at-0

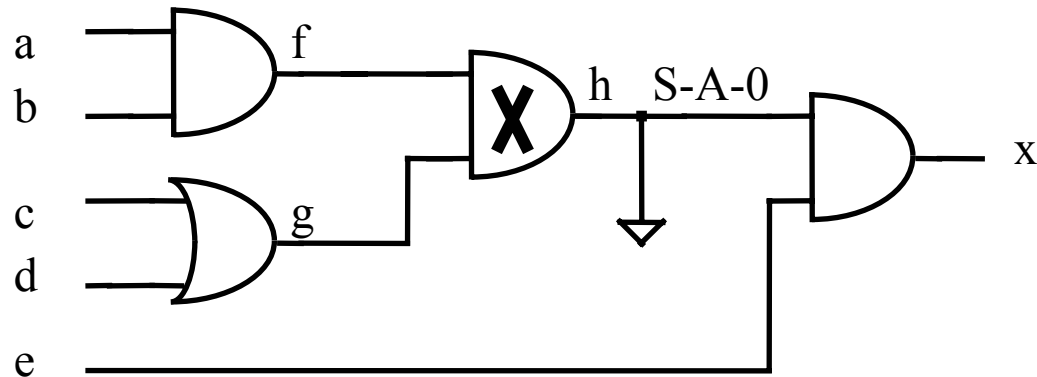

Stuck-at-1

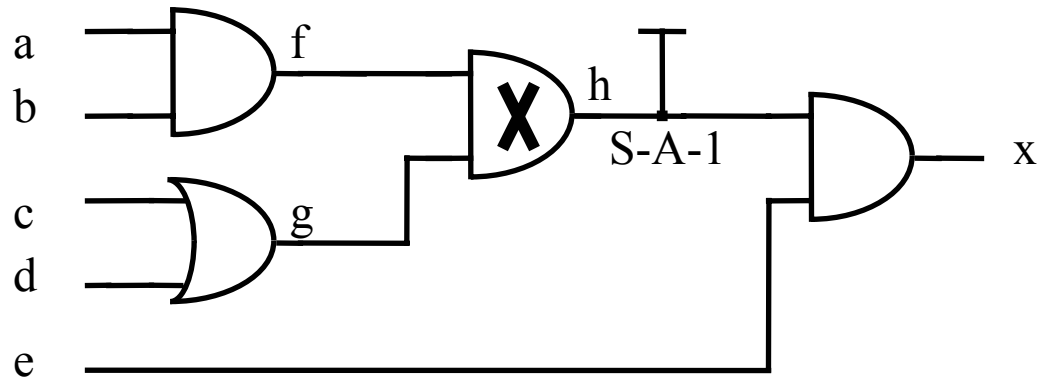

Bridge & Stuck Open

  

Automatic Test Pattern Generation (ATPG)

- Given a logic circuit:
 - ☒ Generate test program to cover all SA faults

- The D-Algorithm
 - ☒ The D-Calculus
 - ☒ Problem: Reconvergent Fanouts

D-Algorithm



- Step 1: Choose a fault to “insert”
 - ☒ Select from a fault dictionary

- Step 2: Activate (excite) the fault
 - ☒ Drive the faulty node to the opposite value of the fault
 - ☒ Example: for SA-1, drive the node to 0


- Step 3: Sensitize a path to an output
 - ☒ Propagate the fault so that it can be observed at the output pin

Path Sensitization

Goals: Determine input pattern that makes a fault controllable (triggers the fault, and makes its impact visible at the output nodes)




Fault enabling

Fault propagation

 

Techniques Used: D-algorithm, Podem

D-Algorithm

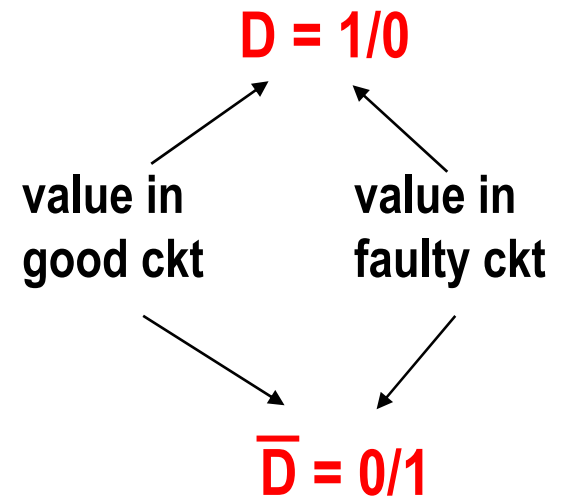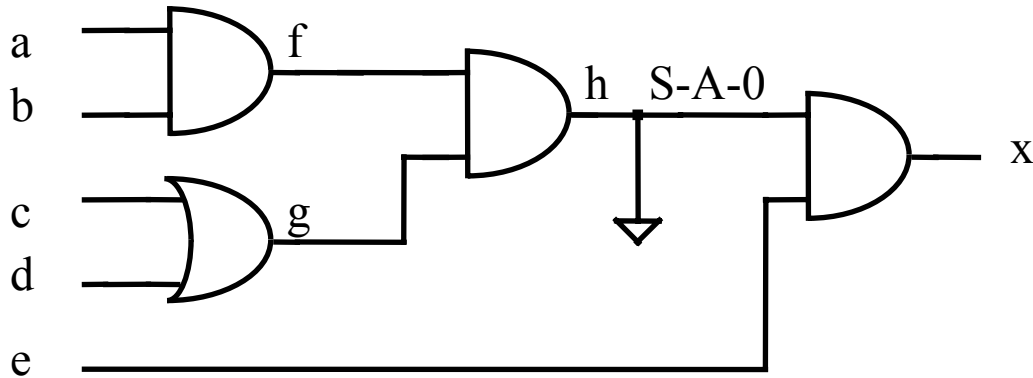 

D-Algorithm

Five value logic simulation

$X = \text{NOT}(A)$

A	X
0	1
1	0
X	X
D	\bar{D}
\bar{D}	D

$X = AB$

A	B				
	0	1	X	D	\bar{D}
0	0	0	0	0	0
1	0	1	X	D	\bar{D}
X	0	X	X	X	X
D	0	D	X	D	0
\bar{D}	0	\bar{D}	X	0	\bar{D}


D-Algorithm

Five value logic simulation


$$X = A + B$$

A	B				
	0	1	X	D	\bar{D}
0	0	1	X	D	\bar{D}
1	1	1	1	1	1
X	X	1	X	X	X
D	D	1	X	D	1
\bar{D}	\bar{D}	1	X	1	\bar{D}

D-Algorithm

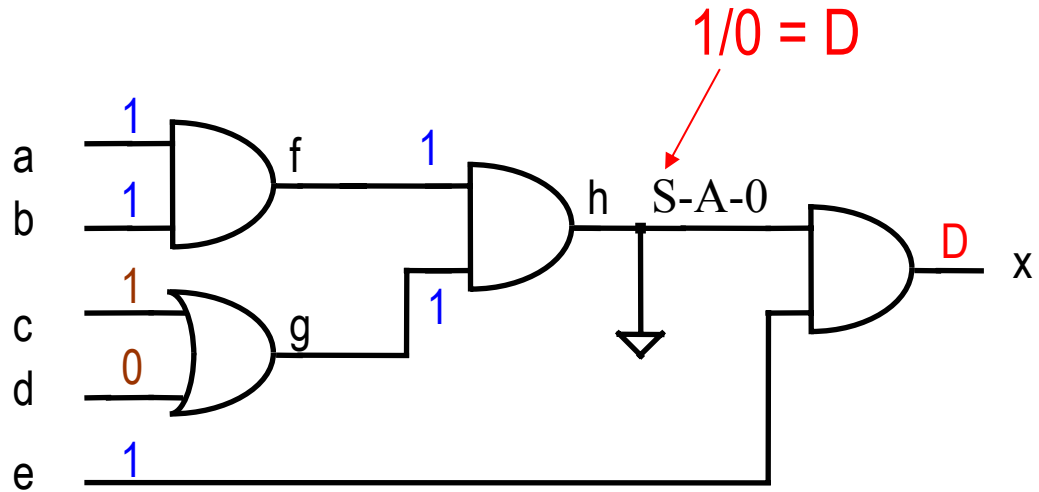

D-Algorithm

 


Conflict !

Need backtracks

Reconvergent Fanout

x

Fault Simulation

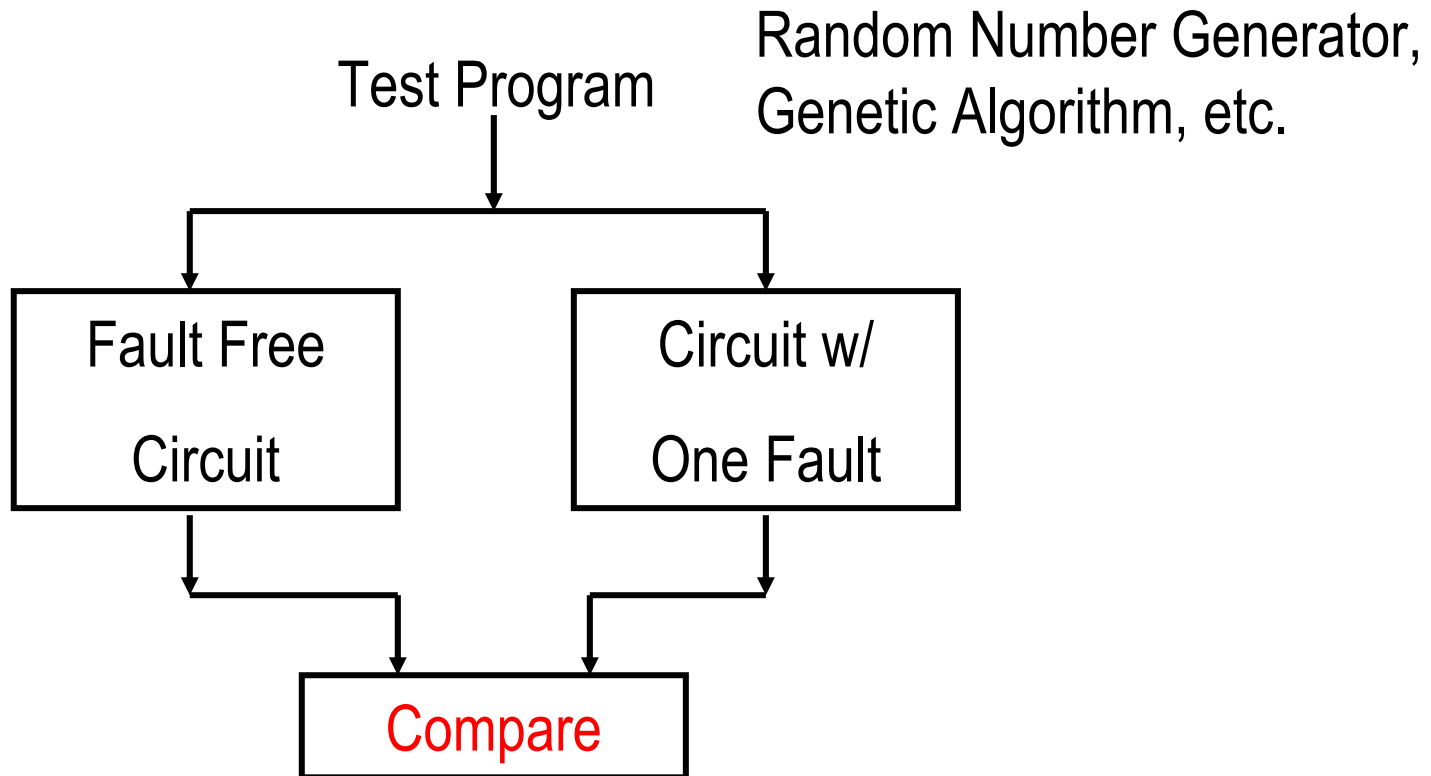


Path Delay Fault

- A defect can affect the speed of a path in the circuit




- Let's see a Path Delay Fault example

 

Path Delay Fault

Path \uparrow c-g2-g4-g5-x

 

Outline



✓ Defects and Faults

- ☒ Reasons for IC malfunctioning

✓ Fault Modeling


- ☒ Types of faults (Stuck-At, bridge, Stuck Open)

- ☒ Automatic Test Pattern Generation


- ☒ Path Delay Fault

■ Design for Testability


Scan-based Test

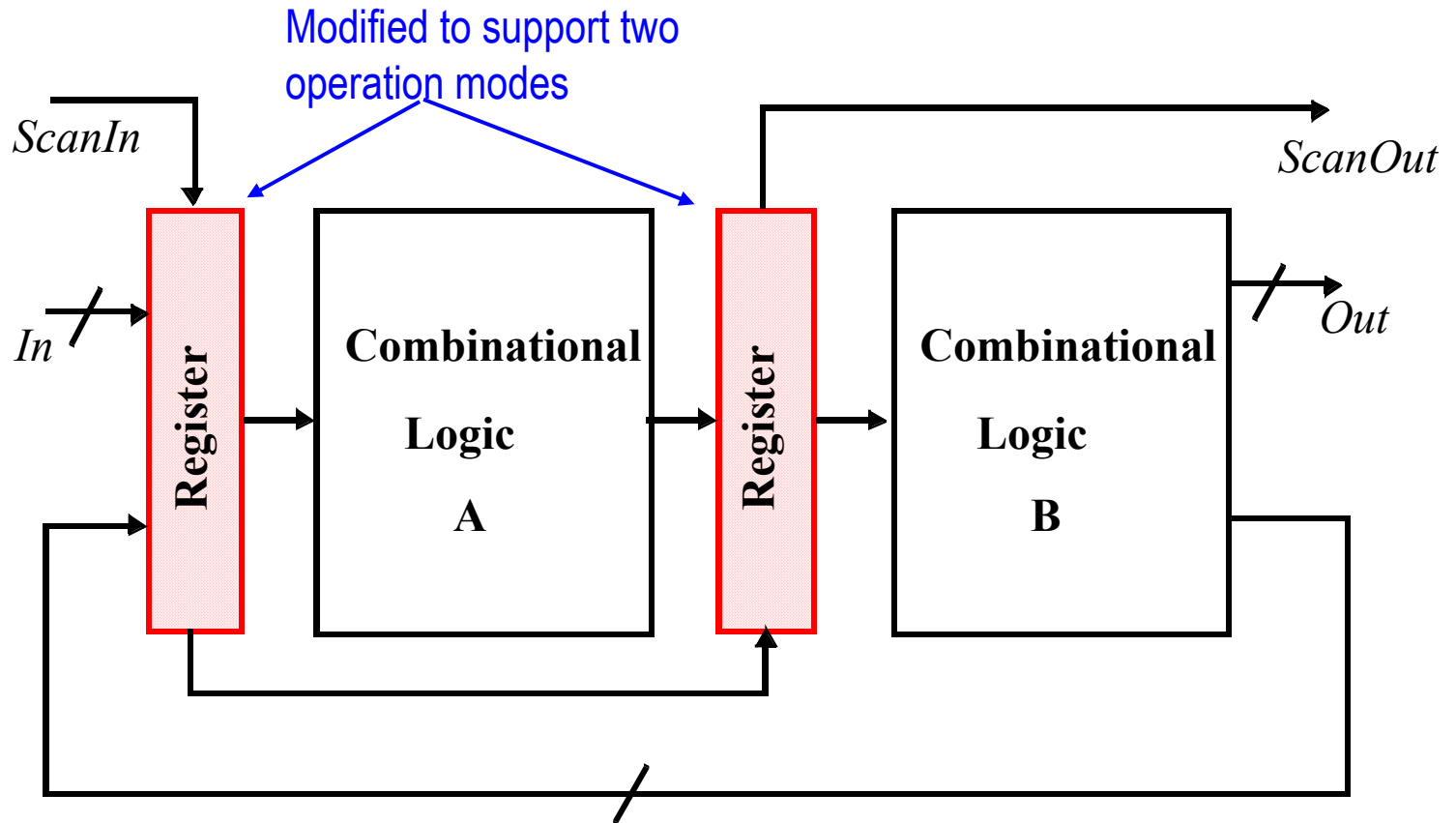


Scan Based Methods

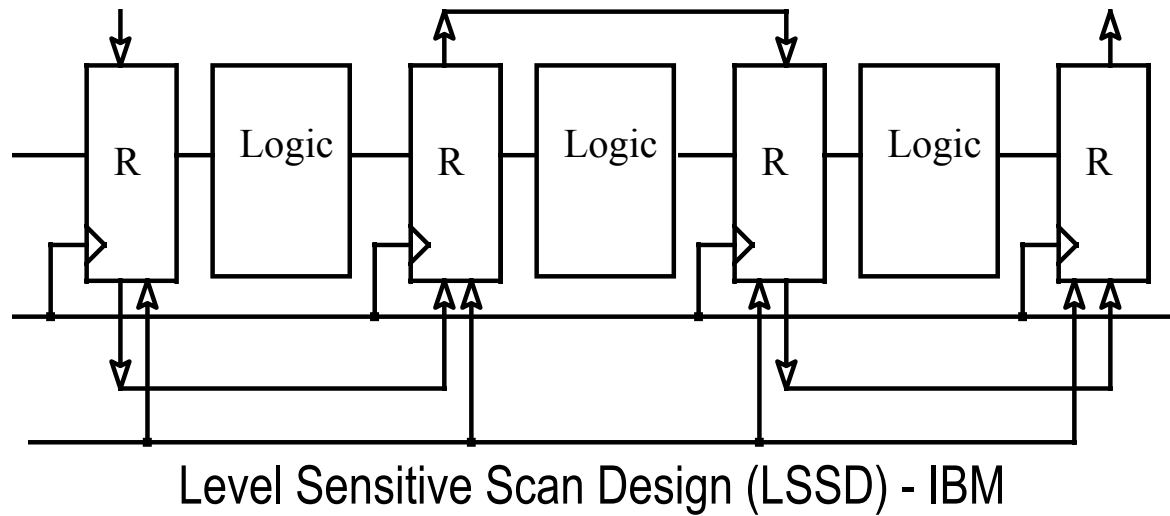


Test Mode: OFF

 

Test Mode: ON

 


Boundary Scan (JTAG: IEEE 1149.1b)

 


Board testing becomes as problematic as chip testing

Built-In Self-Testing (BIST)

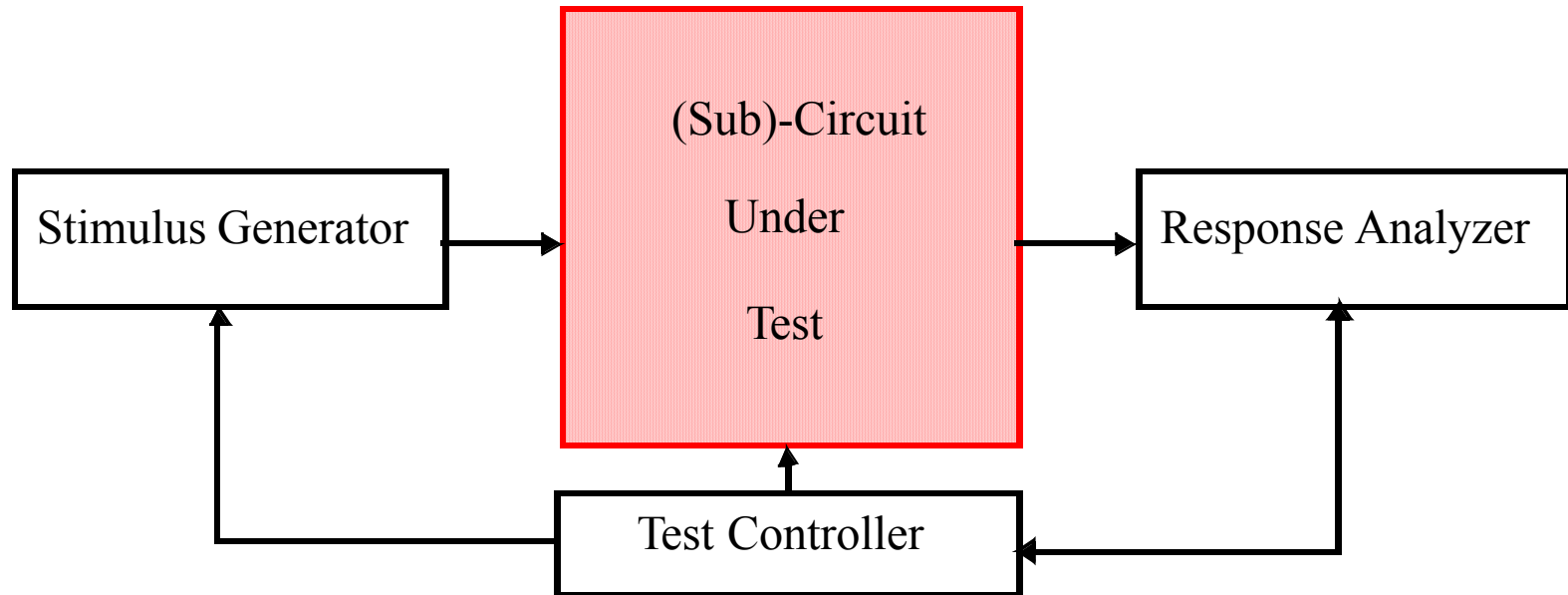

Rapidly becoming more important with increasing chip-complexity and larger modules

Linear-Feedback Shift Register (LFSR)

 

Pseudo-Random Pattern Generator