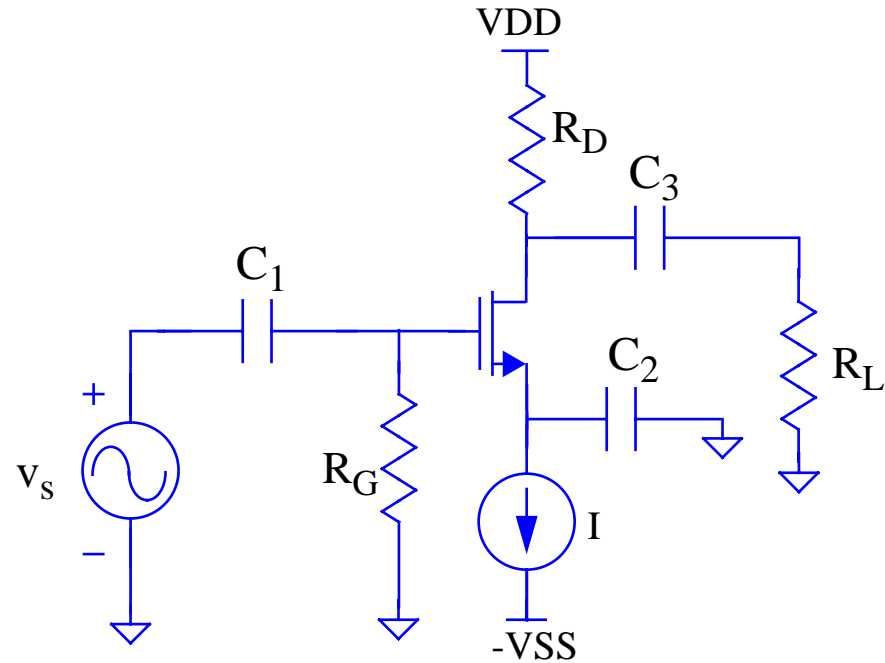



## Common Source Amplifier



- A discrete common source amplifier can be constructed that is very similar in form to a common emitter
- Biasing with a current source is quite common, particularly for ICs
- But IC amplifiers do not include decoupling/bypass capacitors and biasing resistors
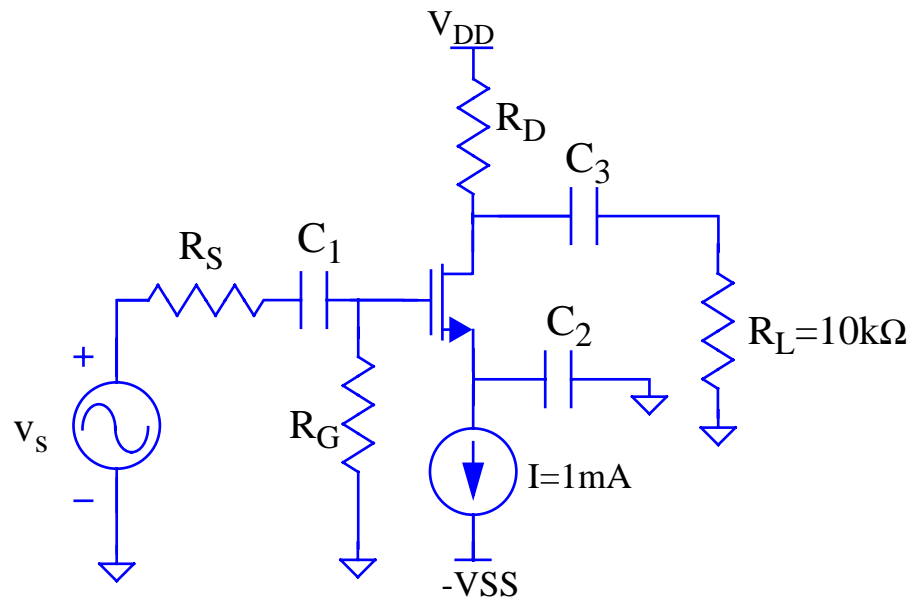
# Common Source Amplifier

- Design the amplifier for maximum possible output voltage swing



$$K=0.25\text{mA/V}^2$$


$$V_t=2\text{V}$$

$$V_{DD}=10\text{V}$$

$$R_G=500\text{k} \ (\gg R_S)$$

$$\lambda=0.02$$

# Common Source Amplifier

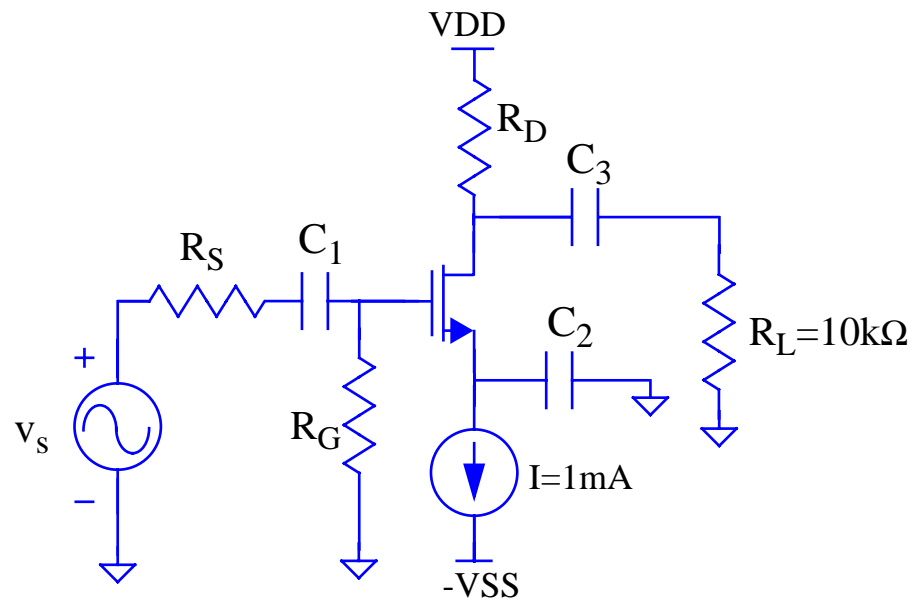

$$K=0.25\text{mA/V}^2$$


$$V_t=2\text{volts}$$

$$V_{DD}=10\text{volts}$$


$$R_G=500\text{k} (\gg R_S)$$
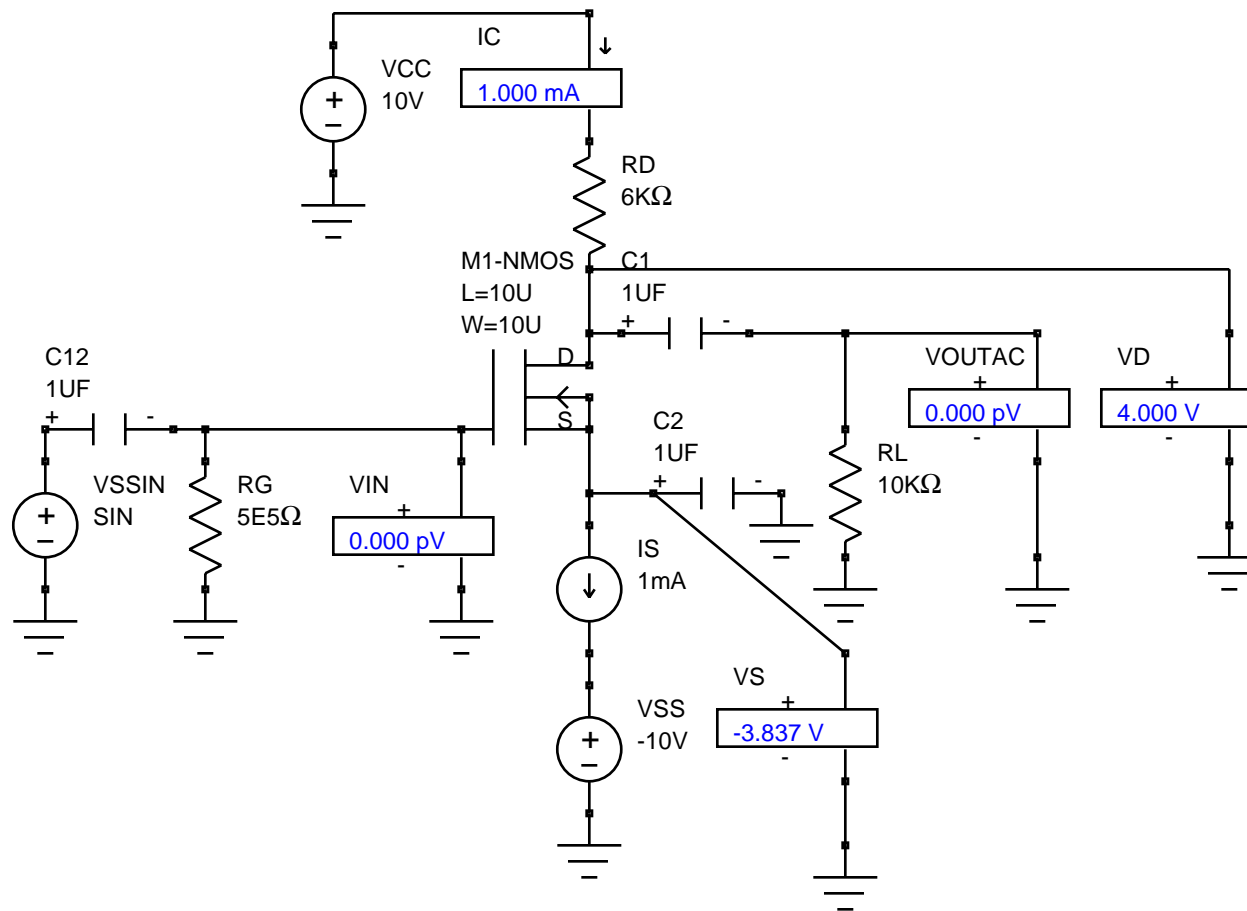
# Common Source Amplifier


- Analyze the circuit --- first solve for the dc bias point:



## Small Signal Model

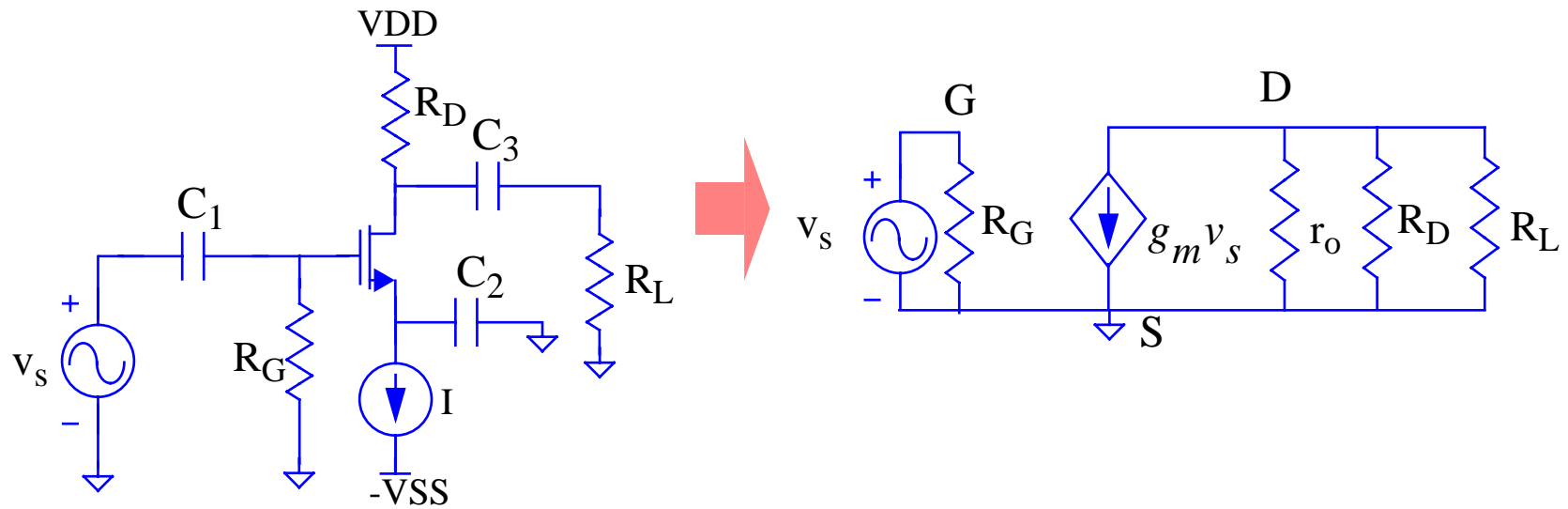


## Small Signal Model

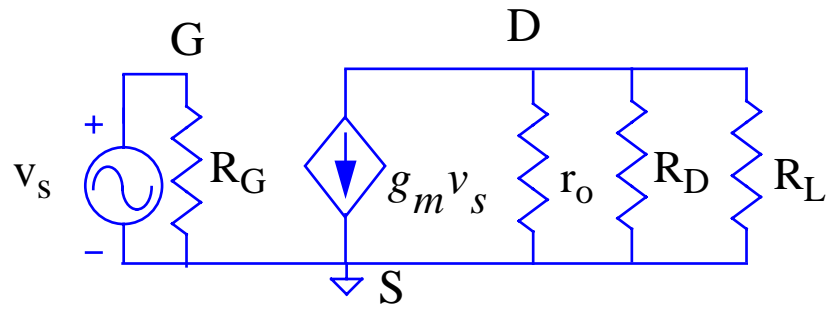


# ac Response

- Frequency response with lamda=0.02

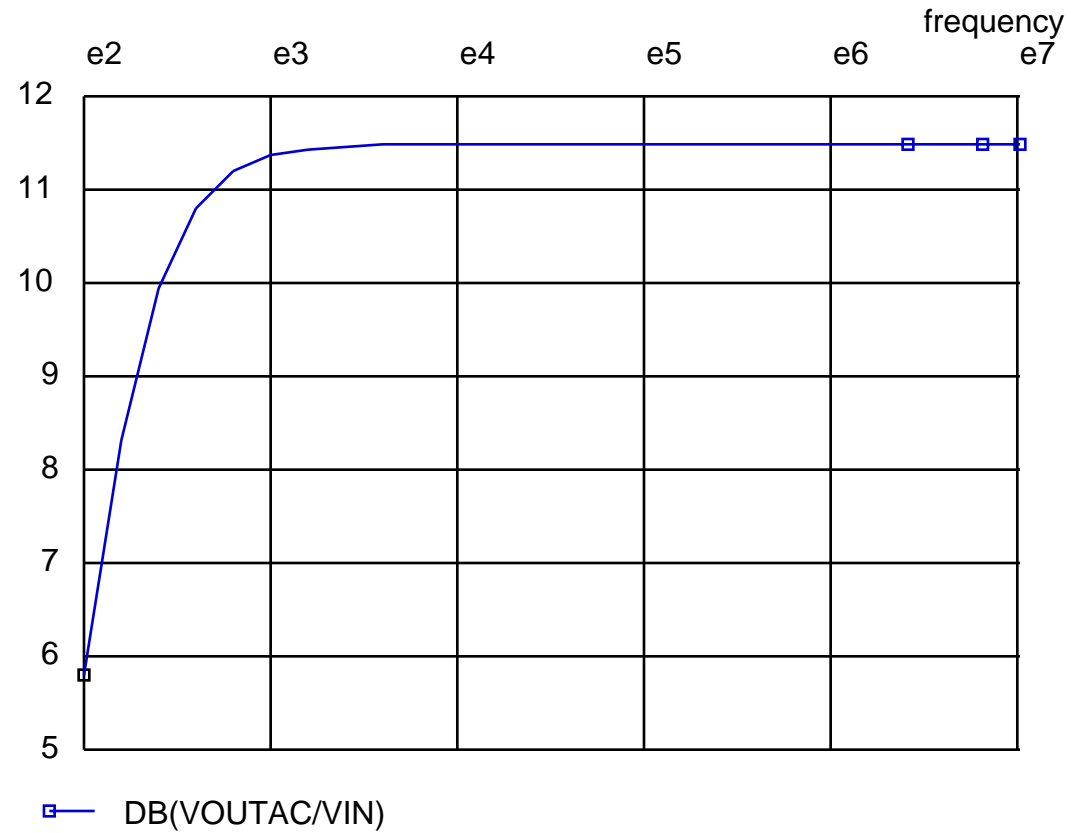
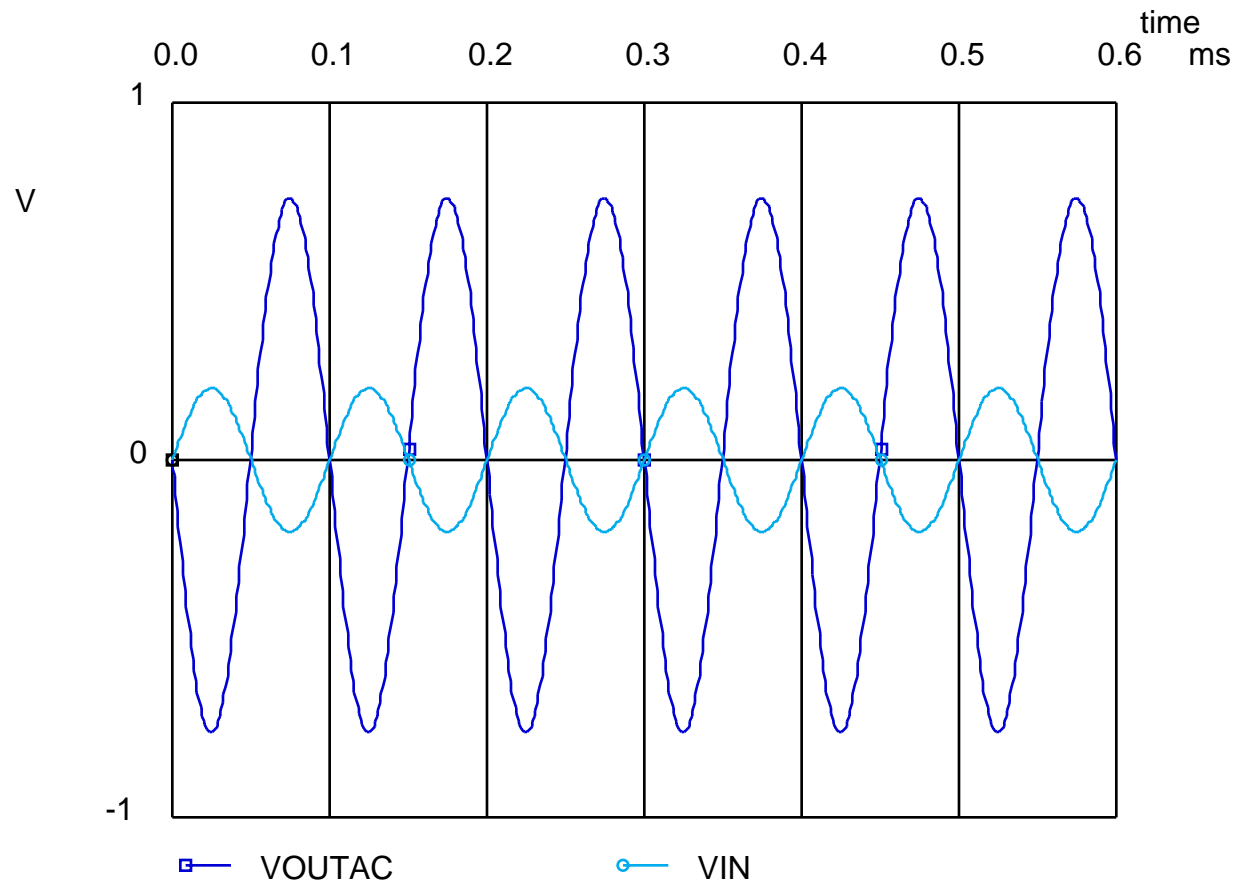
# Transient Response


- Time-domain response for a 10kHz, 0.2v peak ac input signal with  $\lambda=0.02$





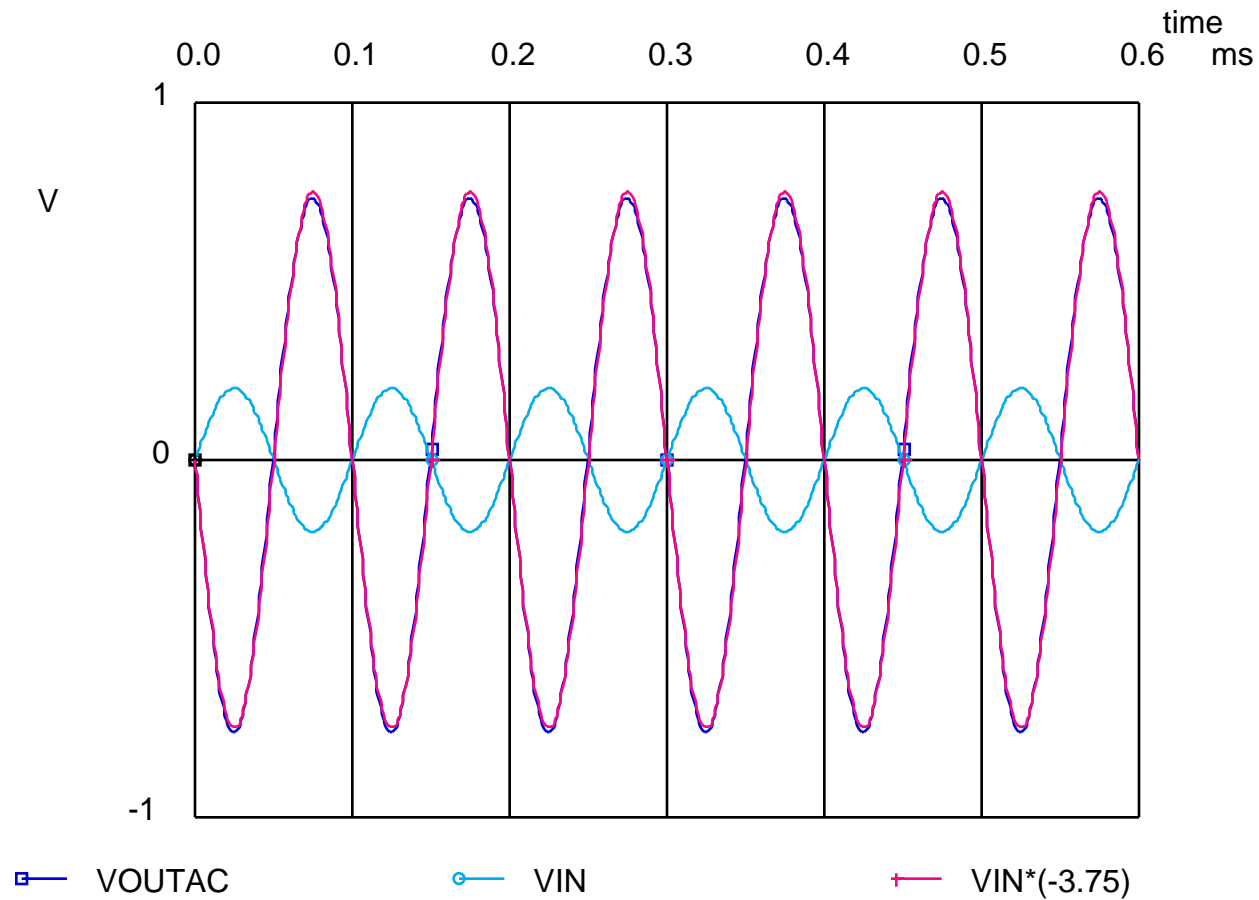
## Transient Response Distortion?

- $V_{in}$  multiplied by the midband gain, and shifted in phase by  $180^\circ$  demonstrates that there is very little distortion



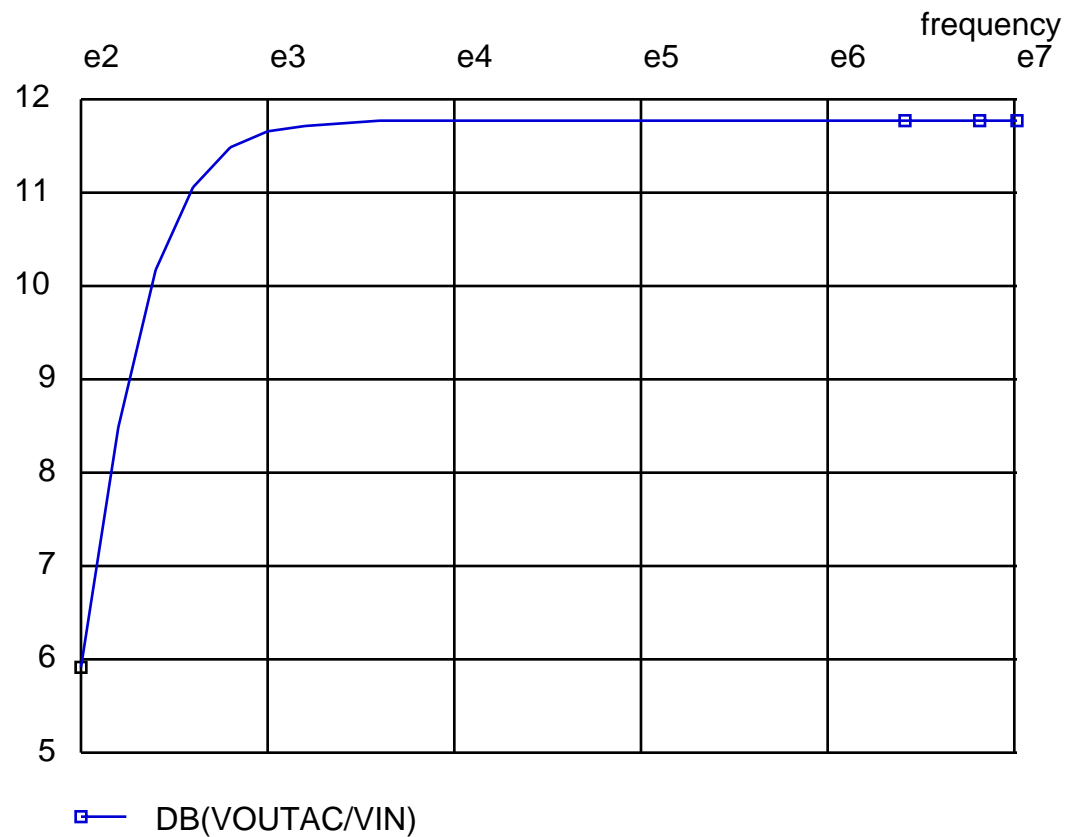
## ac Response

- Response for a 10kHz, 0.2v peak ac input signal with  $\lambda=0$
- How can we change the design so that  $\lambda$  is practically zero?



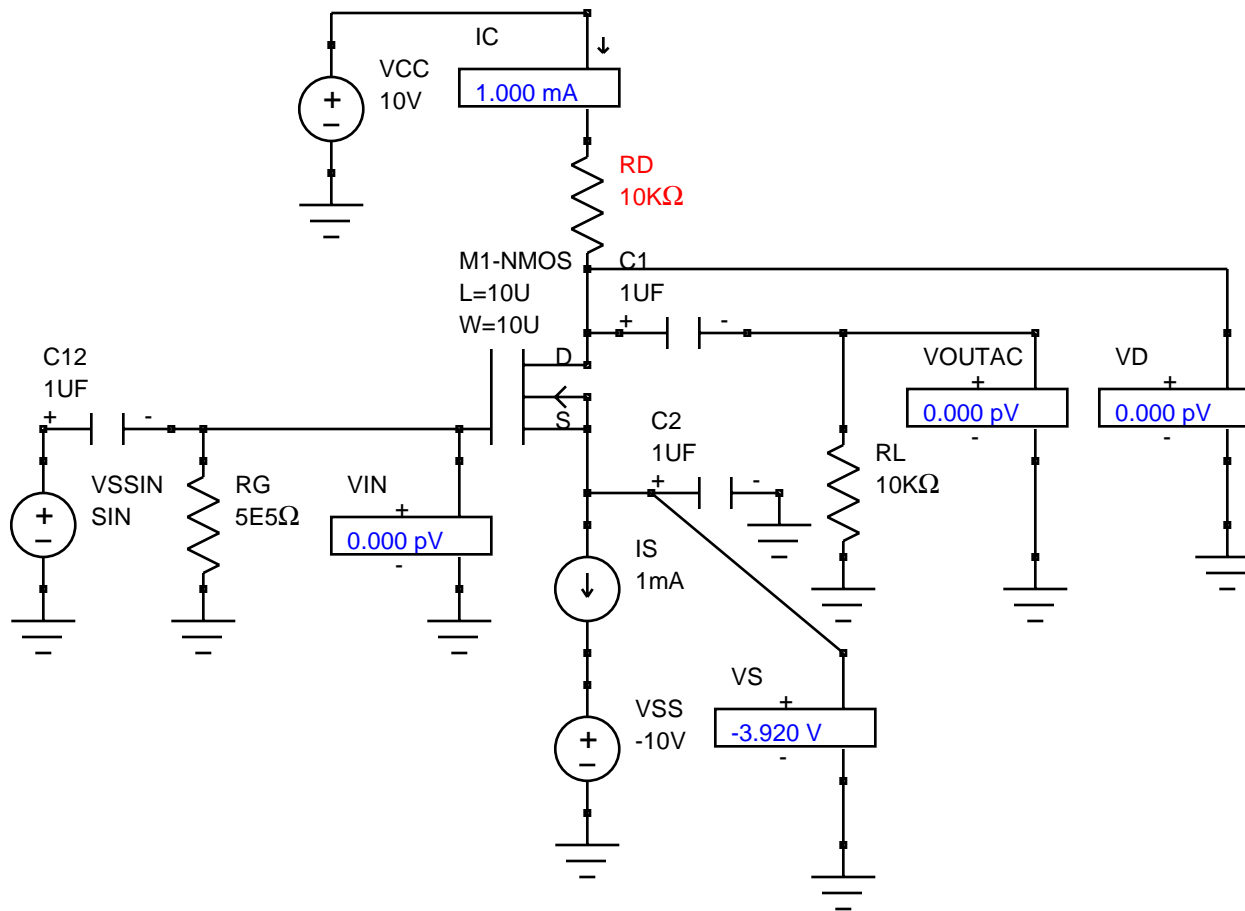
## Improving the Gain

- Assuming that the peak ac output is less than 1.0 volt, we can use a larger value of  $R_D$  to increase the gain but still keep the transistor out of the triode region




# Improving the Gain

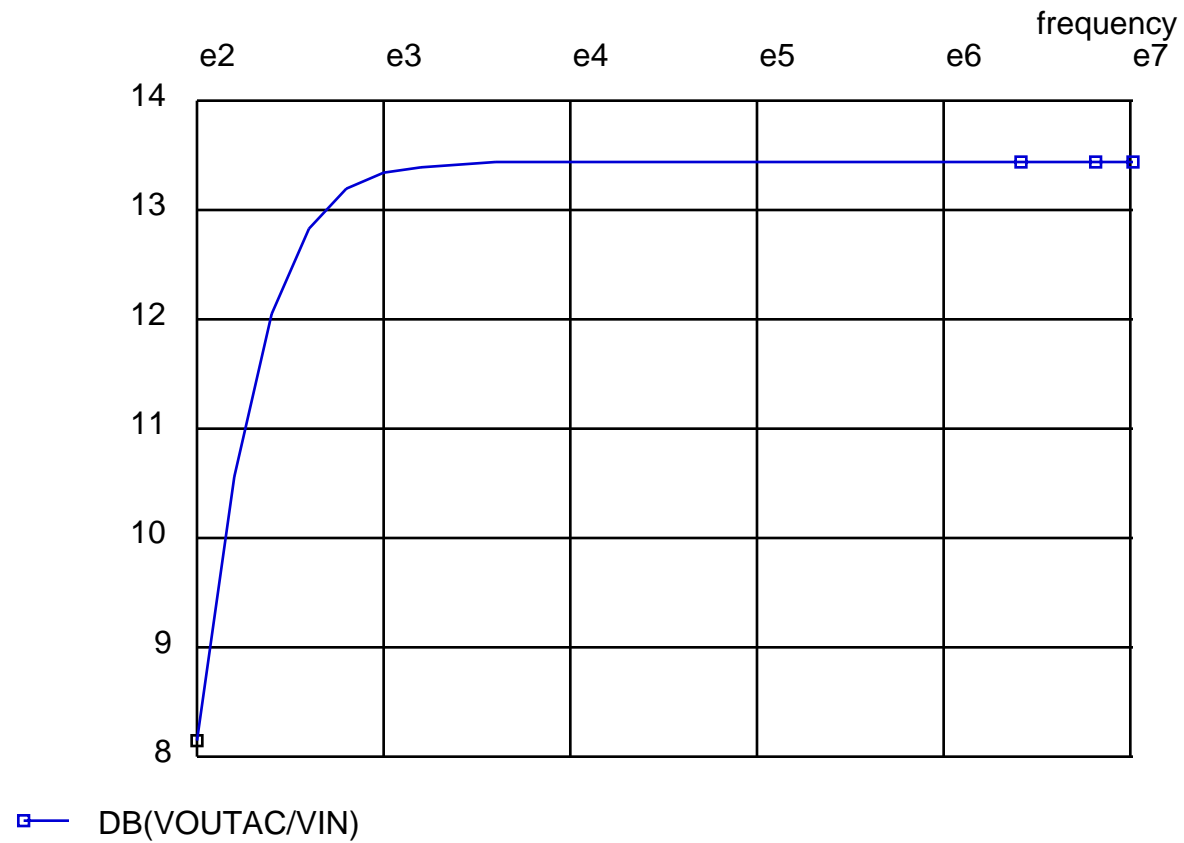

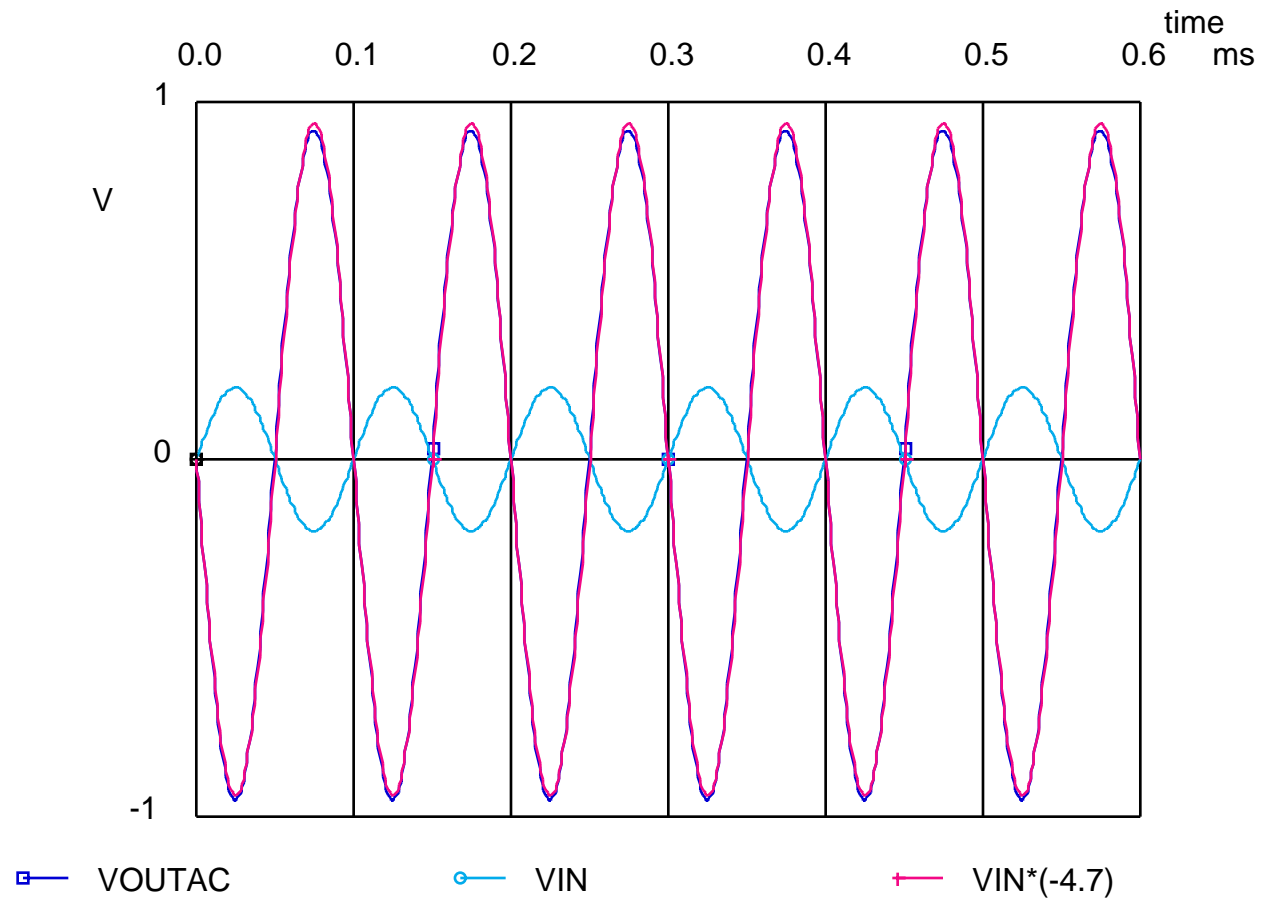
## Improving the Gain

- But further increase in  $R_D$  is not possible



# Current Mirrors

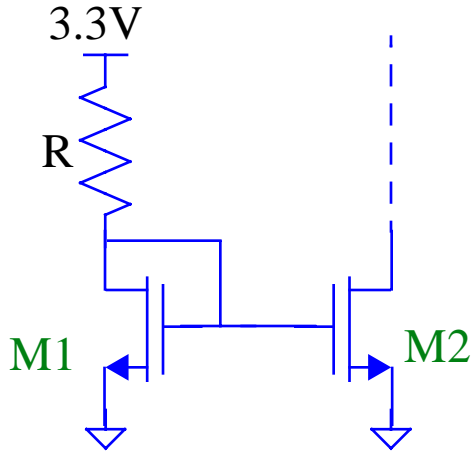



# Current Mirrors-Accuracy

