
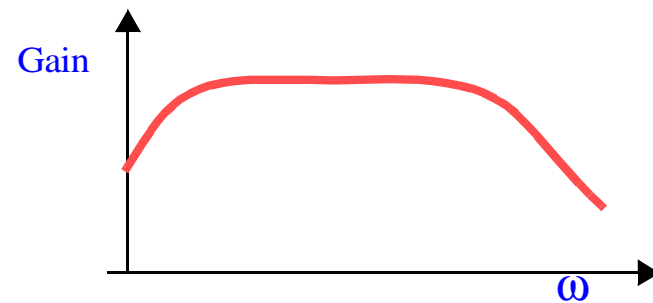
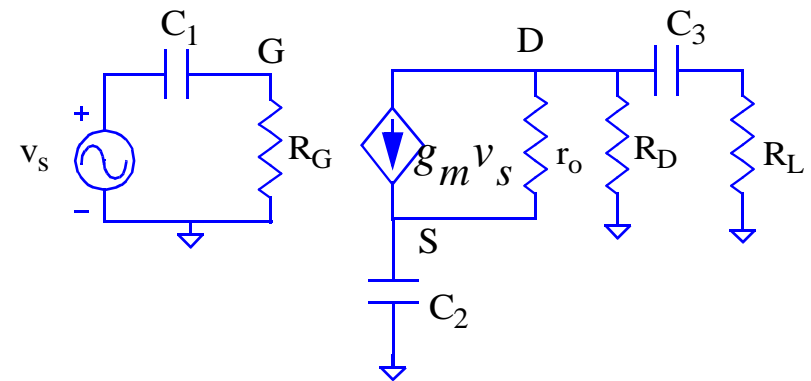




Discrete Amplifier Design: Low Frequency Response

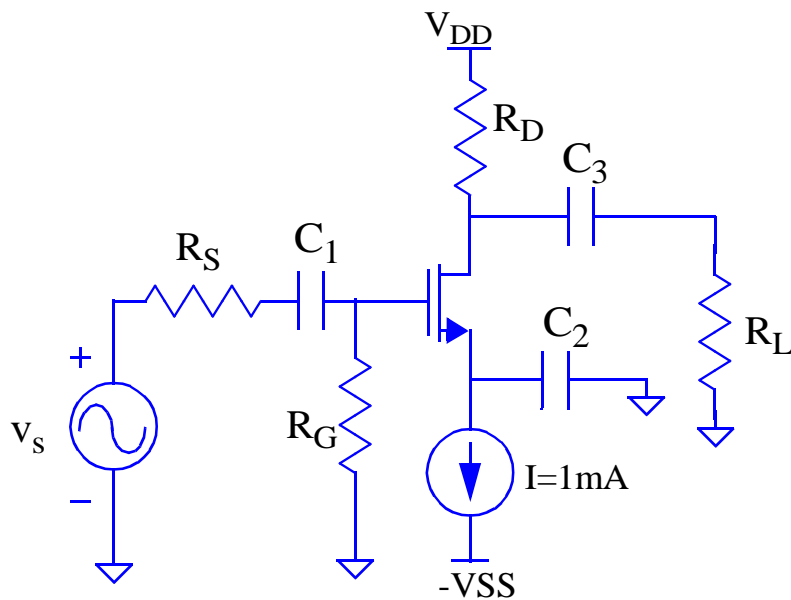- Are decoupling C's large enough? Is bypass C large enough?
- Why not just use the largest values available?




Design Selection of C_C Value

- In general we have to worry about both the **added C's** and the **parasitic C's**
- An approximate expression for the low frequency response as a function of C_C can help us to design coupling capacitor
- Similarly, an approximate expression for the high frequency response as a function of the parasitic capacitance would help in achieving the required bandwidth
- We simplify the analysis with some observations:
 - 1.) At mid-band frequencies we know that the C's do not matter (why?)
- Hypothetical amplifier example:

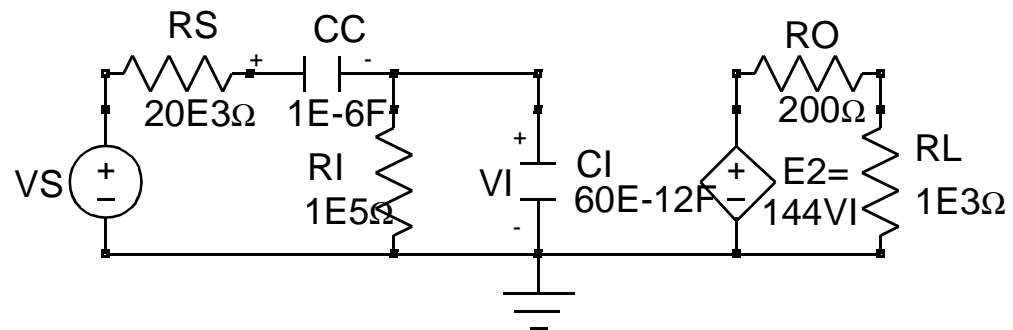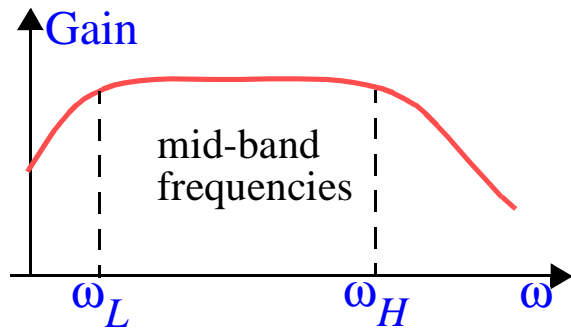


Impact of Decoupling and Parasitic C's

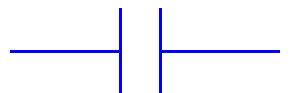
- For frequencies $> \omega_L$ the impedance due to C_C is practically zero compared to other impedances (behaves like a short circuit) due to the large value of C
- Only at extremely small frequencies is Z_{CC} a significant impedance



$$Z_{C_C} = \frac{1}{j\omega C_C}$$

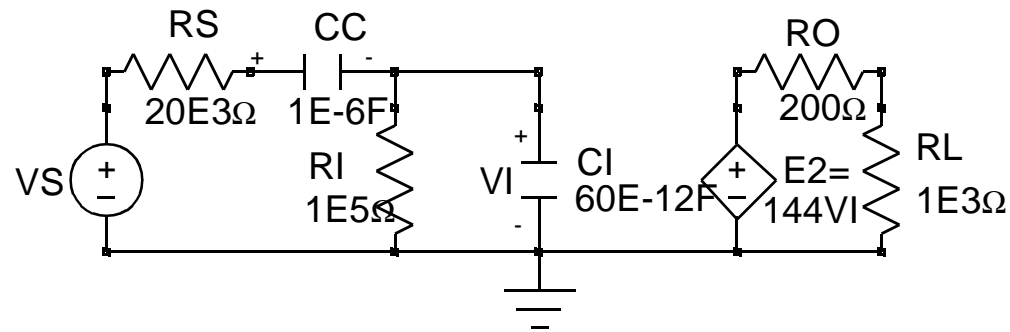

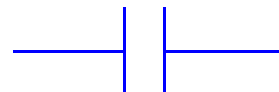
- In contrast, the internal (parasitic) capacitor, C_I behaves like an infinite impedance (open circuit) over the mid-band frequency range, because C_I is small




$$Z_{C_I} = \frac{1}{j\omega C_I}$$

Bandwidth Approximations

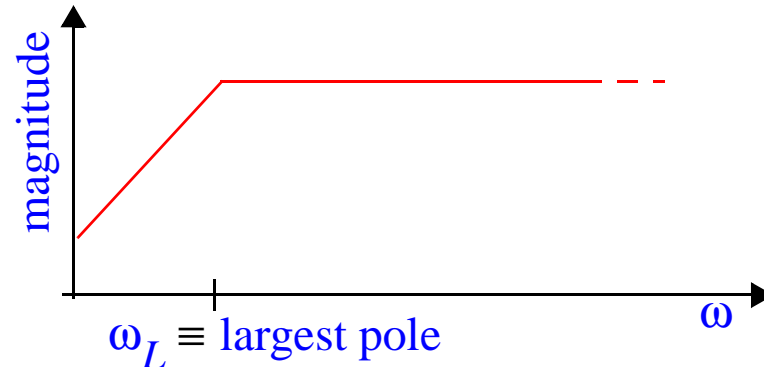- At low frequencies, the frequency response is like a high pass filter



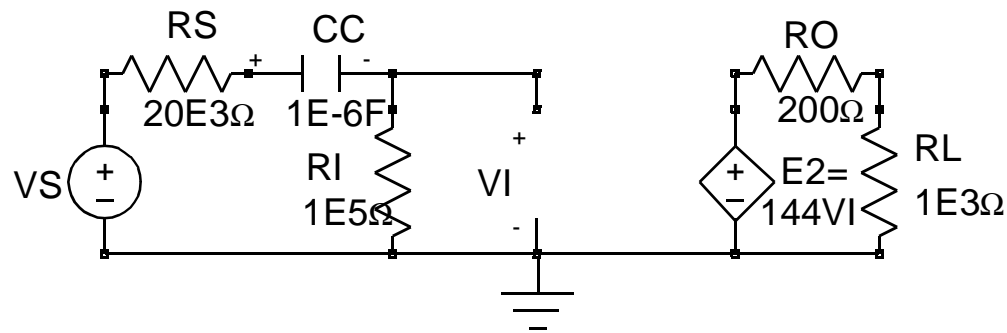
- So the **largest pole** associated with the **low frequency equivalent circuit** represents the low frequency 3dB cutoff point (with parasitic C's opened):




Assuming that there are no other low frequency poles or zeros nearby

Bandwidth Approximations

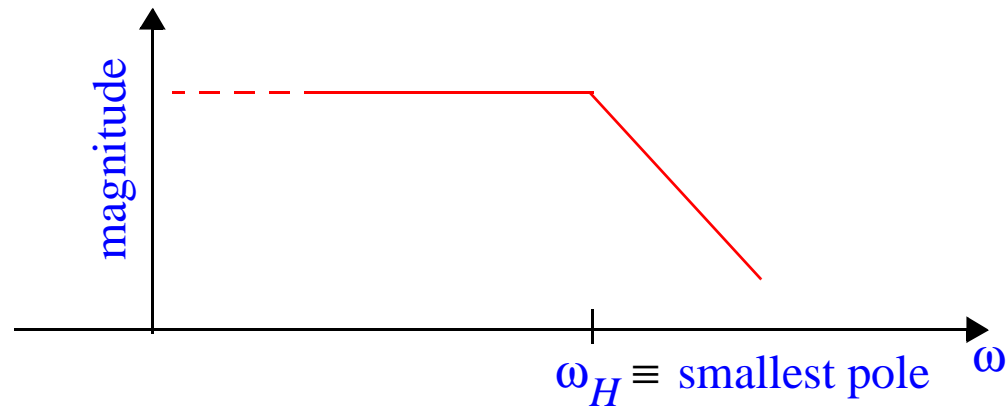- At high frequencies, the frequency response is like a low pass filter




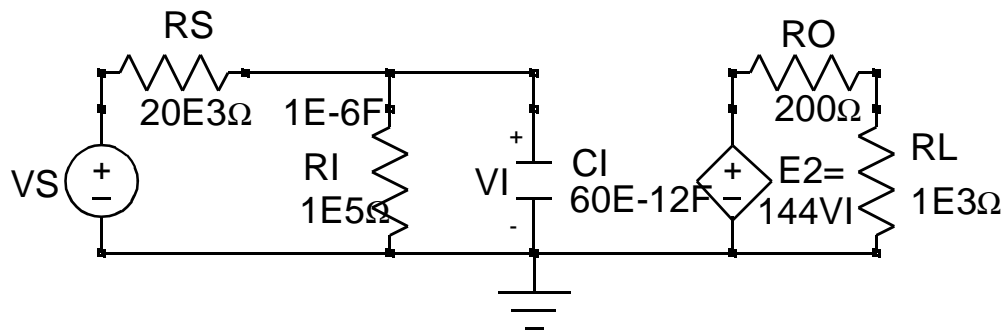- So the **smallest pole** associated with the **high frequency equivalent circuit** represents the high frequency 3dB cutoff point
- The high frequency equivalent circuit is (with decoupling C's shorted):




Amplifier Magnitude with C_C

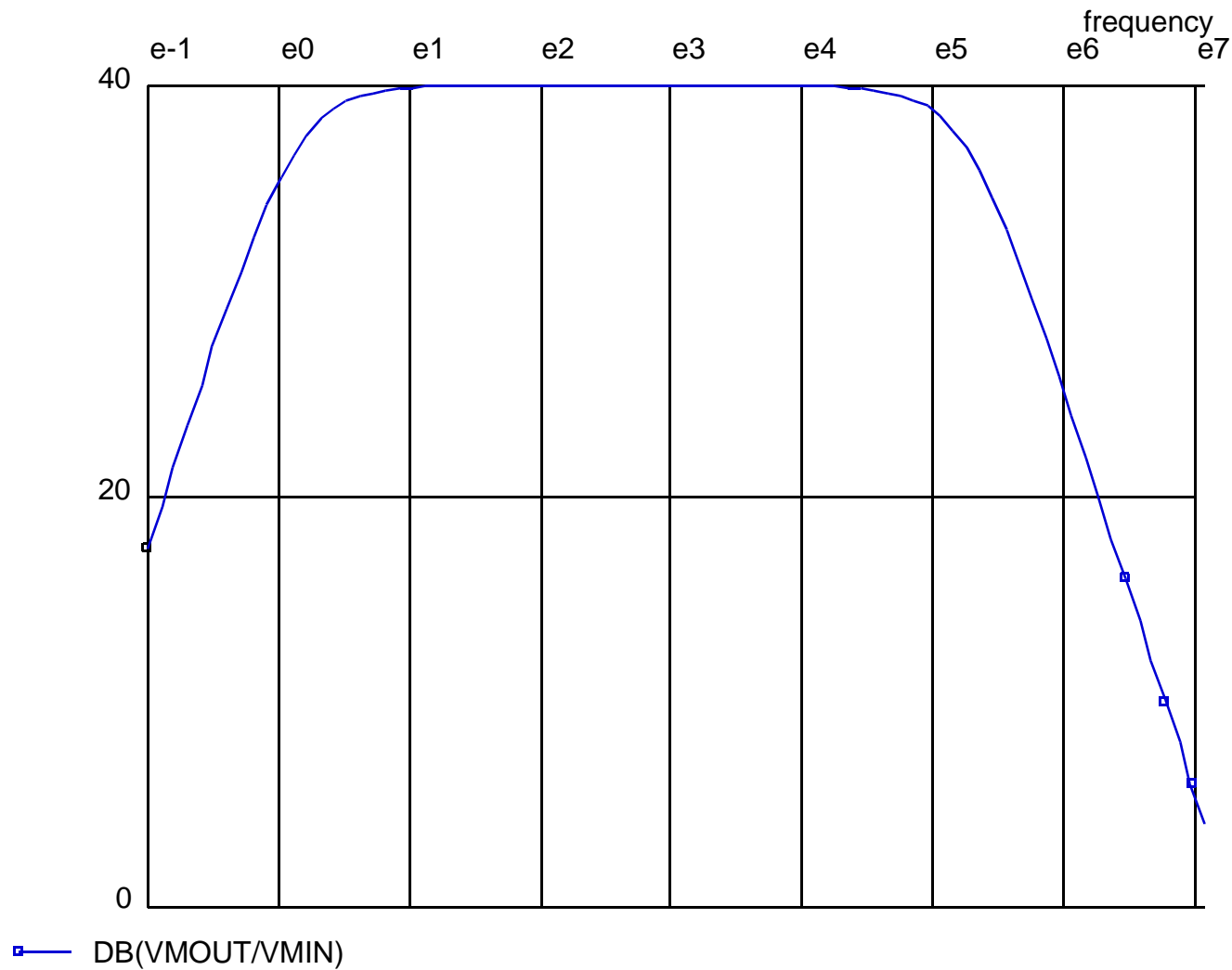- Excellent agreement, but these low and high frequency equivalent circuits contained only one pole each



Open- and Short-Circuit Time Constants

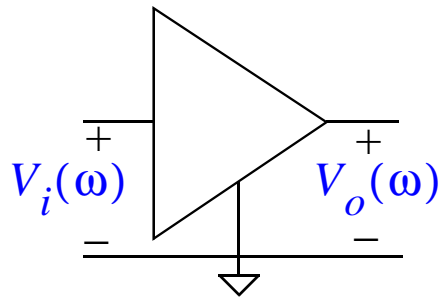- Approximating the 3dB frequencies in terms of the smallest and largest poles of the high- and low-frequency equivalent circuits can be done when there are more poles in the circuit too
- In such cases the smallest and largest poles are approximated in terms of the open and short circuit time constants respectively



$$T(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{1 + a_1s + a_2s^2 + \dots + a_ms^m}{1 + b_1s + b_2s^2 + \dots + b_ns^n}$$

$$= K \frac{1 + a_1s + a_2s^2 + \dots + a_ms^m}{\left(\frac{s}{p_1} + 1\right)\left(\frac{s}{p_2} + 1\right)\dots\left(\frac{s}{p_n} + 1\right)}$$

- b_1 is the sum of the circuit time constants

Open-Circuit Time Constants

- b_1 can be calculated as the sum of the open circuit time constants¹

Calculate the resistance, R , seen by each capacitor, C , when all other C 's are open, and sum the corresponding RC products

- If the poles are separated from one another, then one pole will dominate the b_1 term


$$b_1 = \sum_{i=1}^n \frac{1}{p_i} \cong \frac{1}{p_1} \cong \frac{1}{\omega_H}$$

- Used to approximate the smallest pole (largest time constant) in the ckt

1. The circuit-theoretic foundation for this result can be found in "Analysis and Design of Analog Integrated Circuits," Gray and Meyer, 3rd edition, John Wiley and Sons, pp. 502-505.

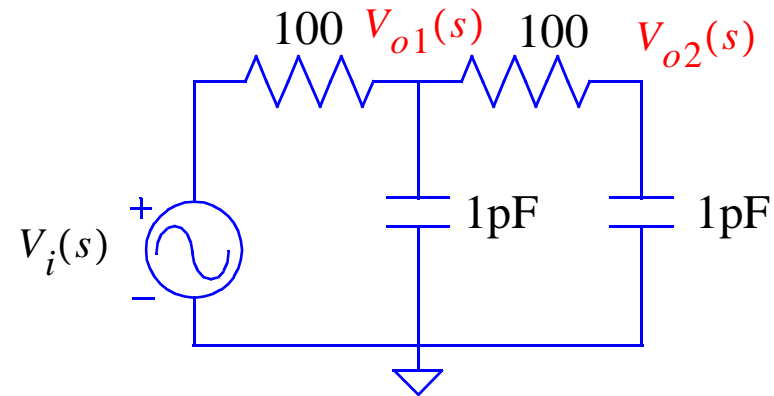Example

- From our simple RC example in lecture 2:




$$H_1(s) = \frac{1}{10^{20}} \cdot \frac{\left(1 + \frac{s}{10^{10}}\right)}{s^2 + s(0.03 \times 10^{12}) + 10^{20}} = \frac{\left(1 + \frac{s}{z}\right)}{\left(\frac{s}{p_1} + 1\right)\left(\frac{s}{p_2} + 1\right)}$$

$$\text{poles} \equiv p_{1,2} = -(-1.5 \times 10^{10} \pm 1.118 \times 10^{10})$$

$$H_2(s) = \frac{1}{\left(\frac{s}{p_1} + 1\right)\left(\frac{s}{p_2} + 1\right)}$$


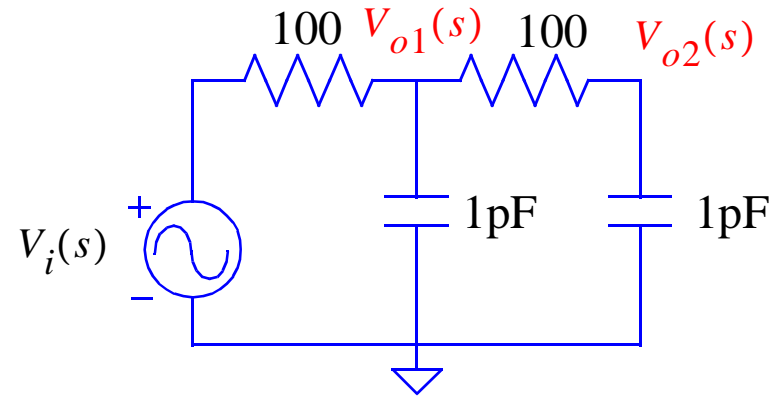
Example

- Calculate the open circuit time constants



SPICE Result

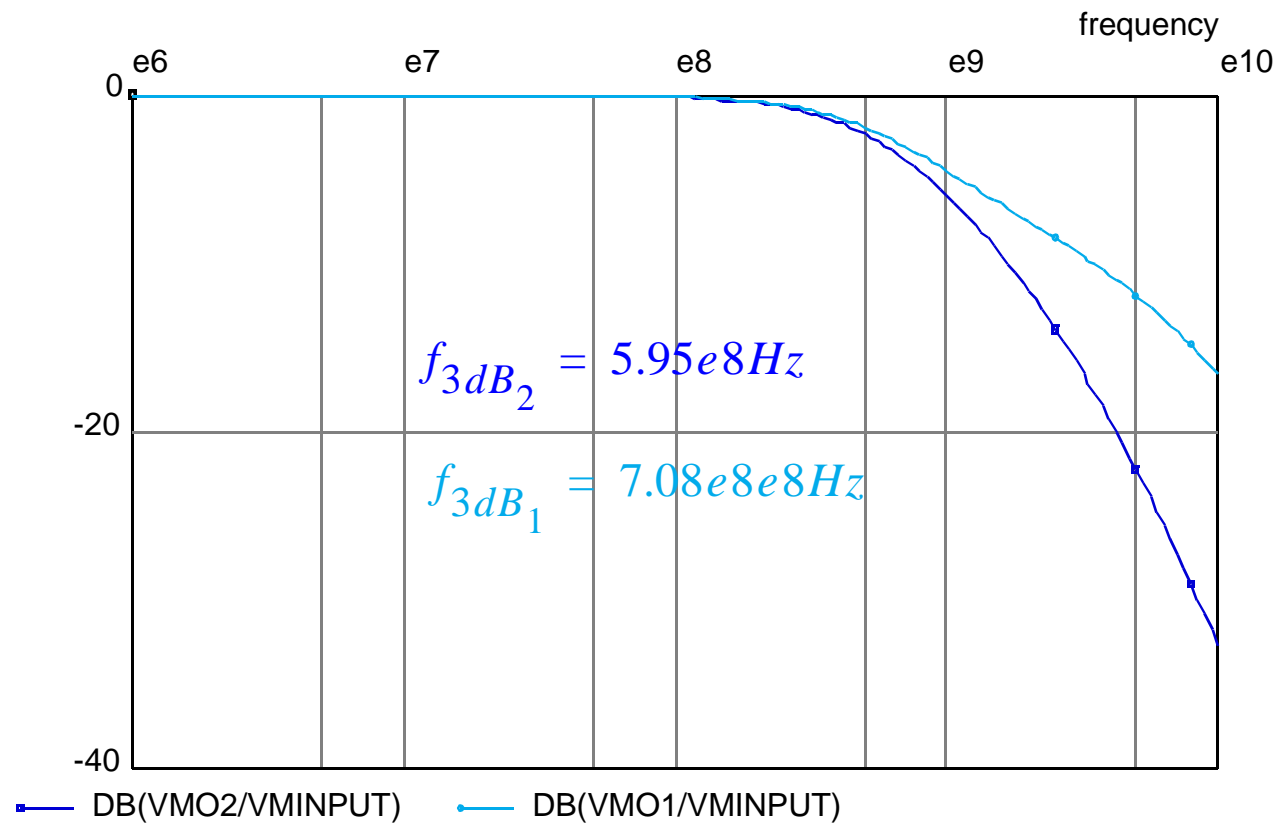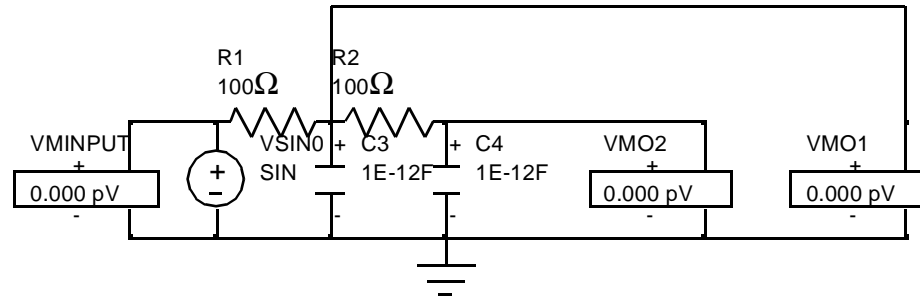- Why is this approximation more accurate for node 2?



Short-Circuit Time Constants

- The largest pole in a circuit can be approximated in a similar way
- First we express the transfer function in the form:

$$T(\omega) = \frac{1 + a_1s + a_2s^2 + \dots + a_ms^m}{1 + b_1s + b_2s^2 + \dots + b_ns^n} = \frac{s^m + d_1s^{m-1} + \dots}{s^n + e_1s^{n-1} + \dots}$$

which can be factored
into the form:


$$= \frac{s^m + d_1s^{m-1} + \dots}{(s + p_1)(s + p_2)\dots(s + p_n)}$$

- e_1 is the sum of the poles
- e_1 can be calculated as the sum of the short circuit reciprocal time constants


Calculate the resistance, R , seen by each capacitor, C , when all other C 's are shorted, and sum the corresponding reciprocal RC products

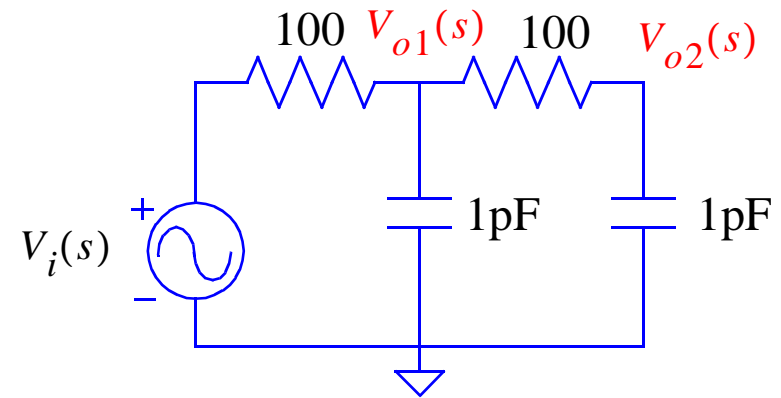Example

- Calculate the short circuit reciprocal time constants




Common Source w/ Decoupling Example

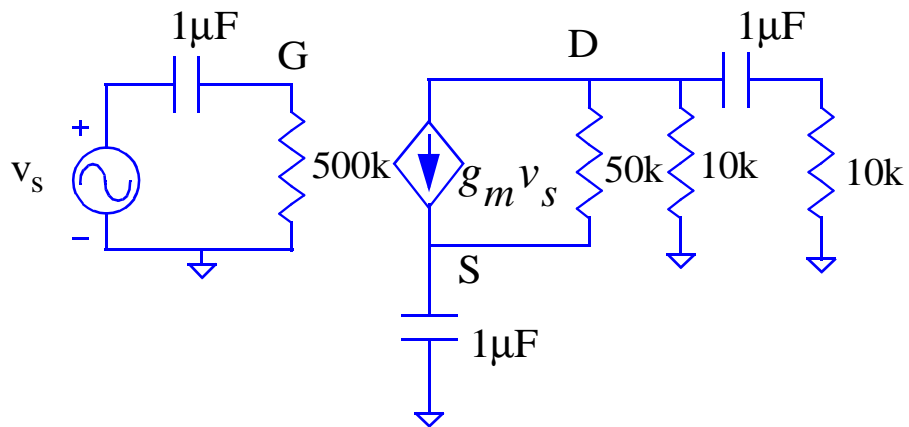

$$g_m = 1\text{m}\frac{\text{A}}{\text{V}}$$


Common Source w/ Decoupling Example

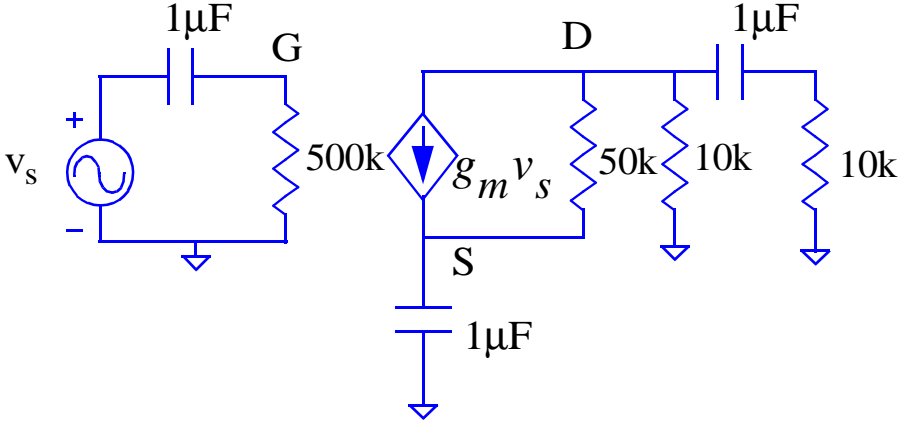

$$g_m = 1\text{mA/V}$$


ac Response

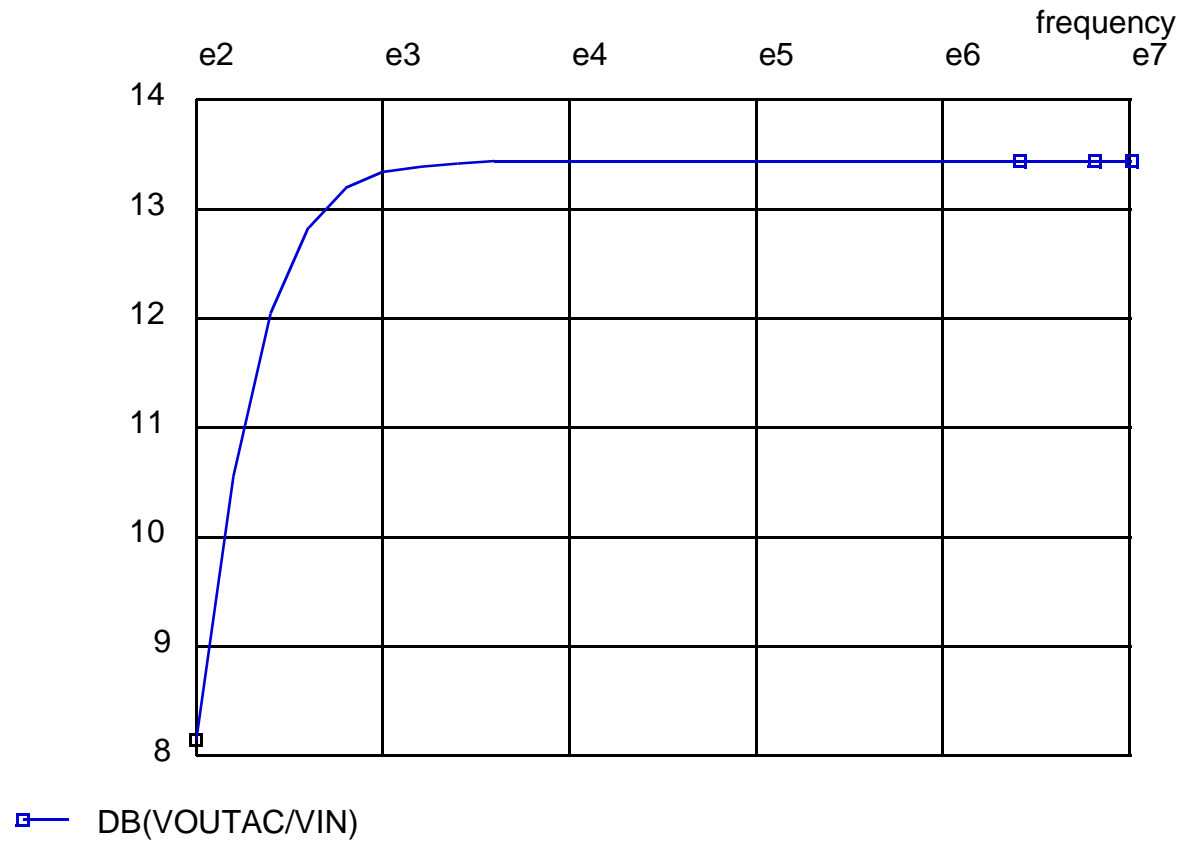- Frequency response for common source amplifier from lecture 22




High Frequency Response

- IC amplifiers do not generally use decoupling since fabricating large C's is costly in terms of silicon area --- **direct coupled amplifiers**
- So we will mainly be interested in the high frequency response for IC amplifiers
- The parasitic capacitances will become evident at high frequencies, especially the **gate to drain capacitor**
- The impact of the gate-to-drain capacitor is amplified by the **Miller Effect**

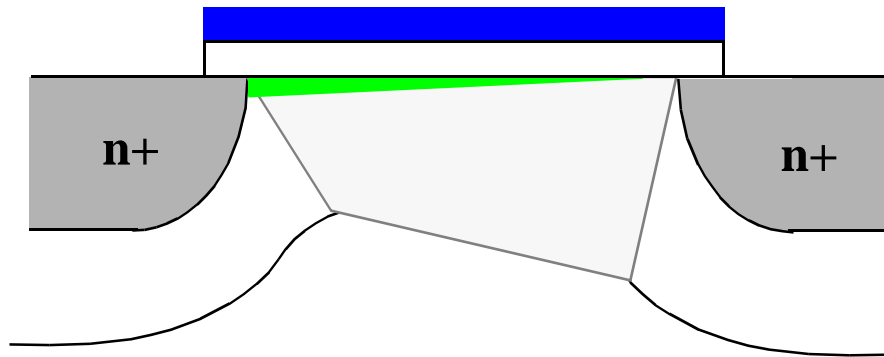


High Frequency Response

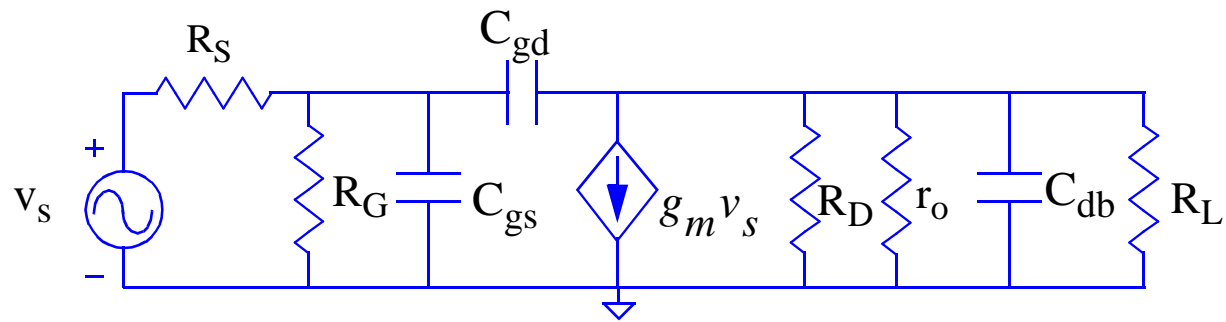- Hypothetical common-source-like amplifier




Miller Effect

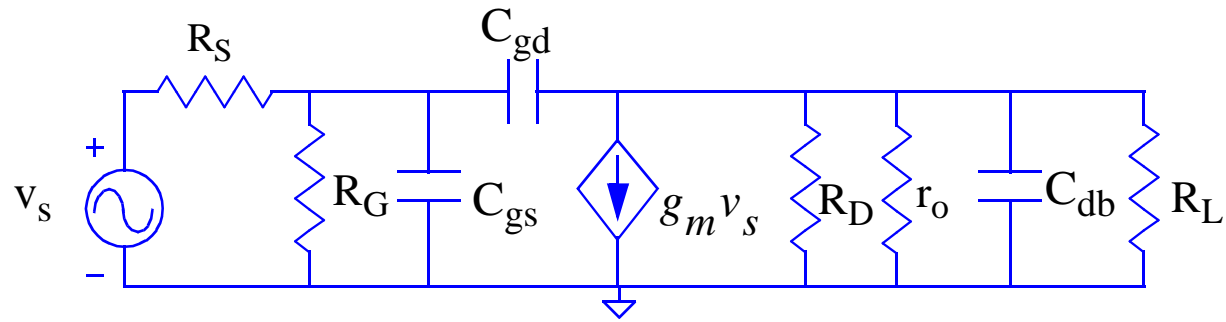

Common Gate

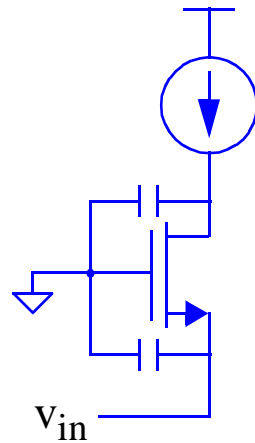- High frequency amplifiers must be designed to minimize the Miller effect
- **Common gate** and **common base** configurations can provide large gains, low input impedance, and improved high frequency behavior
- Why is Miller effect not a factor?



Cascode Amplifiers

- Cascode configurations combine the best of both common emitter (source) and common base (gate)

