
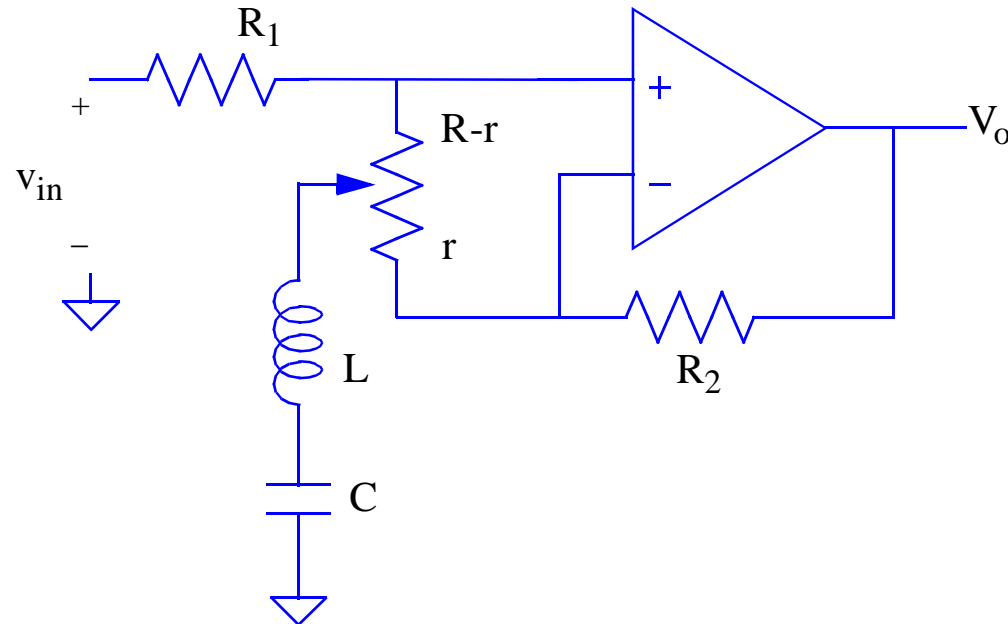

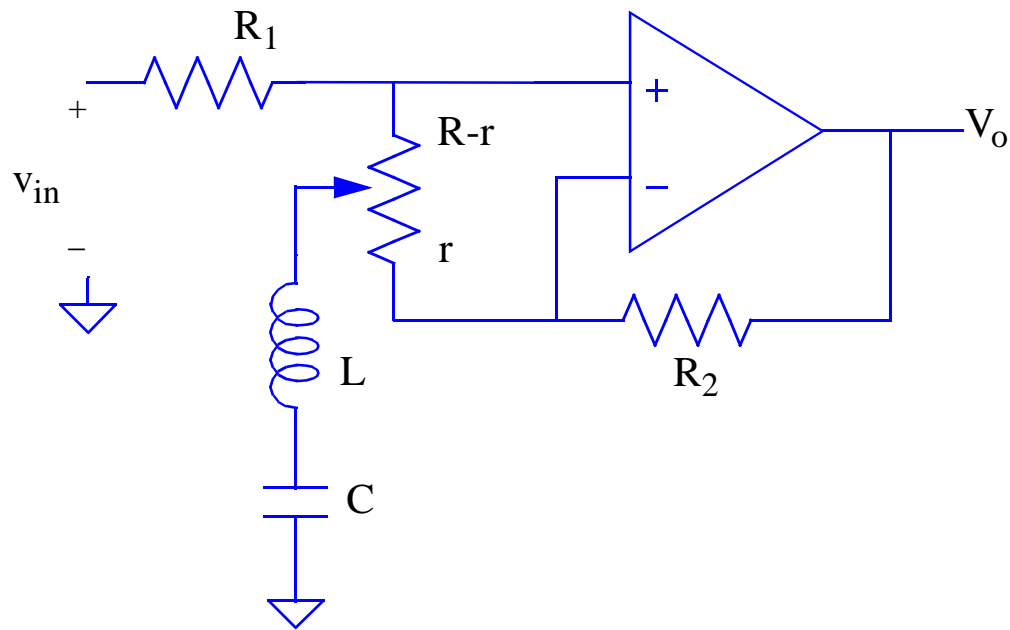
## Combination Notch and Bandpass Filter


- Clever filter design for graphic equalizer can perform both notch and bandpass functions
- Gain or attenuation is controlled by a potentiometer for specific frequency bands





## Combination Notch and Bandpass Filter





## Combination Notch and Bandpass Filter

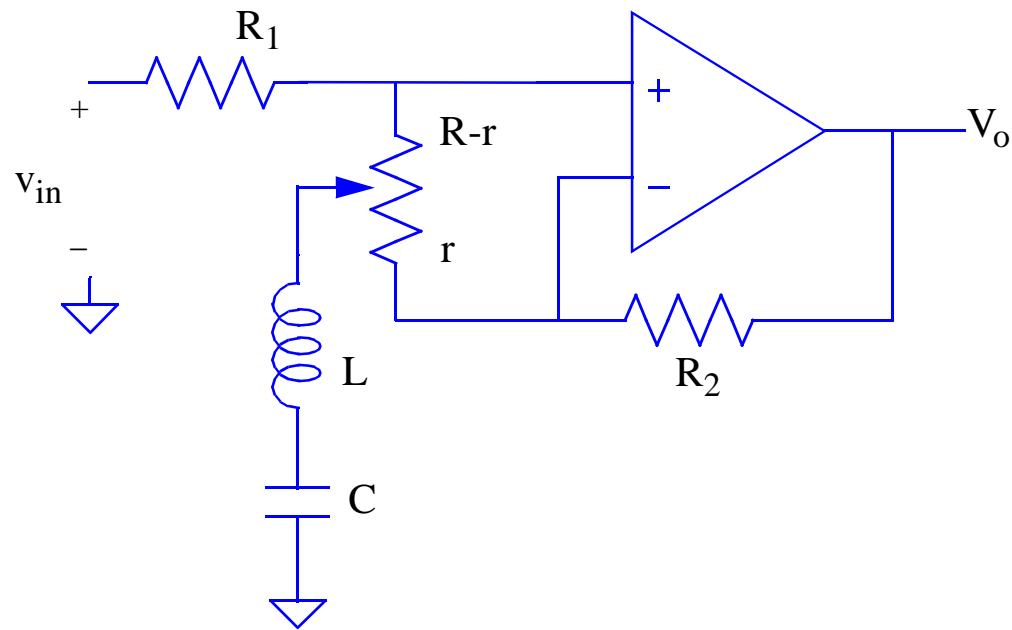

# Combination Notch and Bandpass Filter

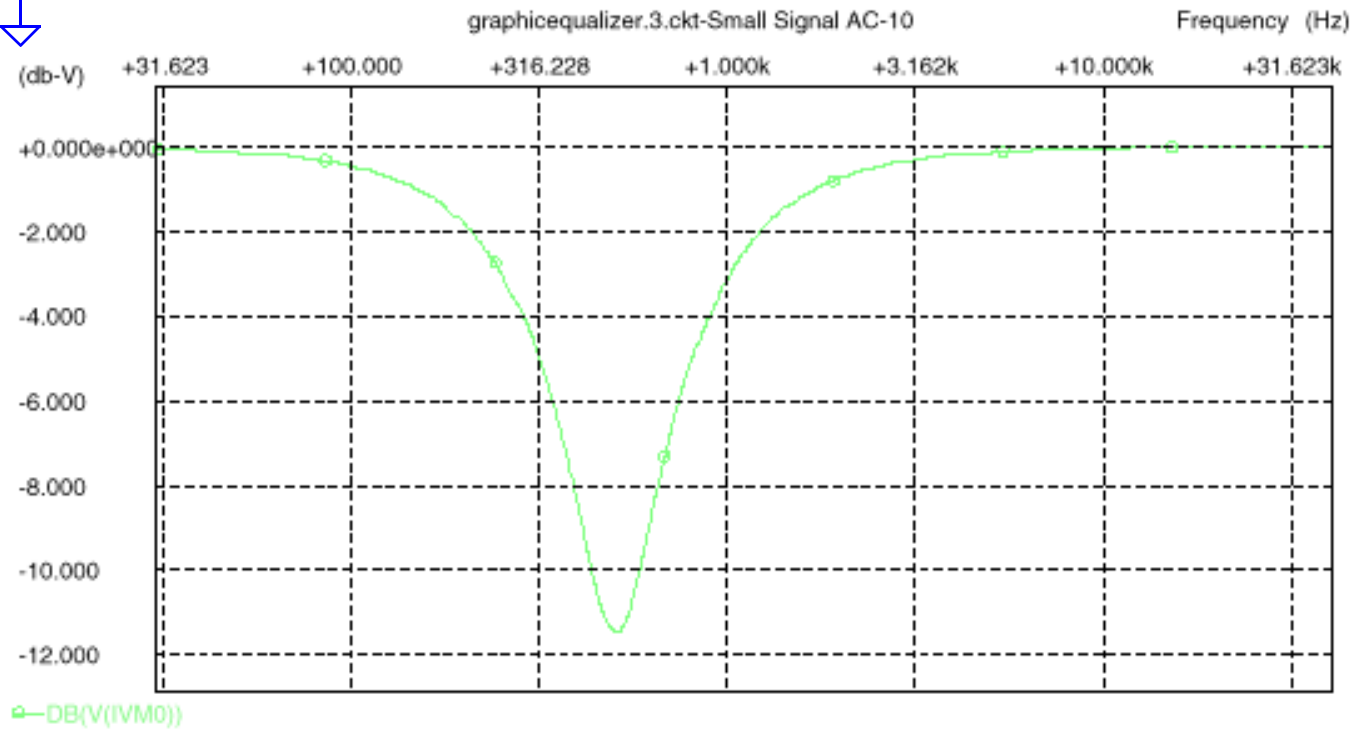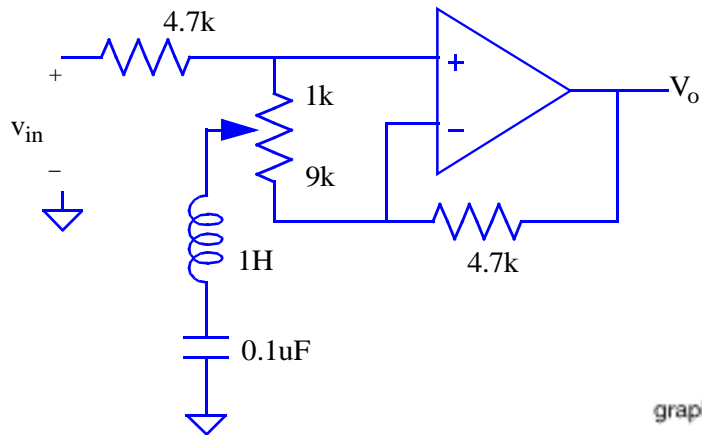


# Combination Notch and Bandpass Filter

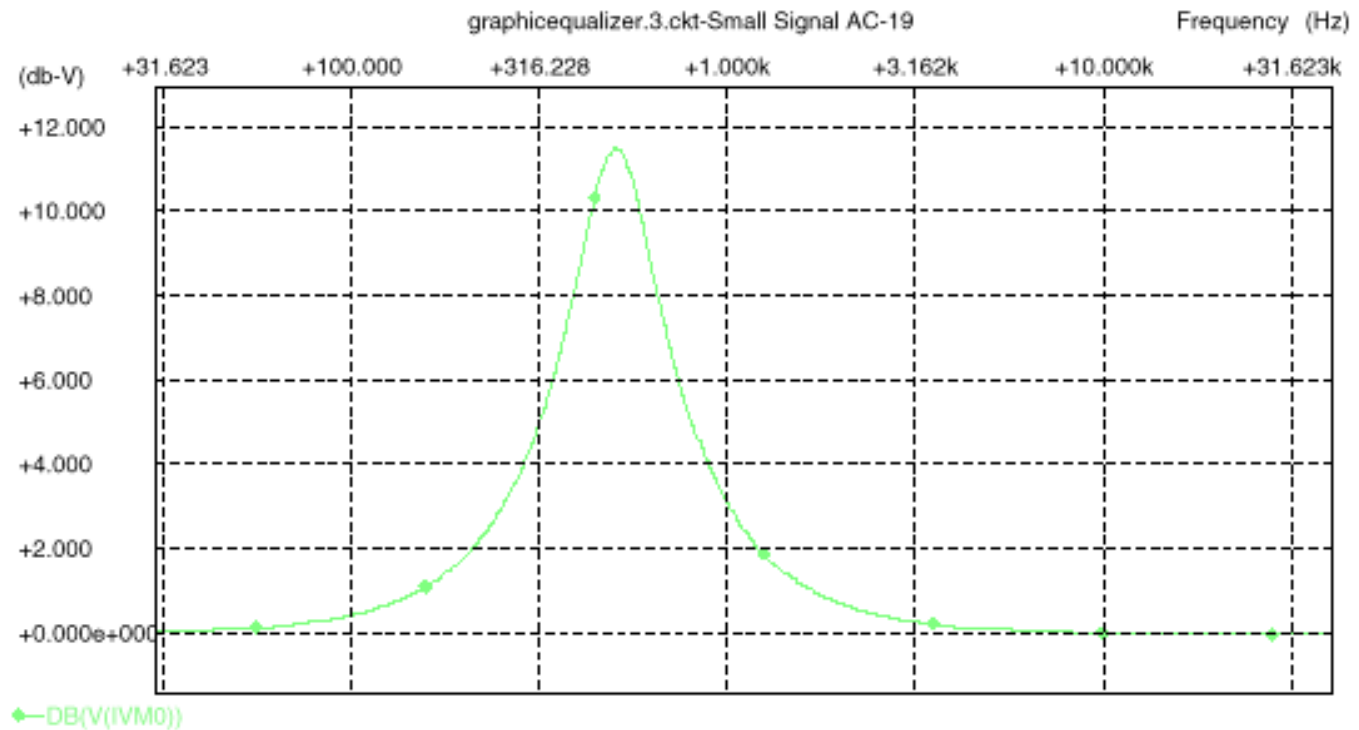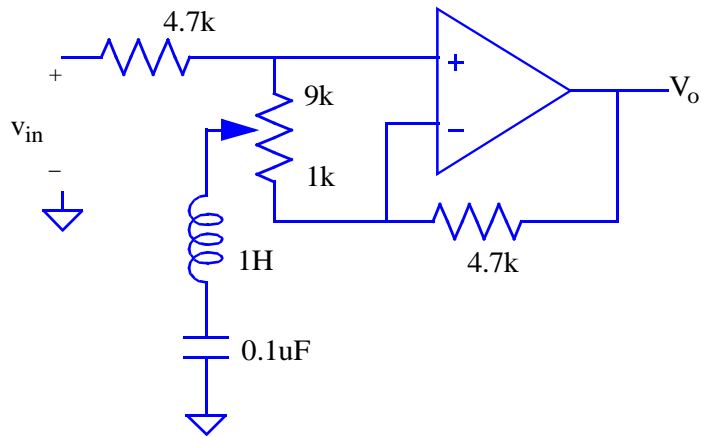
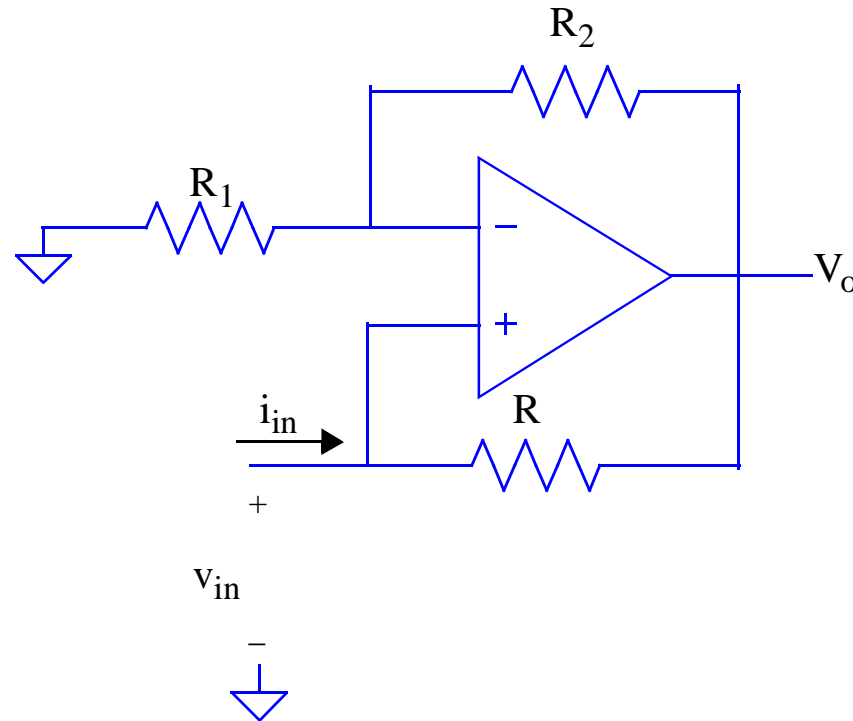
# Integrator via Negative Impedance Converter



- Presents a **negative resistance** at the input terminals
- Best analyzed by applying a test voltage and measuring the input current






- If it is behaving like a linear circuit, we can calculate the Thevenin equivalent
- If it's **passive**, we can simply calculate its impedance (resistance in this case)
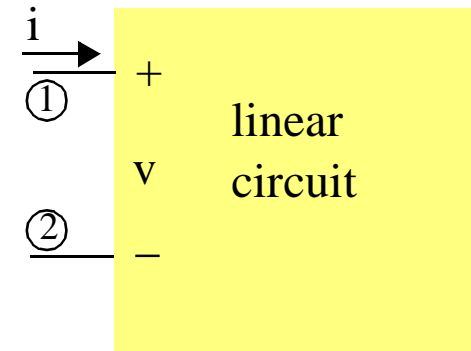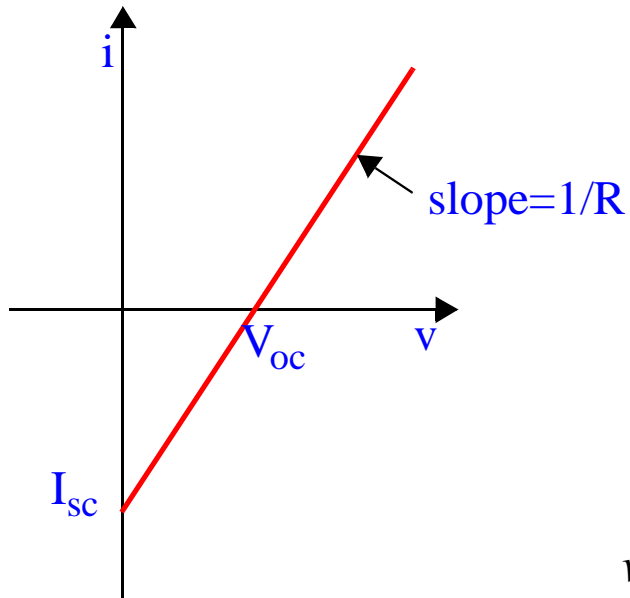
# Thevenin/Norton Equivalents

- By definition, a **linear** circuit has a straight-line i-v characteristic




Which can be represented by

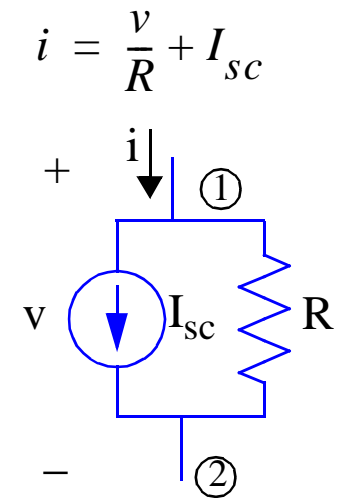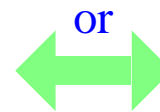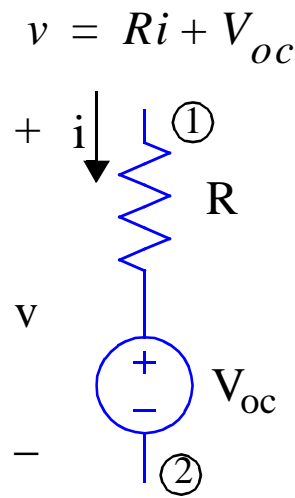

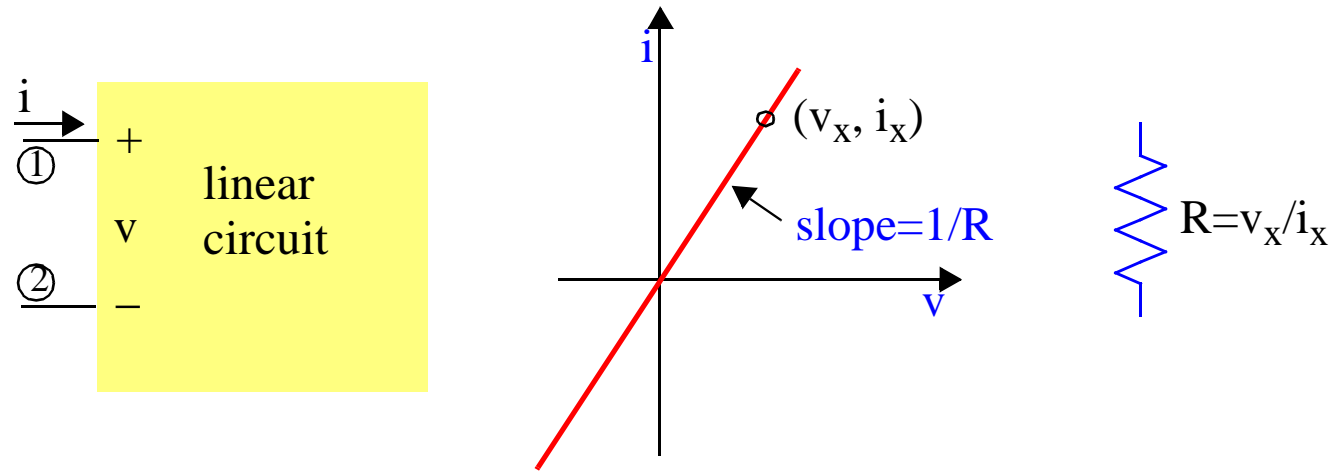
## Thevenin/Norton Equivalents

- If the line passes through the origin, then it is a **passive** linear circuit --- a single impedance
- Only one  $(v_x, i_x)$  point is needed to determine the slope



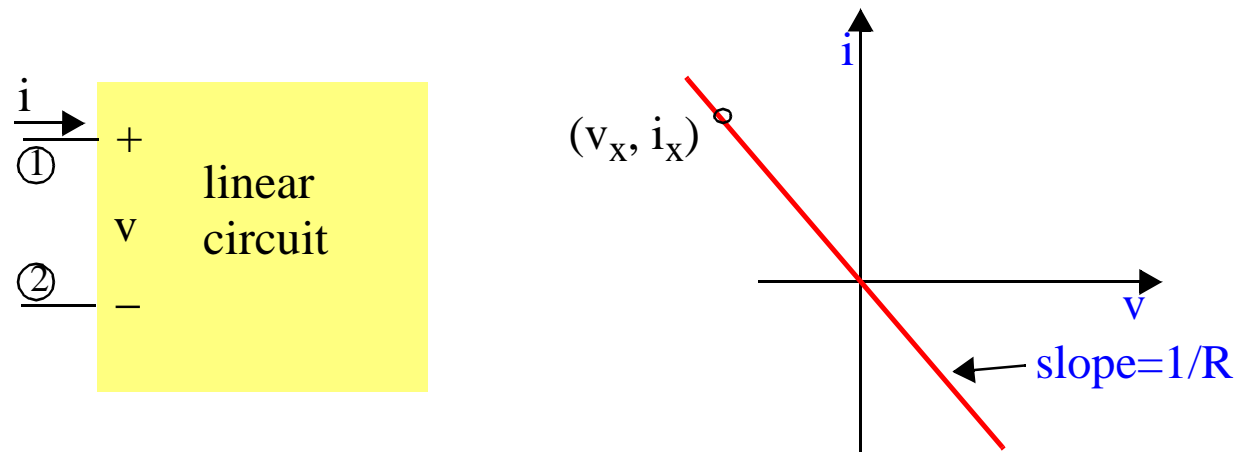
- A negative resistance is recognized by a negative slope (*with directions shown*)




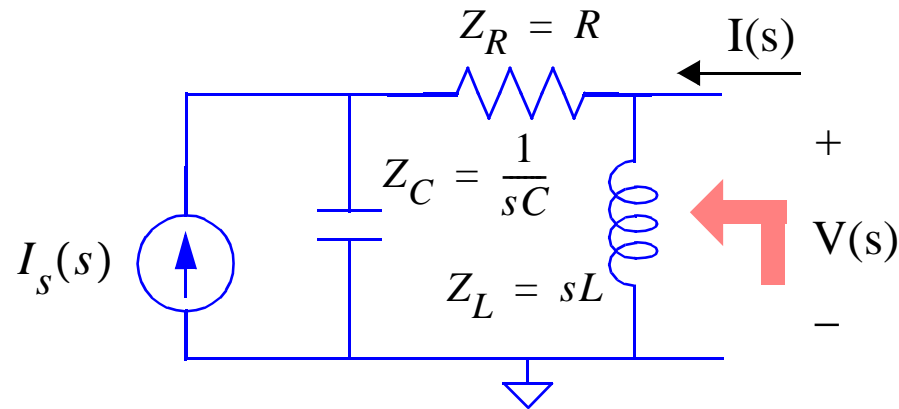
## Thevenin/Norton Equivalents


- Note that the same Thevenin/Norton conversion steps --- applying test voltages and measuring test currents --- works for complex impedances too




- We just can't draw them as two dimensional i-v characteristics

# Negative Impedance Converter

- Calculate  $v_{in}/i_{in}$

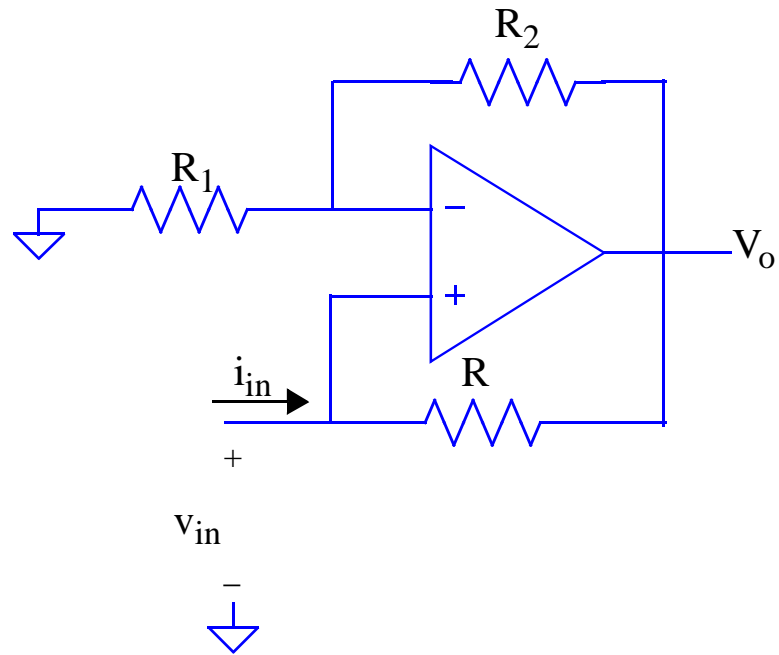


# Negative Impedance Converter

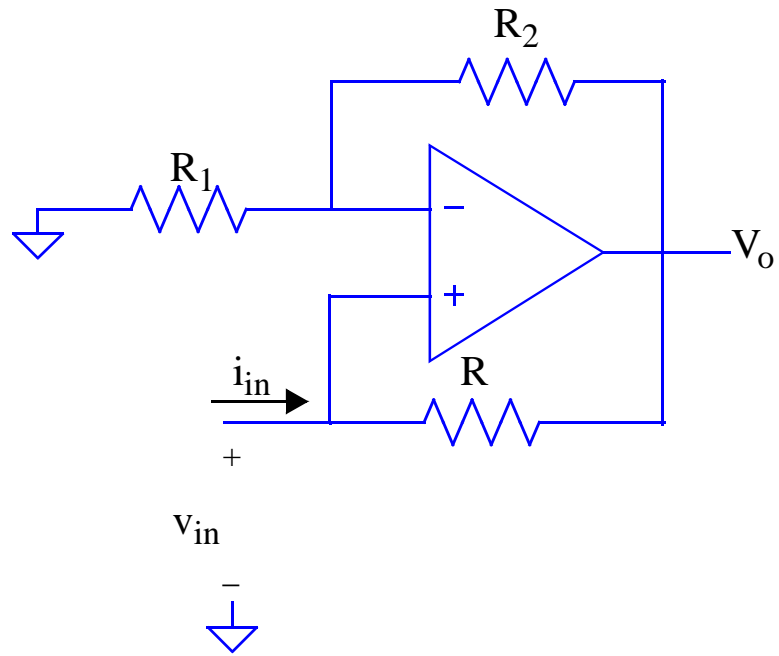

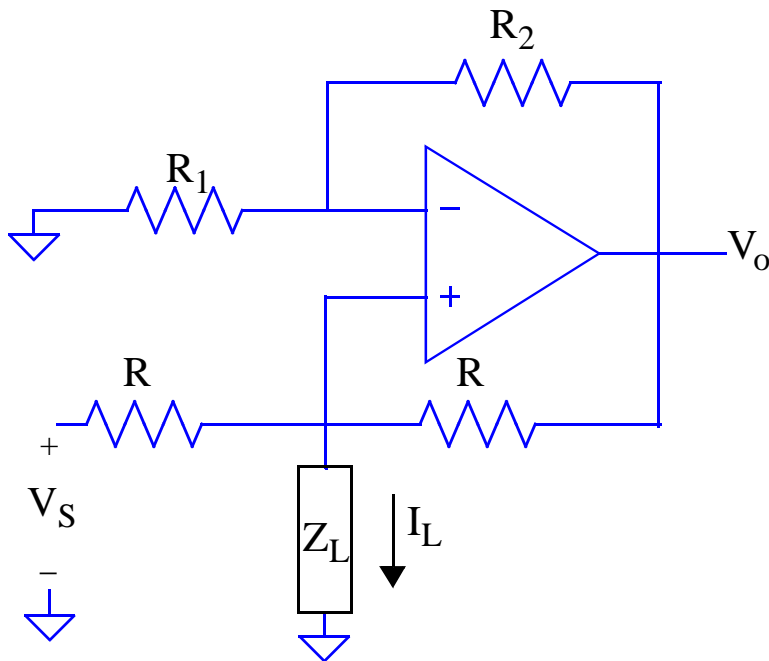
## Voltage-to-Current Converter

- The negative impedance converter can be used to create a voltage-to-current converter where the output load current is independent of the load impedance




## Voltage-to-Current Converter

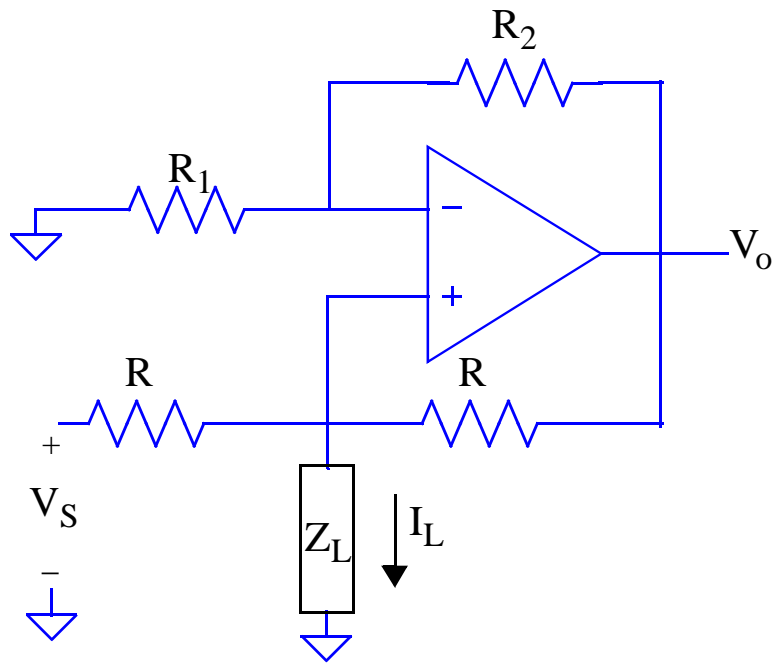

- We could also write out all of the current equations and get the same result

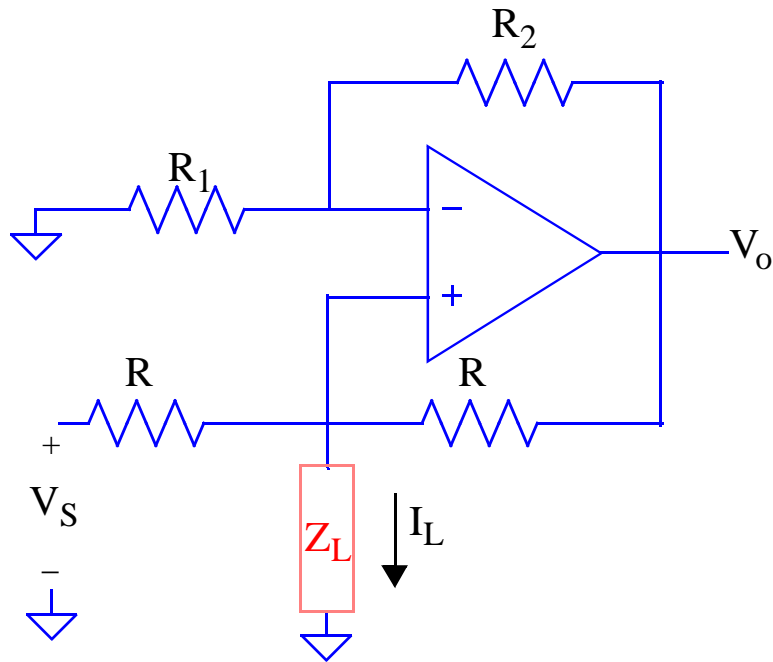
# Integrator

- Use the voltage-to-current converter to design an integrator


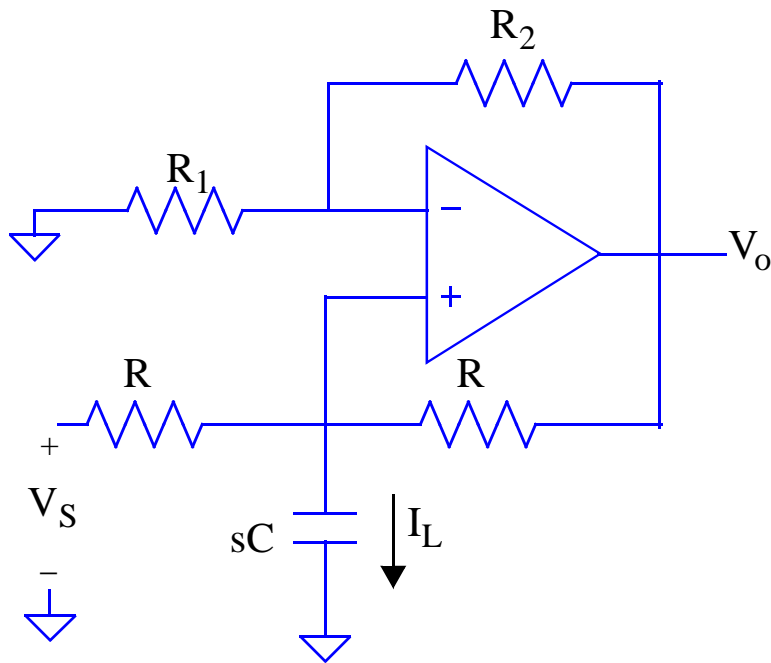
# Integrator

- Need a low output impedance for this circuit -- why?
- If the output impedance is not low enough, what is another design option?




## More Nonidealities

- Along with the frequency dependence of the gain, and the finite output/input impedances of the devices, there are other nonidealities associated with opamps that can cause distortion
- **Saturation**: the output is really limited to a voltage that is 1 to 3 volts less than VCC
- **Slew Rate**: limited gain of transconductance input amplifier can cause severe distortion in the output
- **CMRR**: the signal component that is common to both differential inputs is amplified somewhat, and the CMRR specifies the quality with which this phenomenon is rejected
- **dc Offset Voltage**: the input differential voltage required to set the output to zero when no other signals are applied
- **Finite Input/Output Impedances**: the input resistance/impedance of the inputs and the limited current sourcing capability of the output
- **dc Input Bias Current**: small currents required to bias the transistors at the input stage of the opamp



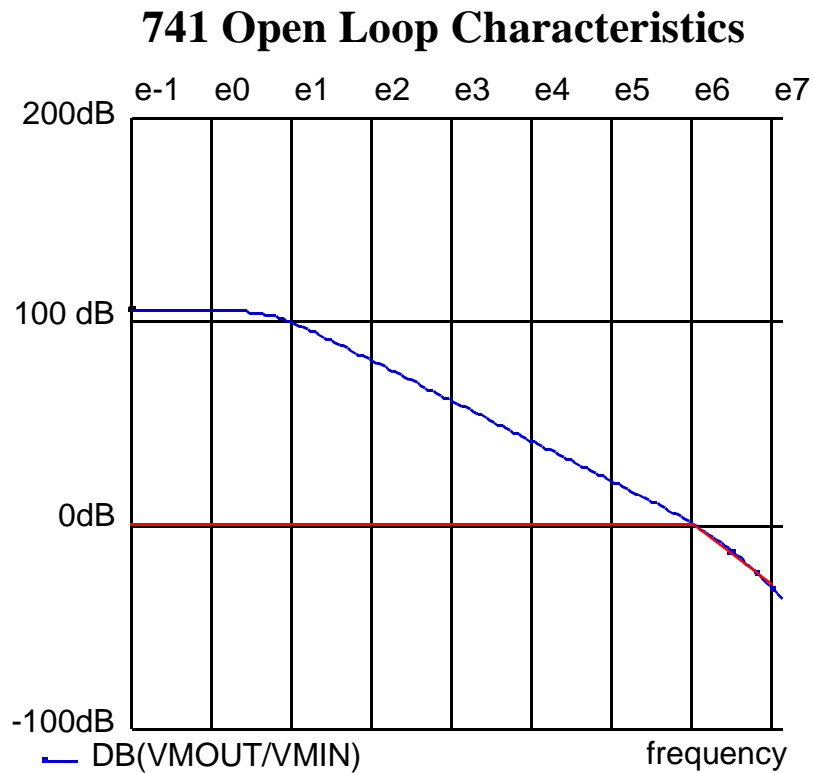
# Slew Rate Limitations

- We know that an opamp behaves like a low pass filter due to the frequency dependence of the gain
- A unity gain amplifier has a bandwidth of  $\omega_t$



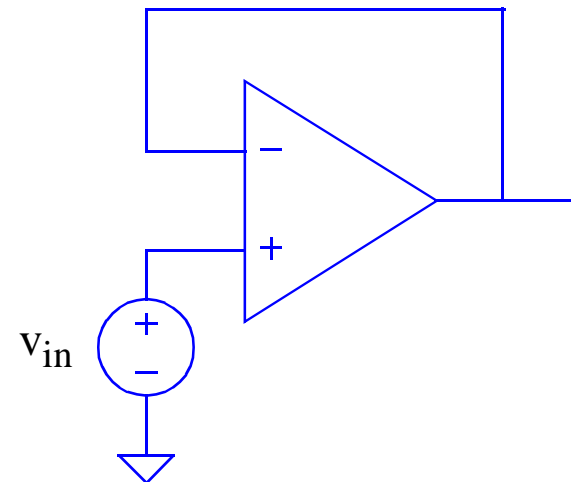
$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$


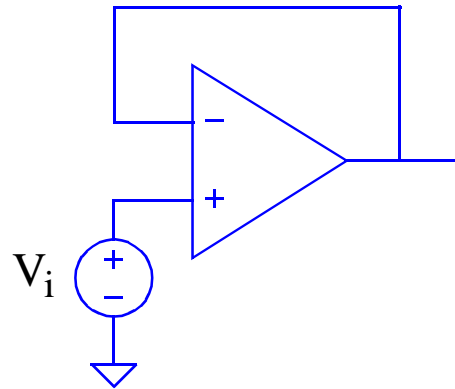
## Slew Rate Limitations

- So we can write an expression for the closed-loop gain as:



$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{s}{\omega_t}}$$

- Which is like a STC with a time constant of  $\frac{1}{\omega_t}$
- In the time domain we'd expect a step response of the form:

$$v_o(t) = V \left( 1 - e^{-\frac{t}{\tau}} \right)$$

- Which has a **maximum possible change** in output voltage of

$$\frac{dv_o(t)}{dt} = \frac{V}{\tau}$$

## Slew Rate Limitations

- If the output wants to change faster than this, it will not be able to do so
- This is especially difficult for large signals; e.g. when  $V$  is large
- The maximum switching speed is limited by  $\omega_t$ , which is due to the compensation capacitor in this case, but all capacitors in the circuit in general
- The open loop roll-off with frequency is due to the limited current sourcing capability of the amplifier and these capacitors

$$\frac{\Delta V}{\Delta t} \Rightarrow \frac{I_{max}}{C}$$


- So the maximum current sourcing capability and the compensation capacitor, for example, may determine the **slew rate**

$$SR = \left. \frac{dV_o}{dt} \right|_{max} \quad (\text{volts}/\mu\text{s})$$

- A smaller change in voltage can go to higher frequencies before encountering the SR limitation
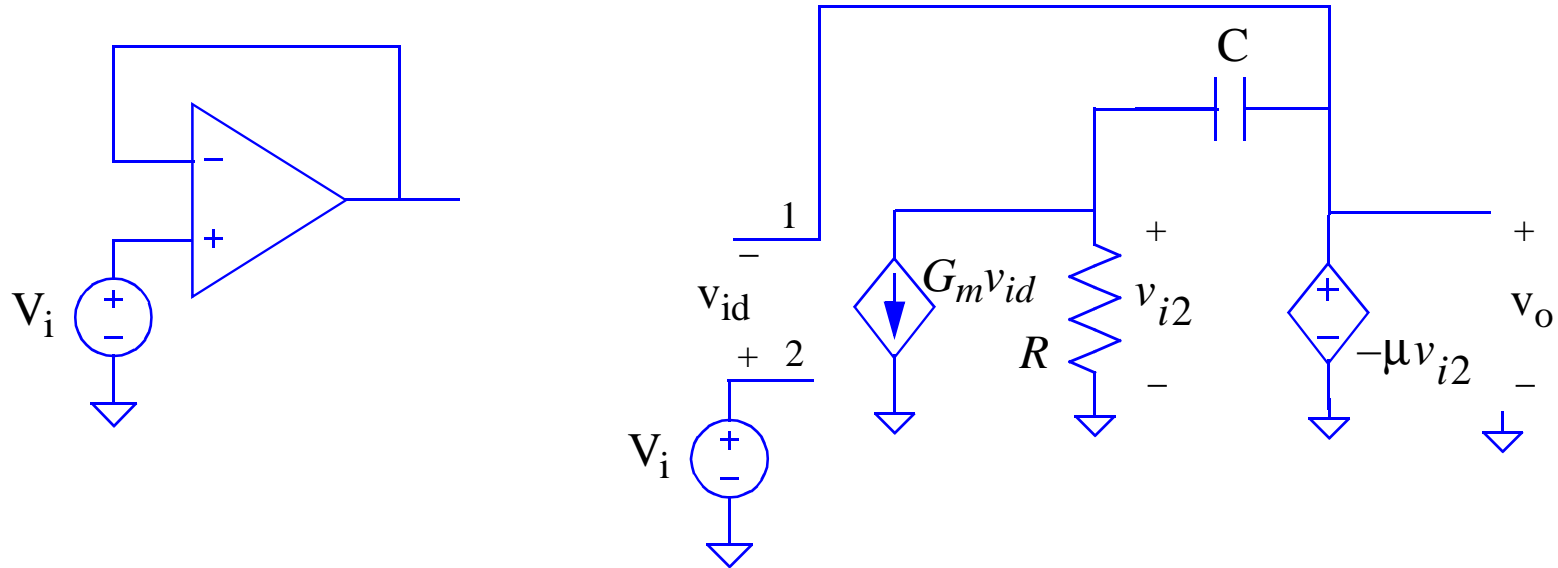
# Opamp Macromodels


- We can look at this limited current sourcing capability of the opamp in terms of the opamp macromodel




- When change in  $v_{id}$  is sudden,  $G_m$  can only supply a limited amount of current,  $I_{max}$  for a real input transconductance amplifier
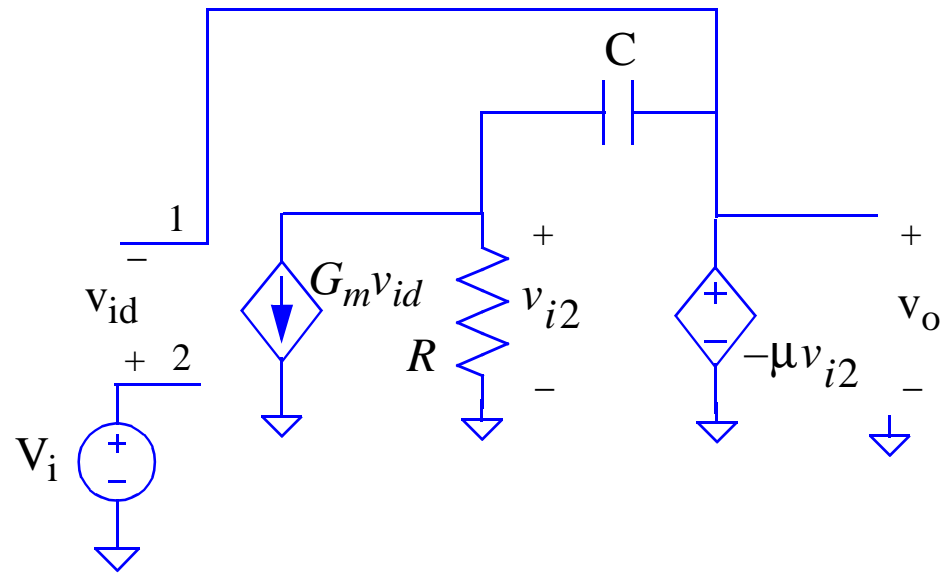
## Slew Rate Limited Response

- At the slew rate limit the output can only ramp up with a slope of  $I_{\max}/C(1+\mu)$



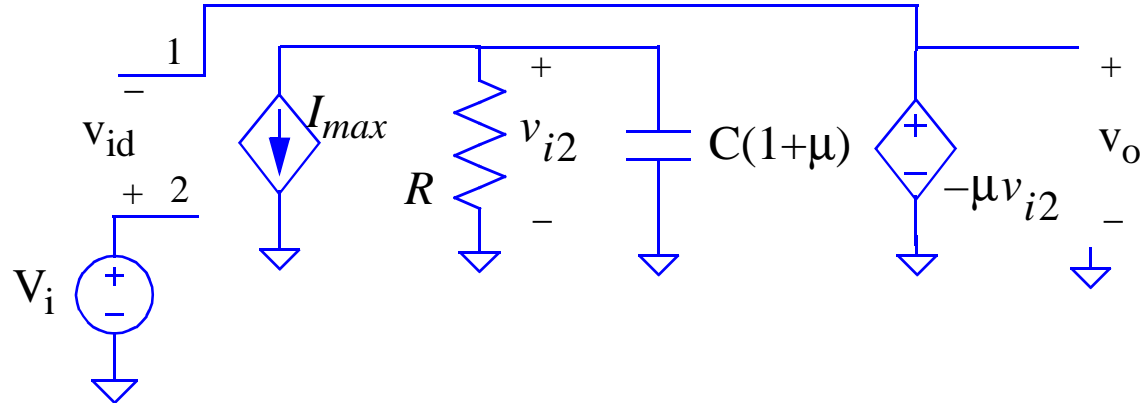For a sudden change in the input voltage,  $V_{id}$




## 741 Example

- Slew Rate for a 741 is  $0.63\text{V}/\mu\text{s}$
- For a sinusoidal signal, the maximum change occurs near the zero crossing, so this is where we will notice the first signs of slewing


$$\left. \frac{dV_o}{dt} \right|_{max} = \omega V$$

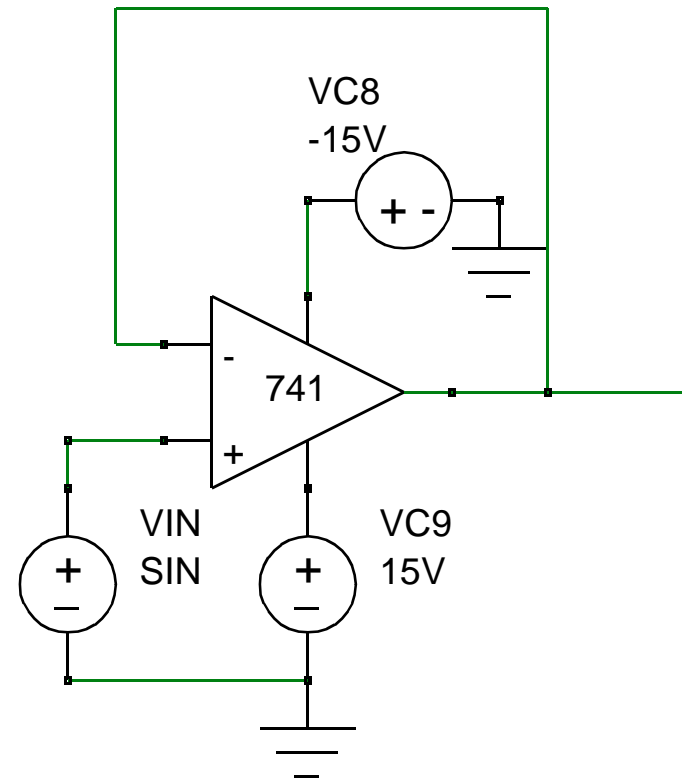- What's the maximum allowable frequency for a peak sinusoidal input voltage of 5.0 volts?



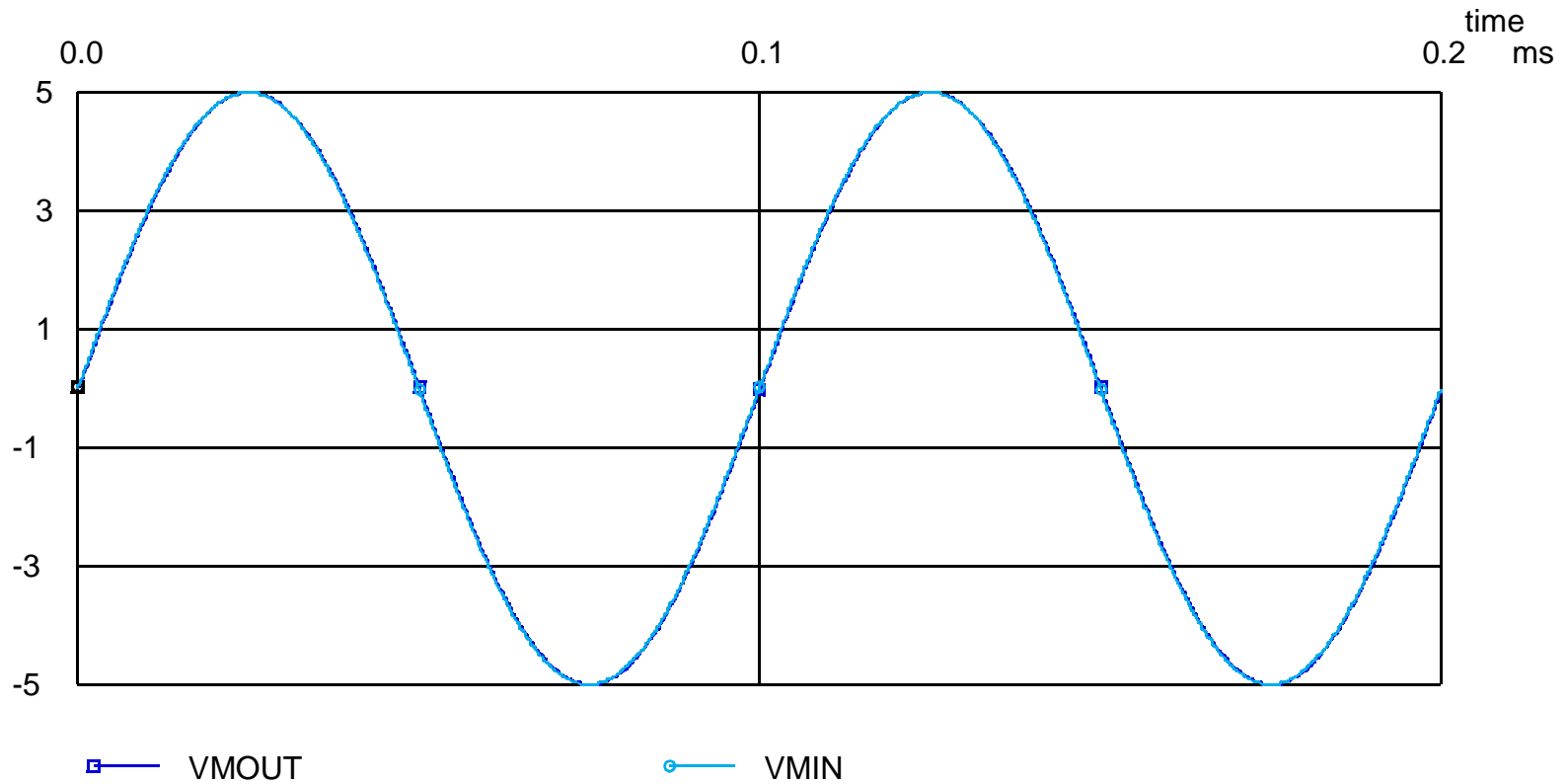
# 741 Example

- Input and output voltage for a 5 volt peak, 10kHz frequency


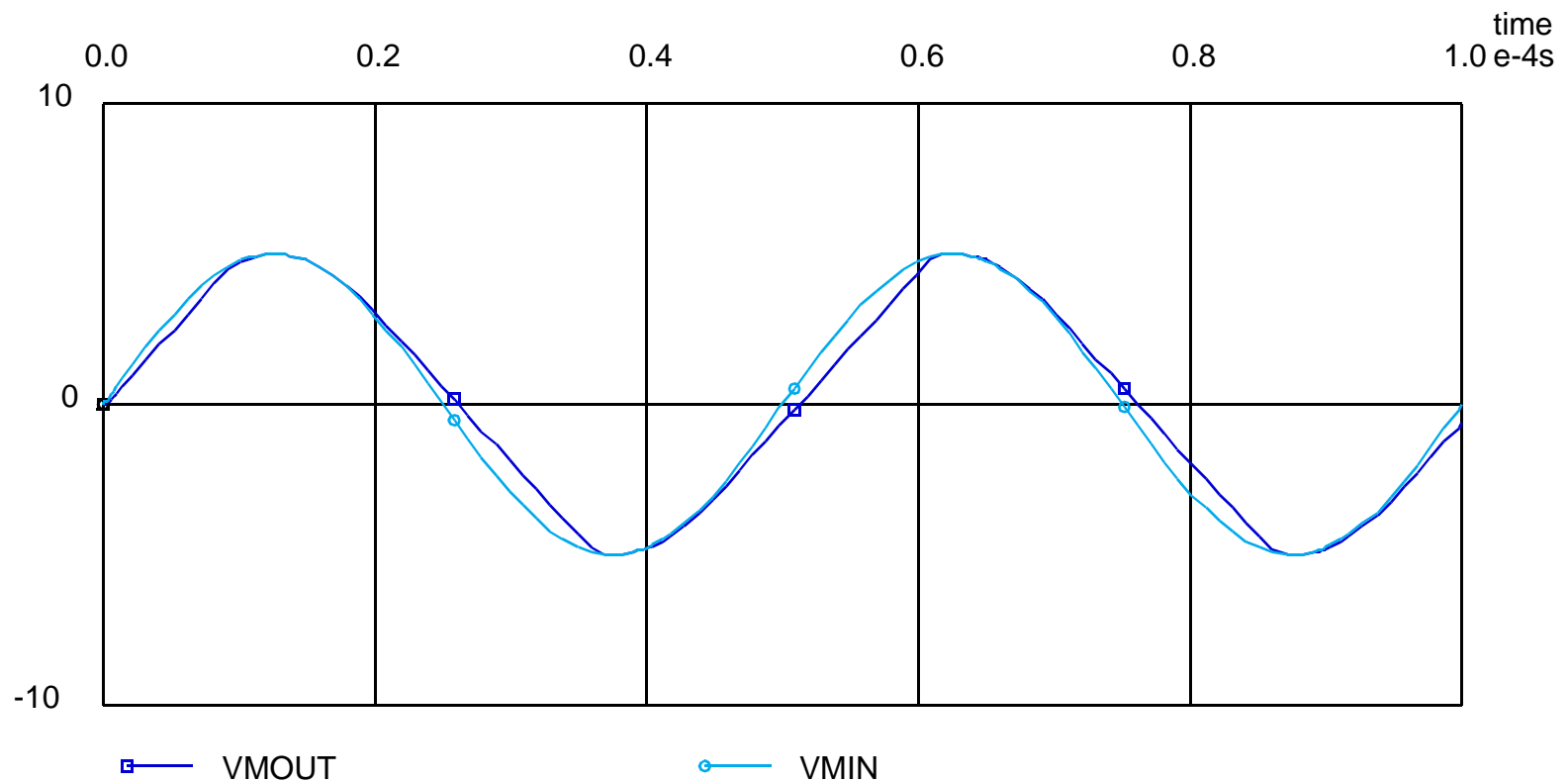
# 741 Example


- Input and output voltage for a 5 volt peak, 20kHz frequency




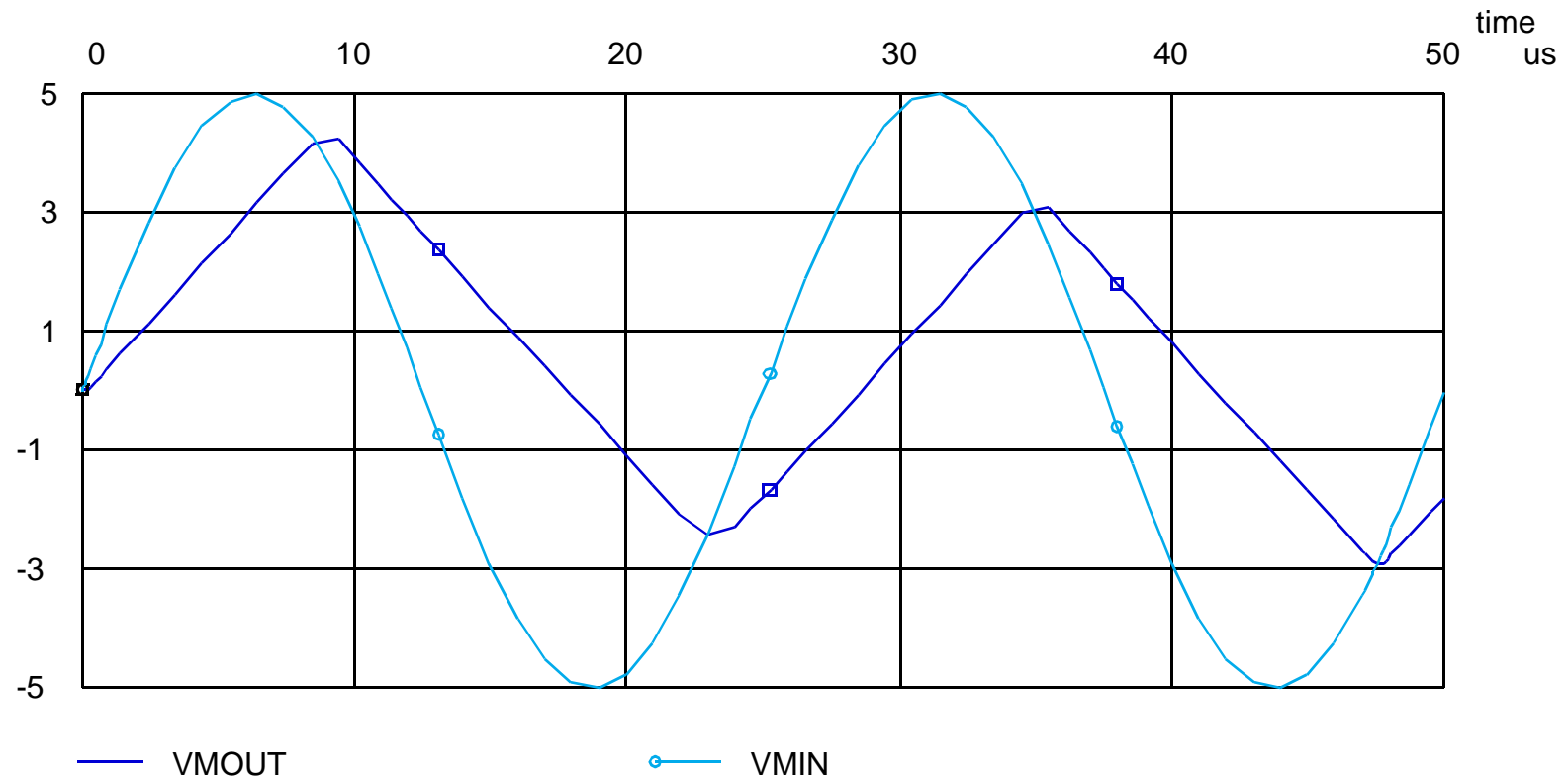
# 741 Example

- Input and output voltage for a 5 volt peak, 40kHz frequency



## 741 Example

- Note that the frequency response of the opamp does not affect the input signal at 20kHz
- It is a slew rate limitation that depends on the magnitude of the input voltage (has  $I_{\max}$  of the input transconductance amplifier been reached?)

