

# 18-447 Lecture 2: Computer Arithmetic: Adders

James C. Hoe  
Dept of ECE, CMU  
January 14, 2009

Announcements: No class on Monday  
Verilog Refresher next Wednesday  
Review P&H Ch 3

Handouts: Lab 1 and HW1 will be posted on Blackboard this weekend

# Binary Number Representation

- ◆ Let  $b_{n-1}b_{n-2}...b_2b_1b_0$  represent an n-bit **unsigned** integer

- its value is  $\sum_{i=0}^{n-1} \underbrace{2^i}_{\text{weight of the } i\text{'th digit}} \underbrace{b_i}_{\text{value of the } i\text{'th digit}}$

- a finite representation between 0 and  $2^n-1$

- e.g.,  $1011_{\text{two}} = 8_{\text{ten}} + 2_{\text{ten}} + 1_{\text{ten}} = 11_{\text{ten}}$

(more commonly rewritten as  $b'1011=11$ )

- ◆ Often written in Hex for easier human consumption

- to convert, starting from the LSB, map 4 binary digits at a time into a corresponding hex digit; and vice versa

- e.g.,  $1010\_1011_{\text{two}} = AB_{\text{hex}}$

For converting between binary and decimal, memorize decimal values of  $2^0 \sim 2^{10}$ , and remember  $2^{10}$  is about 1000.

# 2's-Complement Number Representation

- ◆ Let  $b_{n-1}b_{n-2}...b_2b_1b_0$  represent an n-bit **signed** integer

- its value is

$$-2^{n-1}b_{n-1} + \sum_{i=0}^{n-2} 2^i b_i$$

- a finite representation between  $-2^{n-1}$  and  $2^{n-1} - 1$
- e.g., assume 4-bit 2's-complement

$$b'1011 = -8 + 2 + 1 = -5$$

$$b'1111 = -8 + 4 + 2 + 1 = -1$$

- ◆ To negate a 2's-complement number

- add 1 to the **bit-wise complement**
- assume 4-bit 2's-complement


$$(- b'1011) = b'0100 + 1 = b'0101 = 5$$

$$(- b'0101) = b'1010 + 1 = b'1011 = -5$$

$$(- b'1111) = b'0000 + 1 = b'0001 = 1$$

$$(- b'0000) = b'1111 + 1 = b'0000 = 0$$

# Intuition: a 4-bit example

 

- ◆ how to add two numbers
- ◆ what it means to "overflow" the number representation
- ◆ how to negate a number

Yes, 0 is a positive number in CS

# Smaller to Larger Binary Representation

## ◆ Unsigned numbers

- pad the left with as many 0s as you need (aka 0-extension)  
e.g.  $4'b1111 \rightarrow 8'b0000\_1111$


## ◆ 2's-complement numbers

- positive: pad the left with as many 0s as you need
- negative: pad the left with as many 1s as you need  
e.g.  $4b'1111 \rightarrow 8'b1111\_1111$   
 $4b'1110 \rightarrow 8'b1111\_1110$
- or generically, pad the left with the same value as the original sign-bit as many times as necessary (aka signed-extension)

What about converting from larger to smaller representation?


# (Unsigned) Binary Addition

## ◆ Long Hand

 

What about subtraction?

# Full Adder

 

$c_{in}$	$a$	$b$	$c_{out}$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = bc_{in} + ac_{in} + ab$$

3-way parity  
majority

$a, b, c_{in}$  are functionally indistinguishable as inputs


# Unsigned Binary Addition

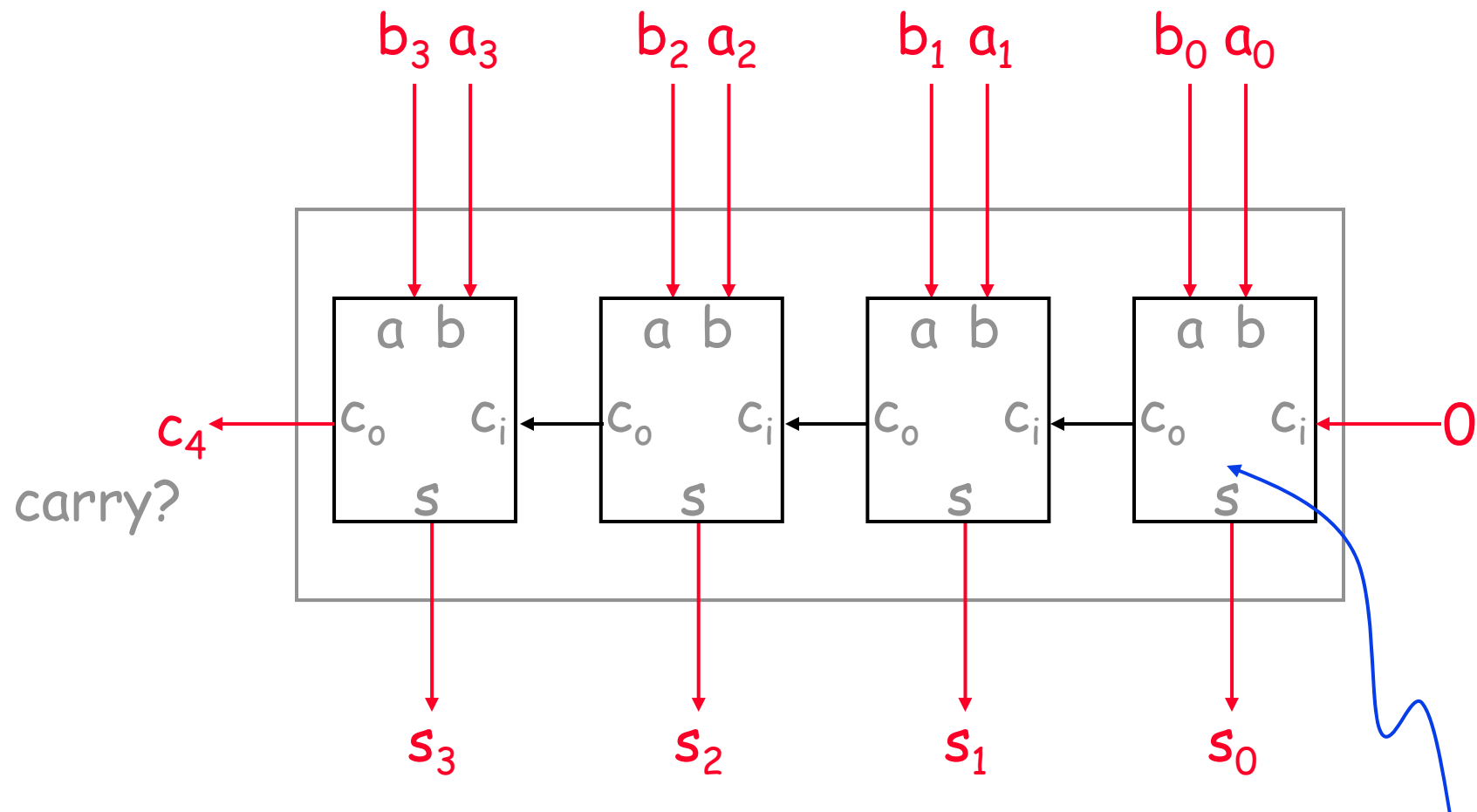

Could use a "half-adder", but let's wait



# 2's-Complement Addition

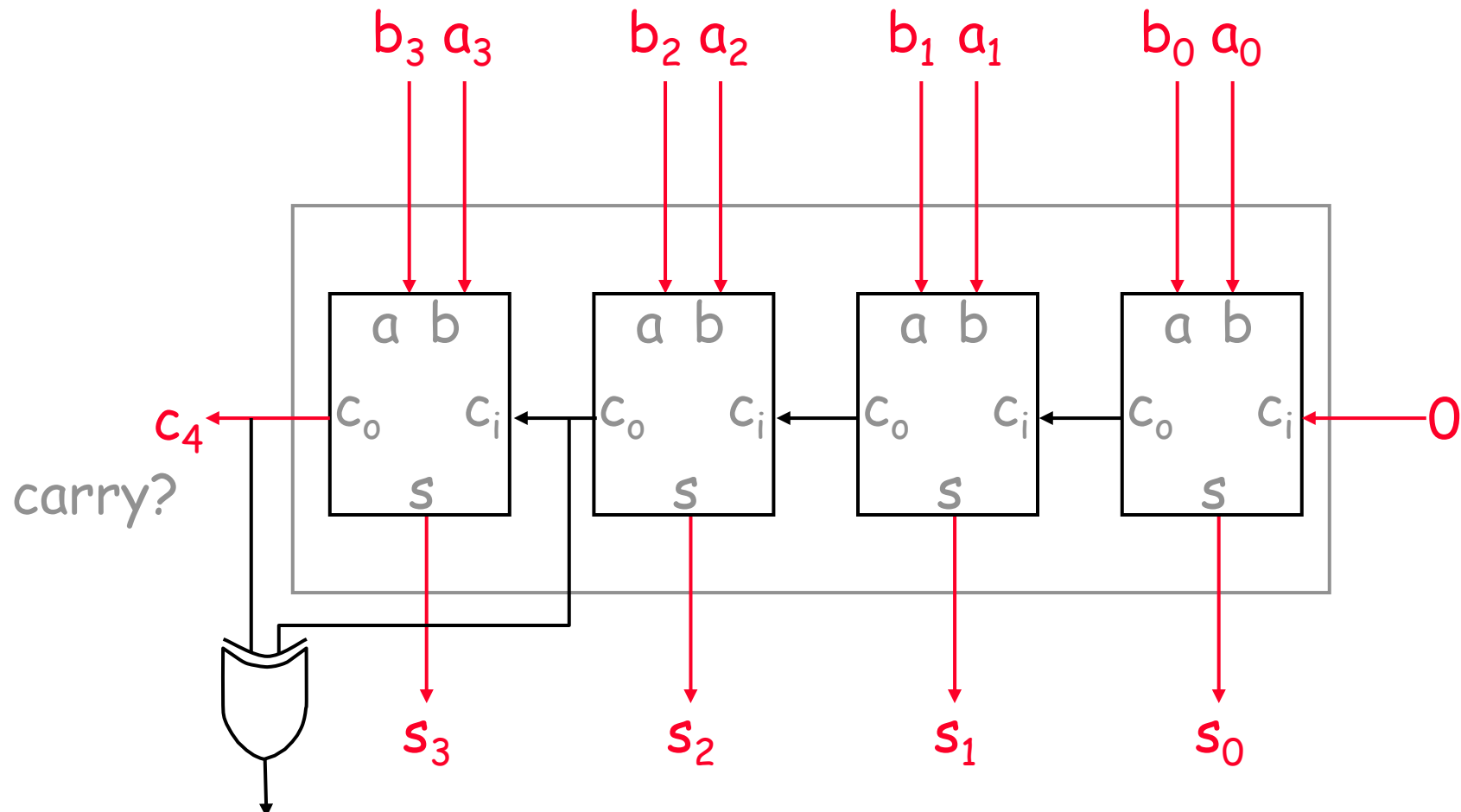


$$\text{overflow?} = (a_3 \oplus b_3) ? 0 : (a_3 \oplus s_3)$$

- can't overflow when adding a pos. and a neg. number
- if 2 pos. numbers yield a neg. number  $\Rightarrow V$ ; vice
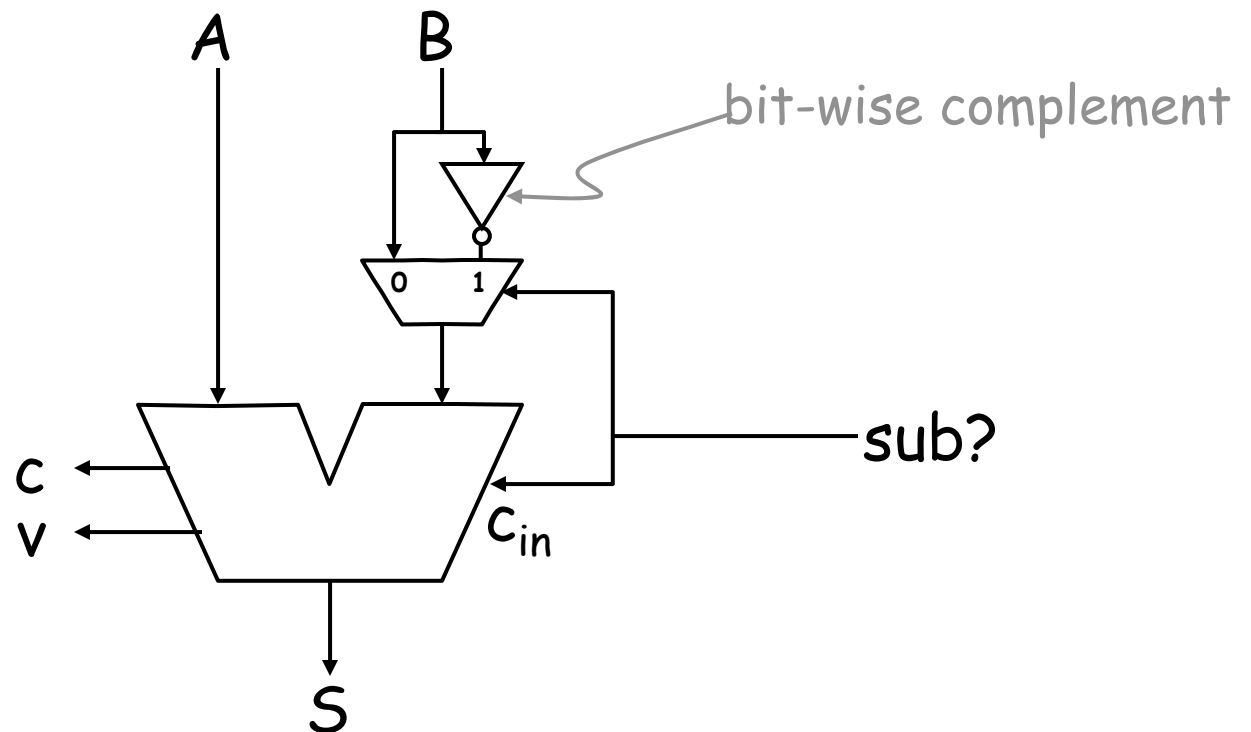
# 2's-Complement Subtraction


- ◆ Subtracting is like adding the negative
- ◆ Negation is easy in a 2's-complement representation




How do you build a comparator (i.e.,  $>$ ,  $<$ )?
 
# Analysis of an n-bit "Ripple-Carry" Adder

- ◆ Size/Complexity:  $O(n)$ 
  - $n \times \text{SizeOf}(\text{Full Adder})$
- ◆ Critical Path Delay:  $O(n)$ 
  - $n \times \text{DelayOf}(\text{Full Adder})$
  - $n \times 2$  gate delays (assuming 2-level SOP is used)



# 18-447 Simplified Timing

 

What about setup-time, hold-time, skew and such?

# High-Performance Adder?

- ◆ Intel P4 is designed around a clock period that is twice the 16-bit adder latency
- ◆ Using a rough estimation  
gate delay  $\approx 0.5$  ns-per-micron  $\times$  feature-size  
a 90nm process has gate delay = 45ps
- ◆ If Intel used a ripple-carry adder then P4 should be running  $\sim 1 / (2 \times 2 \times 16 \times 45\text{ps}) = 347\text{MHz}$
- ◆ Alternatively speaking, 3GHz P4 would have to add 2 16-bit numbers in  $\sim 4$  gate delays

# Cutting Down the Carry Chain

- ◆ How to reduce the **carry-propagation** delay?

Remember, long-hand is how most of us add,  
but not the only way

- ◆ Can we compute an intermediate carry signal without first computing the earlier ones

- e.g., let  $c_m$  (or  $s_m$ ) be a function of  $a_m \dots a_0$  and  $b_m \dots b_0$


$$c_2 = (a_1 a_0 b_0) + (a_1 a_0 c_0) + (a_1 b_0 c_0) + (b_1 a_0 b_0) + (b_1 a_0 c_0) \\ + (b_1 b_0 c_0) + (a_1 b_1)$$

- Complexity grows exponentially in  $n$

exponential isn't too bad for small  $n$ 's


- gate delay is 2, independent of  $n$

true for small  $n$ 's

 

What about large  $n$ 's?


# Carry-Select Adder

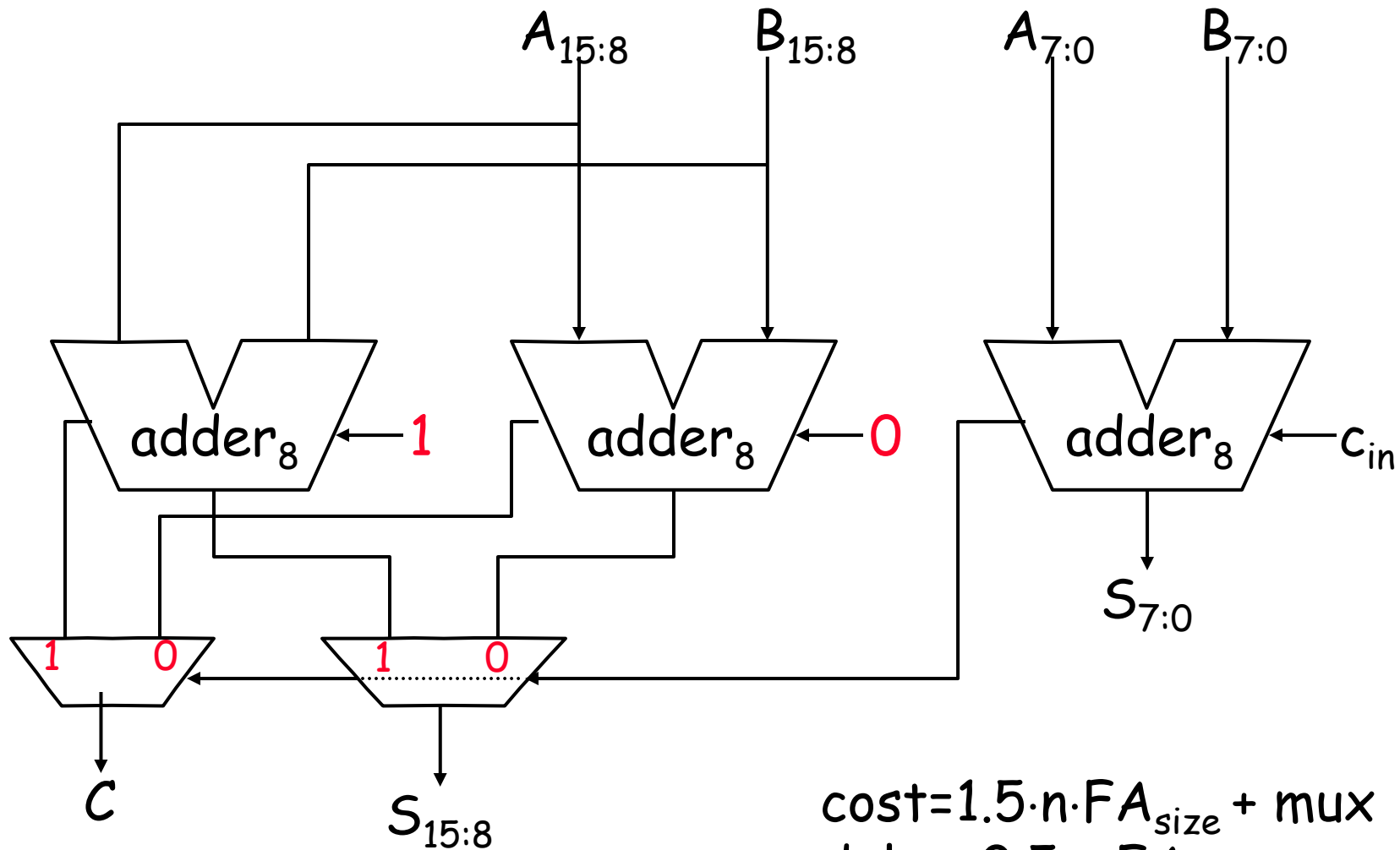

$$\begin{aligned} \text{cost} &= 1.5 \cdot n \cdot FA_{\text{size}} + \text{mux} \\ \text{delay} &= 0.5 \cdot n \cdot FA_{\text{delay}} + \text{mux-delay} \\ \text{if } n=16 &\Rightarrow \sim 16 \text{ gate-delays} \end{aligned}$$

3 adders operate in parallel!!

# Multi-Stage CSA

 

cost =  $(2k-1)/k \cdot n \cdot FA_{size} + \text{mux's}$  --- for k-stage

delay =  $n \cdot FA_{delay} / k + (k-1) \cdot \text{mux-delay}$


k=4, n=16  $\Rightarrow$  ~8 gate-delay + 3 mux-delay

k=8, n=16  $\Rightarrow$  ~4 gate-delay + 7 mux-delay

k=16, n=16  $\Rightarrow$  ~2 gate-delay + 15 mux-delay



# Variable-Length CSA

 

- doubles the cost
- delay set by the longest adder stage, grows by  $O(n^{1/2})$  with careful critical path tuning

Can we have cut-down the carries without 2x cost?

# Carry Generate and Propagate

$c_{in}$	$a$	$b$	$c_{out}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



$c_{in}$	$a$	$b$	$c_{out}$
X	0	0	0
$c_{in}$	0	1	$c_{in}$
$c_{in}$	1	0	$c_{in}$
X	1	1	1

- ◆ If  $a \cdot b$  then  $c_{out}$  is 1 regardless of  $c_{in}$  (carry generate)
- ◆ if  $a \oplus b$  then  $c_{out}$  is the same as  $c_{in}$  (carry propagate)

$$g_i = a_i \cdot b_i$$

$$p_i = a_i \oplus b_i$$

local decisions based on  $a_i$  and  $b_i$  only

# Small Carry-Look-Ahead Adder

Given  $g_i = a_i \cdot b_i$

$$p_i = a_i \oplus b_i$$

$$c_{i+1} = g_i + (p_i \cdot c_i)$$

Thus

$$c_1 = g_0 + (p_0 \cdot c_0)$$

$$c_2 = g_1 + (p_1 \cdot c_1) = g_1 + (p_1 \cdot (g_0 + (p_0 \cdot c_0))) = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$

$$c_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

$$c_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

and so on

- We can compute  $c_n$  in  $O(\log n)$  gate delay and  $O(n^2)$  size, only manageable for small  $n$
- Given  $c_n$  we can compute  $s_n$  for a constant additional delay

# Prefix Carry-Look-Ahead

Given

$$c_1 = g_0 + (p_0 \cdot c_0)$$

$$c_2 = g_1 + (p_1 \cdot c_1) = g_1 + (p_1 \cdot (g_0 + (p_0 \cdot c_0))) = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$


$$c_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

$$c_4 = \underbrace{g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0}_G + \underbrace{p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0}_P$$


As a 4-arity group

$$G_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$$
 
$$P_4 = p_3 \cdot p_2 \cdot p_1 \cdot p_0$$




# Prefix Carry-Look-Ahead

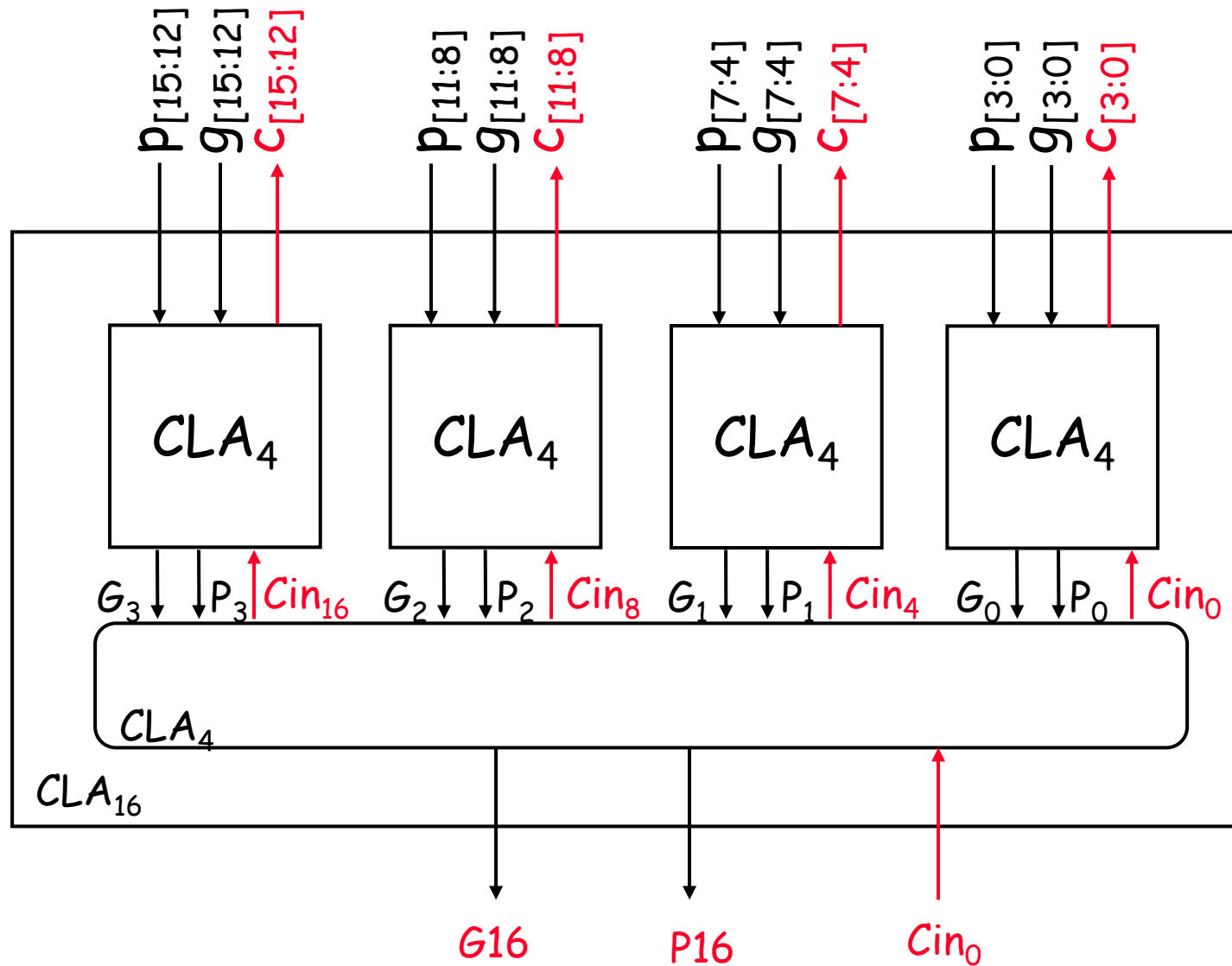

This structure can be recursed:  $O(\log n)$  delay,  $O(n)$  size

# Computing Individual Carries

Example: 8-bit, 2-ary CLA

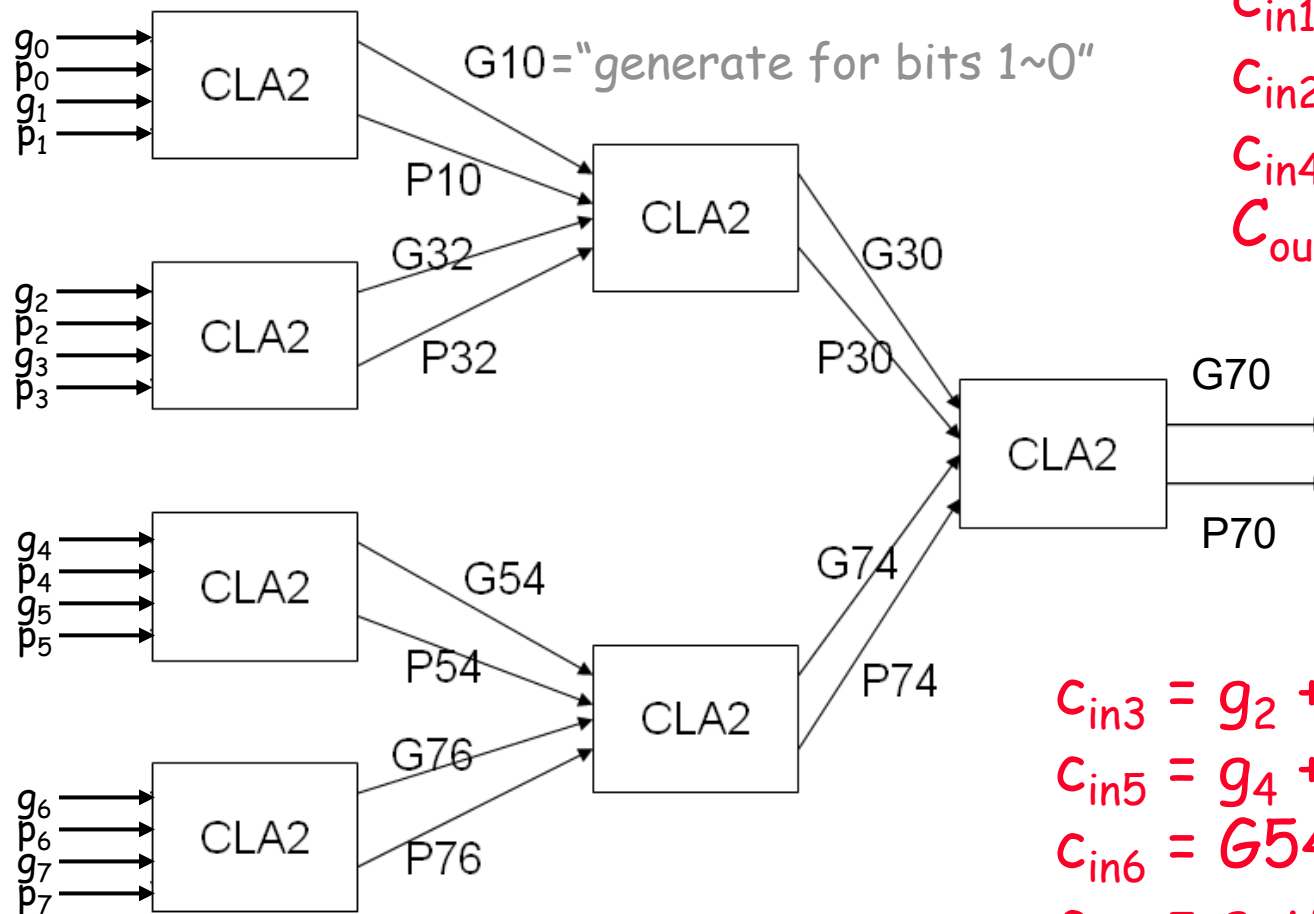

$$C_{in0} = C_{in}$$

$$C_{in1} = g_0 + p_0 \cdot C_{in}$$

$$C_{in2} = G_{10} + P_{10} \cdot C_{in}$$

$$C_{in4} = G_{30} + P_{30} \cdot C_{in}$$

$$C_{out} = G_{70} + P_{70} \cdot C_{in}$$


$$C_{in3} = g_2 + p_2 \cdot C_{in2}$$

$$C_{in5} = g_4 + p_4 \cdot C_{in4}$$

$$C_{in6} = G_{54} + P_{54} \cdot C_{in4}$$

$$C_{in7} = g_6 + p_6 (G_{54} + P_{54} \cdot C_{in4})$$

# Large Adder using Carry-Skip

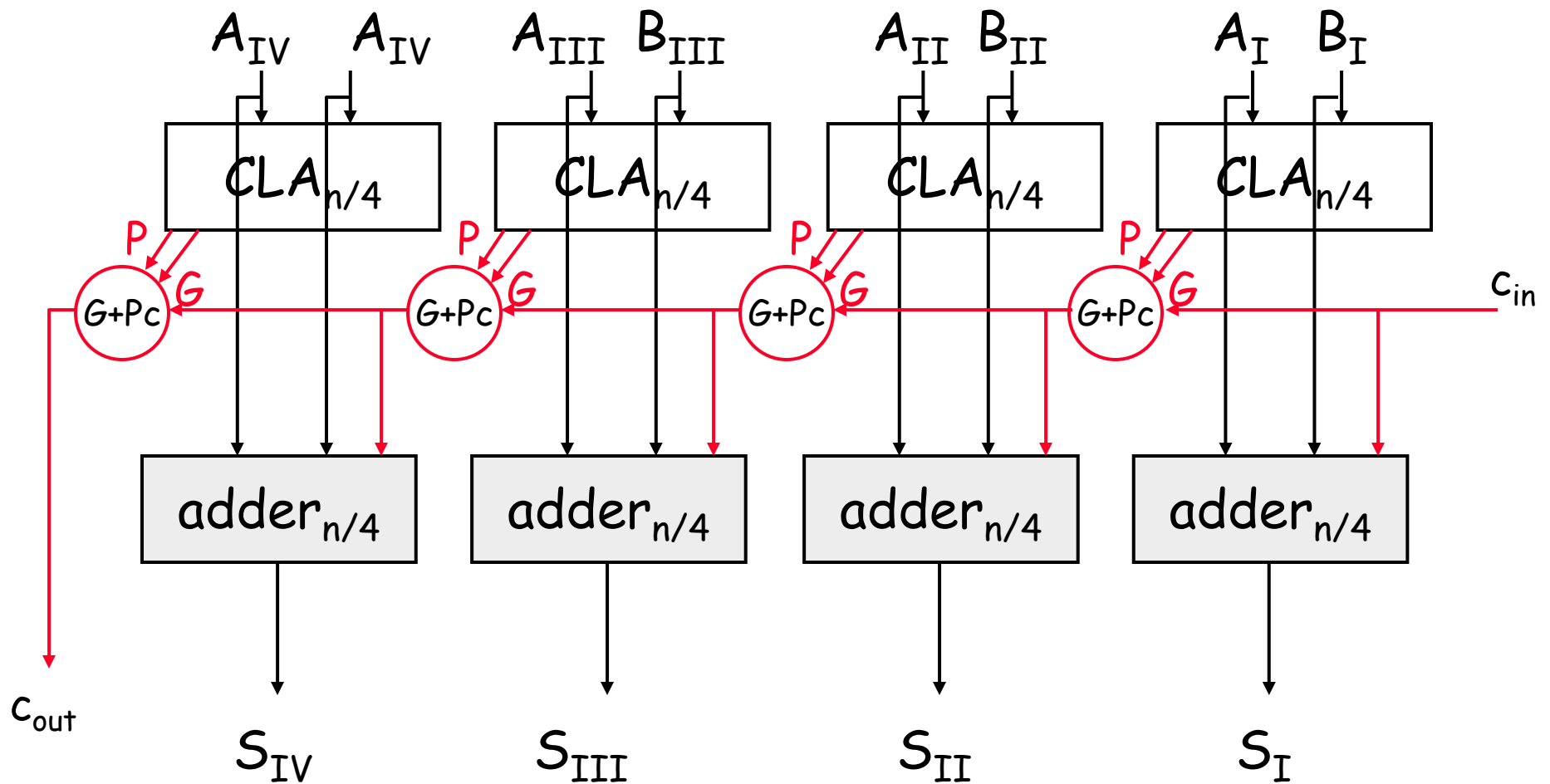

Fast enough and cheaper than computing individual  $c_i$ 's by  $G.P$ .

# Adder at a Glance

- ◆ Ripple Adder
  - $O(n)$  size,  $O(n)$  delay
- ◆ Carry-Select Adder
  - $O(n)$  size,  $O(n^{0.5})$  delay
- ◆ Carry-Look-Ahead Adder
  - $O(n^2)$  size,  $O(\log n)$  delay
- ◆ Prefix Adder
  - $O(n)$  size,  $O(\log n)$  delay
- ◆ But, remember all approaches have design sweet-spots and make different tradeoffs
- ◆ There also are circuit-level adder tricks  
(e.g., Manchester carry chain)




# Black Magic of Adder Design

- ◆ High-performance adder designs are extremely important to high-performance computing
- ◆ Studied extensively in theoretical frameworks
- ◆ Worked on extensively in practice
- ◆ Nevertheless remain very much a trial-and-error design exercise
- ◆ For a 64-bit adder, one might construct
  - adders of various (short) length using 2-level logic
  - a 16-bit adder from small adders with variable-length carry-select
  - a 32-bit adder from 2 16-bit CSA with CLA to determine carry for the upper 16 bits
  - a 64-bit 2-stage CSA adder from 3 32-bit adders


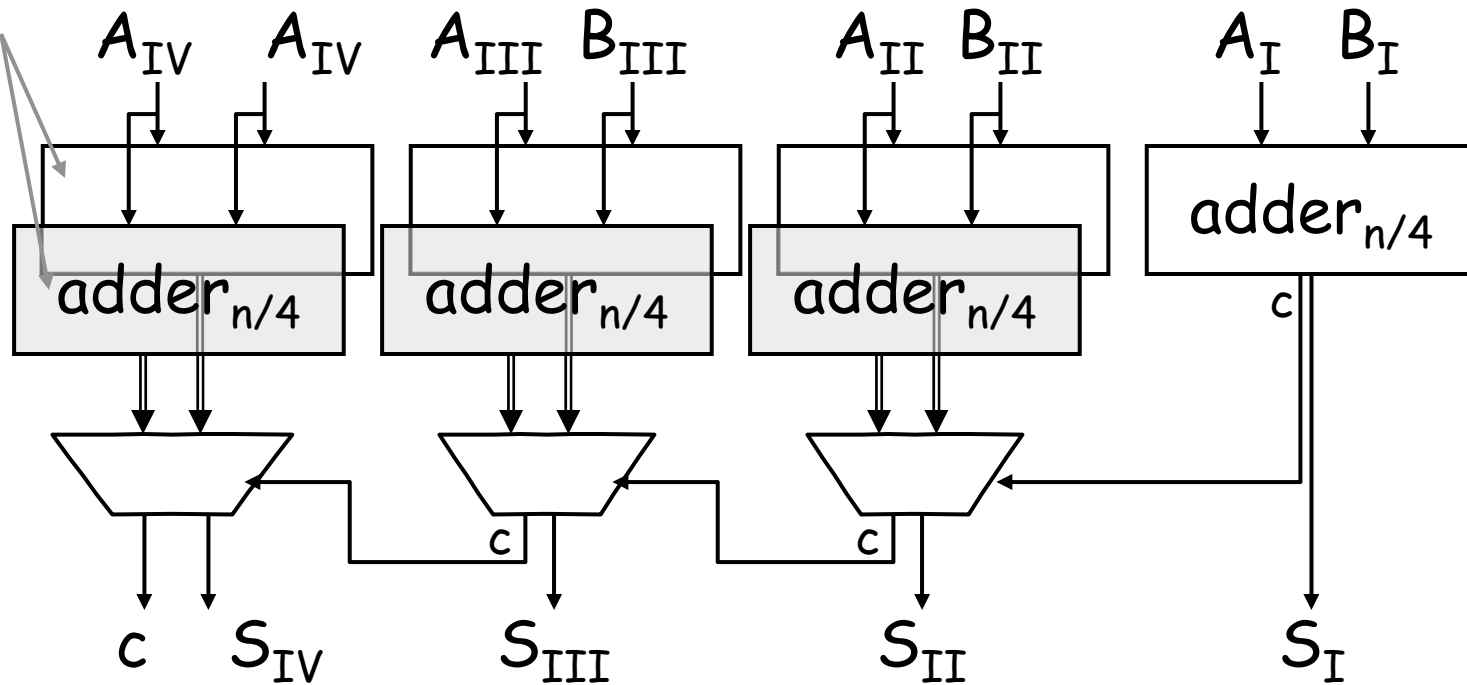
# Building Wide Adders: the CSA approach

The fastest  
sub-adder  
you can  
muster



$$\text{cost} = (2k-1) \cdot \text{SizeOf}(\text{sub-adder}) + \text{mux's}$$

$$\text{delay} = \text{DelayOf}(\text{sub-adder}) + (k-1) \cdot \text{mux-delay}$$

- CSA pays  $\sim 2\times$  the cost to avoid the carry delay
- Is there a cheap way to compute carry fast?