
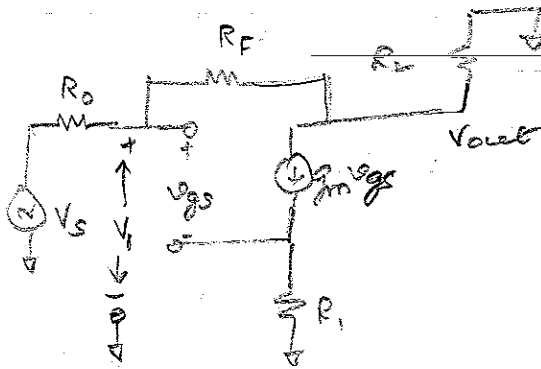


General wideband amplifier techniques:


- 1) Cascade of single-pole amplifiers (with or w/o)
- 2) Bandwidth enhancement techniques (shunt peaking, series peaking, T-coil etc.)
- 3) Regeneration (positive feedback)
- 4) Distributed amplifiers.

Shunt-series Amplifier

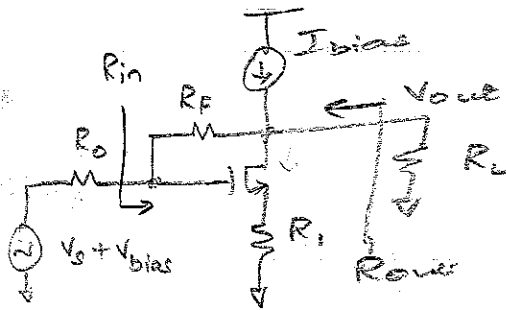

- Use feedback to obtain accurate input & output impedances & gain
- Gain accuracy over PVT variations
- R_F gives shunt feedback (takes a fraction of the output current which feeds back and subtracts from input current)
- R_i gives series feedback (senses output current, converts it to voltage and subtracts this feedback voltage from the input voltage)

(a) Input resistance:

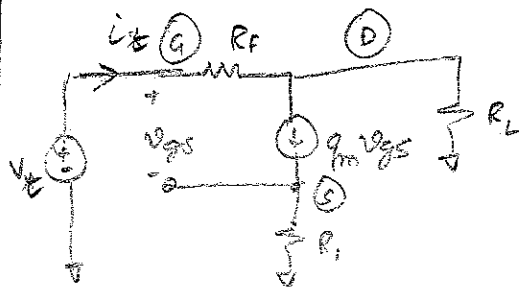


$$(1) V_i = V_{gs} + g_m V_{gs} R_i = (1 + g_m R_i) V_{gs}$$

(2) KCL at (D)

$$\Rightarrow i_i = g_m V_{gs} + \frac{V_o}{R_L}$$

$$= \frac{g_m V_i}{1 + g_m R_i} + \frac{V_i - i_i R_F}{R_L}$$

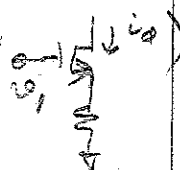
Define $G_m = \frac{g_m}{1 + g_m R_i}$ (effective transconductance of )

$$\therefore \left(1 + \frac{R_F}{R_L}\right) i_E = v_E \left[G_m + \frac{1}{R_L} \right]$$

Note:
When $g_m R_i \gg 1$, $G_m \approx \frac{1}{R_i}$

$$\Rightarrow R_{in} = \frac{R_L + R_F}{1 + G_m R_L} \approx \frac{R_L + R_F}{1 + R_L/R_i}$$

(b) Output resistance:

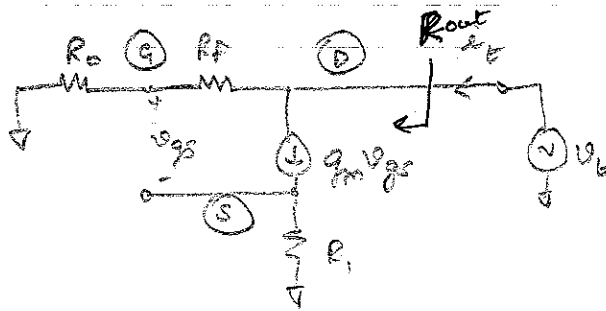

$$v_{gs} = v_G - v_S = \frac{R_o}{R_o + R_F} v_b - g_m v_{gs} R_i$$

$$\therefore v_{gs} = \frac{R_o}{R_o + R_F} \cdot \frac{1}{1 + g_m R_i} v_b$$

$$i_E = g_m v_{gs} + \frac{v_b}{R_o + R_F} = \left[\frac{g_m}{1 + g_m R_i} \cdot \frac{R_o}{R_o + R_F} + \frac{1}{R_o + R_F} \right] v_b$$


$$\Rightarrow R_{out} = \frac{v_b}{i_E} = \frac{R_o + R_F}{1 + G_m R_o} \approx \frac{R_o + R_F}{1 + R_o/R_i}$$

(c) Voltage gain:

First calculate $A_{V_i} = \frac{v_{out}}{v_i}$ and

then use the voltage divider rule to calculate

$$A_v = \frac{v_{out}}{v_i}$$

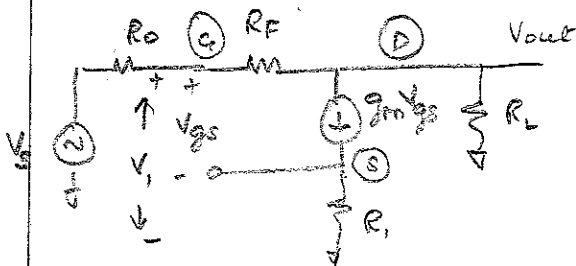

$$v_i = v_{gs} + g_m v_{gs} R_i \Rightarrow v_{gs} = \frac{v_i}{1 + g_m R_i}$$

KCL at (D): $g_m V_{gs} + \frac{V_{out}}{R_L} + \frac{V_{out} - V_1}{R_F} = 0$

$$\therefore \frac{g_m V_1}{1 + g_m R_1} - \frac{V_1}{R_F} = - \left(\frac{V_{out}}{R_L} + \frac{V_{out}}{R_F} \right)$$

$$\therefore (G_m - 1/R_F) V_1 = - \frac{V_{out}}{R_L \parallel R_F}$$

$$\text{or } \frac{V_{out}}{V_1} = A_{V_1} = - \frac{R_L \parallel R_F}{R_F} (G_m R_F - 1)$$

$$\Rightarrow \boxed{A_{V_1} = \frac{R_L}{R_L + R_F} (1 - G_m R_F)}$$

\Rightarrow usually choose $R_F \gg R_L$
 and $G_m R_F \gg 1$
 $\Rightarrow A_{V_1} \approx -G_m R_L$

Also, $V_{out} = V_s \cdot \frac{R_{in}}{R_{in} + R_o} \cdot A_{V_1}$ and $A_V = \frac{V_{out}}{V_s}$

$$\Rightarrow \boxed{A_V = \frac{R_{in}}{R_{in} + R_o} \cdot \frac{R_L}{R_L + R_F} (1 - G_m R_F)} \approx - \frac{R_{in}}{R_{in} + R_o} G_m R_L$$

(d) Bandwidth: Until now, we have neglected all capacitances. To calculate the BW, we will use the method of open-circuit time constants (OCT). Consider a network with only R 's, C 's, independent I or V sources and dependent sources (VCCS, VCVS etc.). The OCT technique consists of the following steps:

- (a) Calculate the effective resistance R_{j0} facing the j^{th} cap C_j with all other capacitors removed.
- (b) Find the time constant $\tau_{j0} = R_{j0} C_j$ for every capacitor
- (c) 3dB BW of the network = $\frac{1}{\sum \text{all such "open-circuit" time constants}}$

$$\Rightarrow \omega_{3dB, OCT} = \frac{1}{\sum_{j=1}^m R_{j0} C_j} \quad \text{for a total of } m \text{ capacitors}$$


Beware! There is a long list of caveats associated with this method. In particular, it assumes the existence of a dominant pole. For details, see Section 7.3.2 of Gray & Meyer or Chapter 8 of Tom Lee's "Design of CMOS RFICs".

However, OZs can give a pessimistic estimate of BW with much less computational complexity than an exact analysis.

For our circuit we will consider only C_{gs} and C_{gd} :

(i) $C_{gs} \rightarrow$ calculate resistance facing C_{gs} (R_{Cgs})

$$R_{Cgs} = \frac{v_x}{i_x}$$

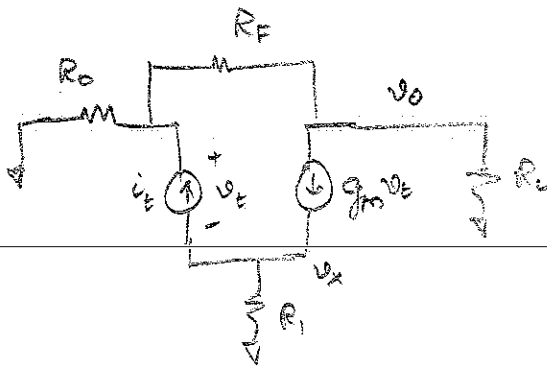


The algebra involved is tedious, but to simplify things, assume that

- A_V is large
- $R_0 = R_L = R$

Then,
$$R_{Cgs} = \frac{R}{R_S} \cdot \frac{1}{g_m}$$

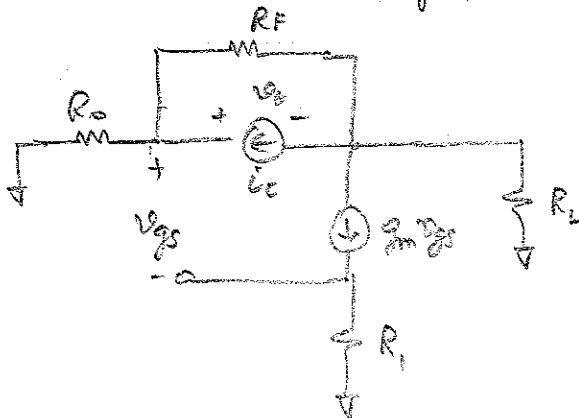(ii) To calculate R_{Cgd} , the resistance facing C_{gd} :



$$R_{Cgd} = \frac{v_x}{i_x}$$

Again, after painful algebra and same assumptions as before,

$$R_{Cgd} \approx |A_V| \frac{R}{2}$$

$$\Rightarrow \omega_{3dB} \approx \frac{1}{C_{gd} R_{Cgd} + C_{gs} R_{Cgs}} = \frac{1}{|A_V| \left(\frac{C_{gs}}{g_m} + \frac{R C_{gd}}{2} \right)}$$

Design: Very easy to design for equal source and load resistances, i.e., $R_0 = R_L = R$ (which are usually known)

$$\Rightarrow R_{in} = \frac{R_L + R_F}{1 + G_m R_0} = \frac{R + R_F}{1 + G_m R}$$

$$R_{out} = \frac{R_0 + R_F}{1 + G_m R_L} = \frac{R + R_F}{1 + G_m R}$$

$$R_{in} = R_{out}$$

For power match at both ports, set $R_{in} = R_{out} = R$

$$\Rightarrow R = \frac{R + R_F}{1 + G_m R} \Rightarrow 1 + G_m R = 1 + \frac{R_F}{R} \quad \text{or} \quad \boxed{G_m = \frac{R_F}{R^2}} \quad (1)$$

With a given gain specification

$$A_V \approx \frac{1}{2} G_m R_L \Rightarrow \boxed{G_m = \frac{2|A_V|}{R_L}} \quad (2)$$

$$\Rightarrow \boxed{R_F = \frac{2|A_V| R^2}{R_L}} \quad (3)$$

Now, we only need to set g_m and R , to get

$$G_m = \frac{g_m}{1 + g_m R}$$


Advantages of shunt-series amp:

- broadband
- stable, accurate gain, $R_{in} \approx R_{out}$
- easy to design

Disadvantages:

- performance so-so
- Noisy
- With $R_{in} \neq R_{out}$, cannot get simultaneous power match at input & output. (the equations become inconsistent!)


Other wideband approaches:

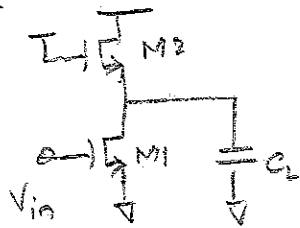



$$A_v = -\frac{g_{m1}}{g_{m2}} = \sqrt{\frac{2K_n'(W/L)_1 I_{D1}}{2K_n'(W/L)_2 I_{D2}}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$\omega_p \approx \frac{g_{m2}}{C_L}$$

Compare with

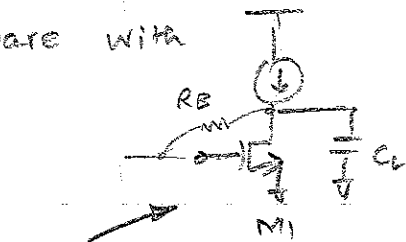

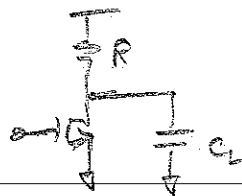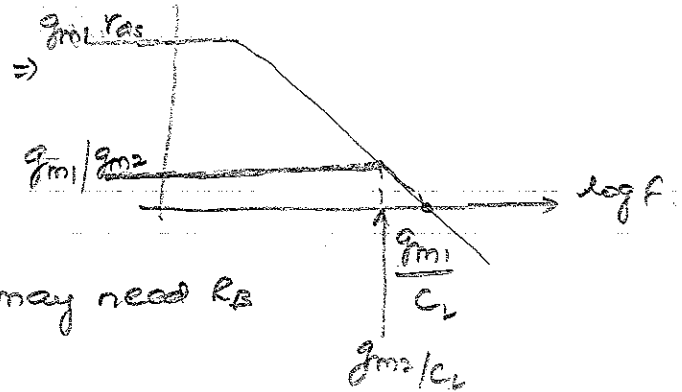output bias not accurately set \Rightarrow may need R_B




$$A_v = -g_m R$$

$$\omega_p \approx \frac{1}{RC_L}$$


usually the fastest because resistor has lower parasitic cap. compared to MOS current source

(08)

self-biased

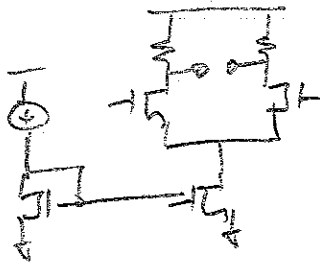


Cascading amplifiers:

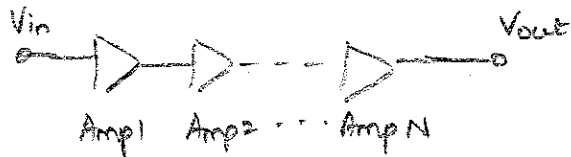

Consider a cascade of N identical amplifiers, each with a single-pole response

$$A(s) = \frac{A_0}{1 + s/\omega_p}$$

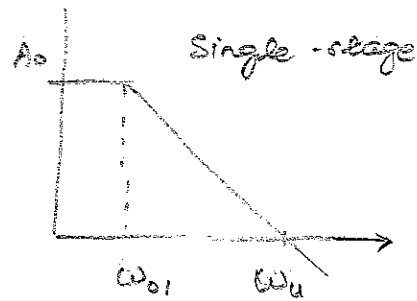

Recall gain-BW tradeoff for single stage! If we wanted $2A_0$ gain, we would necessarily have to give up BW

Overall transfer function is $H(s) = \left(\frac{A_0}{1 + s/\omega_p} \right)^N$

→ Calculate the 3dB frequency of the cascade, (ω_{0N})

$$\text{At } \omega = \omega_{0N}, |H(j\omega)| = \frac{1}{\sqrt{2}} |H(0)|$$



$$\Rightarrow \left(\frac{A_0}{\sqrt{1 + \frac{\omega_{0N}^2}{\omega_p^2}}} \right)^N = \frac{1}{\sqrt{2}} A_0^N \Rightarrow \frac{\omega_{0N}}{\omega_p} = \sqrt{2^{1/N} - 1}$$

$$\text{Recall } A_0 \omega_p = \omega_u \Rightarrow \omega_{0N} = \frac{\omega_u}{A_0} \sqrt{2^{1/N} - 1}$$

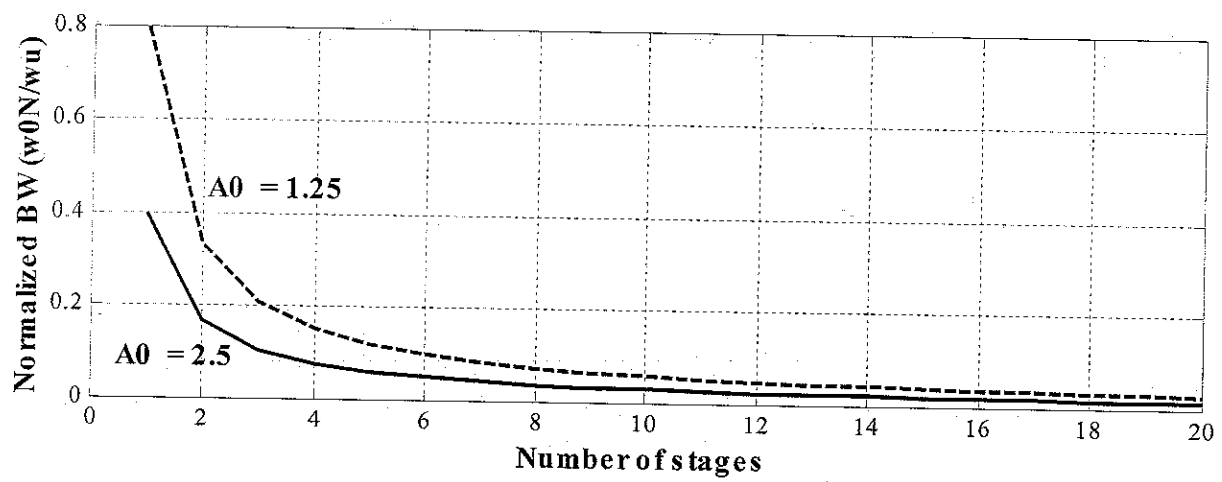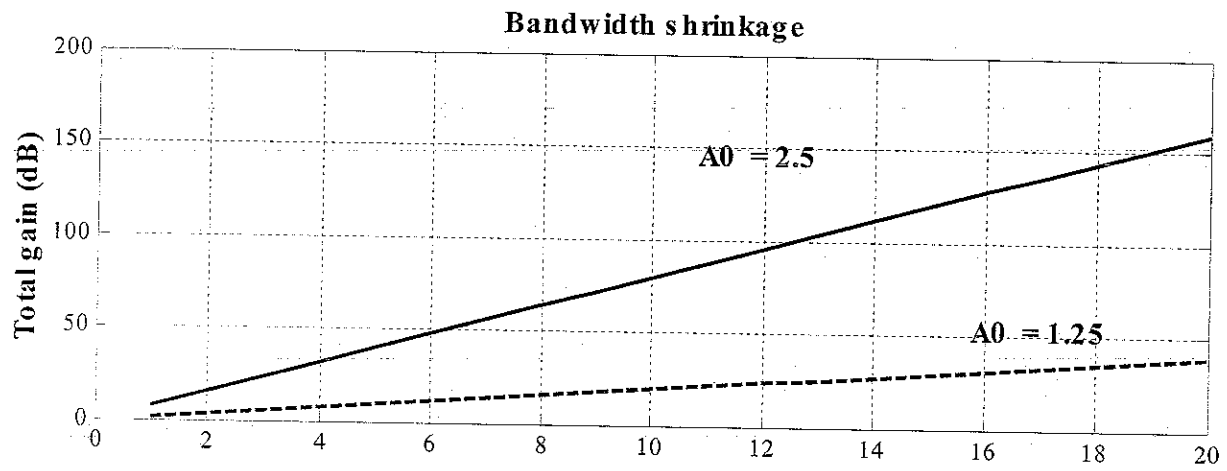(a) Bandwidth shrinkage: Suppose we fix the gain of each stage to be A_0 and cascade more and more stages. Assuming ($A_0 > 1$):

→ Total DC gain $A_{tot} = A_0^N \rightarrow \infty$ as $N \rightarrow \infty$

→ Cascaded 3dB frequency $\omega_{0N} \rightarrow 0$ as $N \rightarrow \infty$



(b) Now, fix total gain A_{tot} and find an optimal N to maximize BW:

→ The DC gain A_0 and pole frequency of each stage ω_p are variable, but the unity gain frequency of each stage is constant: $\omega_u = A_0 \omega_p$

$$\Rightarrow A_0^N = A_{tot} \quad \text{or} \quad A_0 = A_{tot}^{1/N}$$

$$\Rightarrow \omega_{ON} = \frac{\omega_u}{A_{tot}^{1/N}} \sqrt{2^{1/N} - 1}$$

⇒ Maximize BW: $\frac{d\omega_{ON}}{dN} = 0$

After some algebra: $N_{opt} = \frac{\ln 2}{\ln \left(1 + \frac{\ln 2}{2 \ln A_{tot}} \right)}$

For large A_{tot} ,

$$\ln \left(1 + \frac{\ln 2}{2 \ln A_{tot}} \right) \approx \frac{\ln 2}{2 \ln(A_{tot})} \Rightarrow N_{opt} \approx 2 \ln A_{tot}$$

⇒ Find optimum gain of each stage:

$$A_{0,opt} = A_{tot}^{1/N} = \exp \left(\frac{1}{N} \ln A_{tot} \right) \approx e^{1/2}$$

$$\Rightarrow A_{0,opt} = \sqrt{e}$$

⇒ Find optimum BW:

$$\omega_{ON,opt} = \frac{\omega_u}{A_{tot}^{1/N_{opt}}} \sqrt{2^{1/N_{opt}} - 1} \approx \frac{\omega_u}{\sqrt{e}} \left[\exp \left(\frac{1}{N_{opt}} \ln 2 \right) - 1 \right]^{1/2}$$

$$\omega_{ON,opt} \approx \omega_u \sqrt{\frac{\ln 2}{2e \ln A_{tot}}}$$

⇒ Overall BW trades-off as square-root of total gain!!

