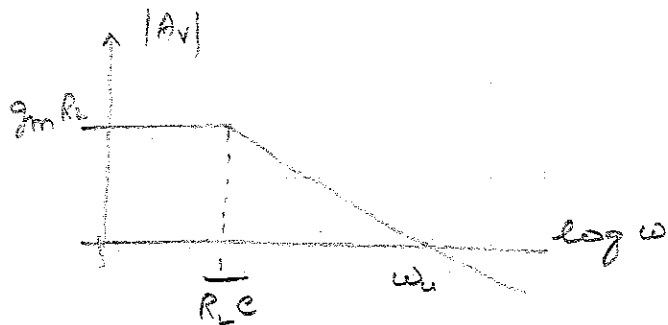
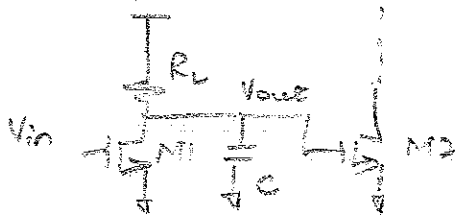
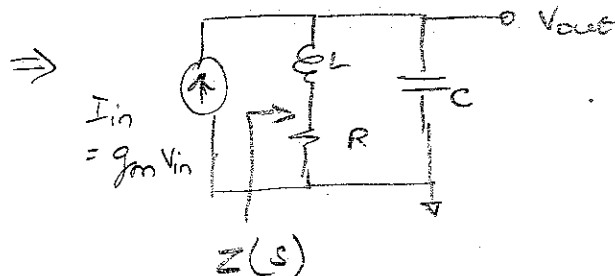
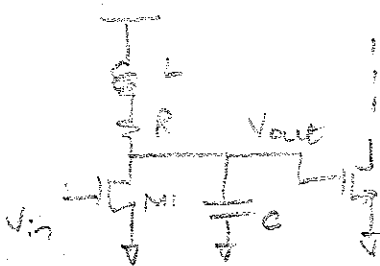


Lecture #10Bandwidth Enhancement using zeros:• Basic c-s stage:

Basic idea: Use an inductor to introduce "peaking" into the frequency response to increase 3dB frequency!

① Shunt peaking:

- At low frequencies, inductor is a short and gain is a constant $g_m R$
- At very high frequencies, C presents a diminishing impedance, and gain falls off.
- At mid-band frequencies, L introduces a zero i.e. presents an impedance component that increases with frequency & offsets the decreasing component presented by C .

More intuition: Recall that in L , current lags voltage. Here, L delays the flow of current to the $L-R$ branch, which leaves more current to charge the C .
 \Rightarrow faster risetime \Rightarrow more BW.

(A) Analysis: $z(s) = (sL + R) \parallel \frac{1}{sC} = R \frac{sL/R + 1}{s^2 LC + sRC + 1}$

• Since voltage gain $|A_v| = g_m |z(j\omega)|$, it is sufficient to study the frequency response of $z(s)$.

• Here: one zero $\omega_z = -R/L$

& two poles, possibly complex conjugate.

• Note that when $L \rightarrow 0$, this boils down to the "un-peaked" C-S amp: $z_0(s) = R \frac{1}{1 + sRC} = R \frac{1}{1 + s/\omega_c}$

• Define the following variables:

(i) uncompensated 3dB BW: $\omega_c = \frac{1}{RC}$

(ii) "New" time constant $\tau = L/R$

(iii) $m = \frac{\text{Uncompensated 3dB time constant}}{\text{New time constant}} = \frac{RC}{L/R}$

$$\Rightarrow \frac{z(s)}{R} = \frac{s\tau + 1}{s^2 \tau^2 m + s\tau m + 1}$$

• Find the compensated 3dB BW:

At $\omega = \omega_{3dB}$, $\left| \frac{z(j\omega)}{R} \right| = \frac{1}{\sqrt{2}}$

$$\Rightarrow \left| \frac{1 + j\omega\tau}{(1 - \omega^2 \tau^2 m) + j\omega\tau m} \right| = \frac{1}{\sqrt{2}}$$

$$\text{or } \frac{1 + \omega^2 \tau^2}{(1 - \omega^2 \tau^2 m)^2 + (\omega^2 \tau^2 m)^2} = \frac{1}{2}$$

Define $x = \omega^2 \tau^2$;

$$\Rightarrow \frac{x + 1}{(1 - mx)^2 + m^2 x} = \frac{1}{2}$$

$$\Rightarrow m^2 x^2 + (m^2 - 2m - 2)x - 1 = 0$$

$$\Rightarrow x = \frac{(2m+2-m^2) + [(2m+2-m^2)^2 + 4m^2]^{\frac{1}{2}}}{2m^2}$$

$$\text{or } x = \frac{1}{m^2} \left\{ \left(m+1 - \frac{m^2}{2} \right) + \left[\left(m+1 - \frac{m^2}{2} \right)^2 + m^2 \right]^{\frac{1}{2}} \right\}$$

$$\text{But } x = (\omega_{3dB} \cdot \tau)^2 = \left(\frac{\omega_{3dB}}{\omega_1} \cdot \omega_1 \tau \right)^2 = \left(\frac{\omega_{3dB}}{\omega_1} \right)^2 \cdot \frac{1}{m^2}$$

$$\therefore \frac{\omega_{3dB}}{\omega_1} = \left[\left(m+1 - \frac{m^2}{2} \right) + \left\{ \left(m+1 - \frac{m^2}{2} \right)^2 + m^2 \right\}^{\frac{1}{2}} \right]^{\frac{1}{2}} \quad (\text{BW} \times \text{F})$$

- This gives us the ratio of the new 3dB BW to the uncompensated BW in terms of "m".

(a) Optimization of "m" for max. ω_{3dB}/ω_1 (see plot of BWXF vs m)

$$\Rightarrow \text{Max. BW extension occurs when } m \approx 1.4, \text{ and } \frac{\omega_{3dB}}{\omega_1} = 1.85 \leftarrow \text{BW extension factor (BWXF)}$$

But, is this a good value for m? To investigate normalize the frequency axis and plot $|Z(j\omega)|$



$$\rightarrow \text{Define } s_1 = \frac{s}{\omega_1} \Rightarrow s = s_1 \omega_1$$

$$\therefore \frac{Z(s)}{R} = \frac{s_1 \omega_1 \tau + 1}{s_1^2 (\omega_1 \tau)^2 m + s_1 (\omega_1 \tau) m + 1} \quad \text{But } m = \frac{RC}{L/R} = \frac{1}{\omega_1 \tau}$$


$$\Rightarrow \frac{Z(s_1)}{R} = \frac{s_1/m + 1}{s_1^2/m + s_1 + 1} \Rightarrow \omega_1 \tau = 1/m$$

Now define $s = j\omega$ so that $s_1 = j \frac{\omega}{\omega_1} = j\omega_{norm}$

& plot $|Z(j\omega)|/R$ vs ω_{norm} . (see graph)

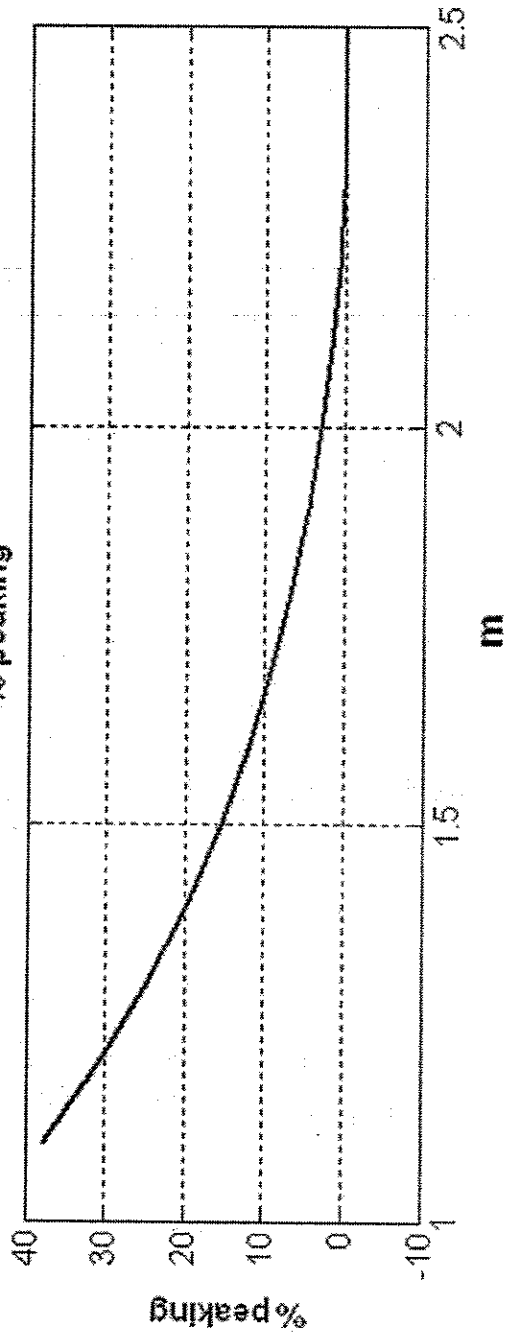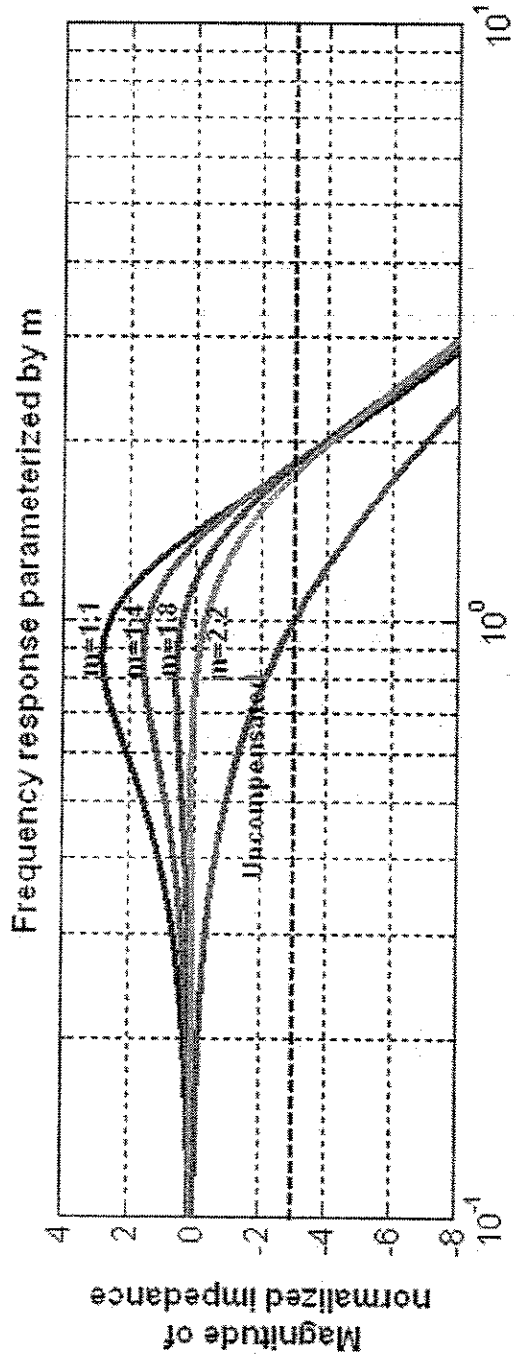

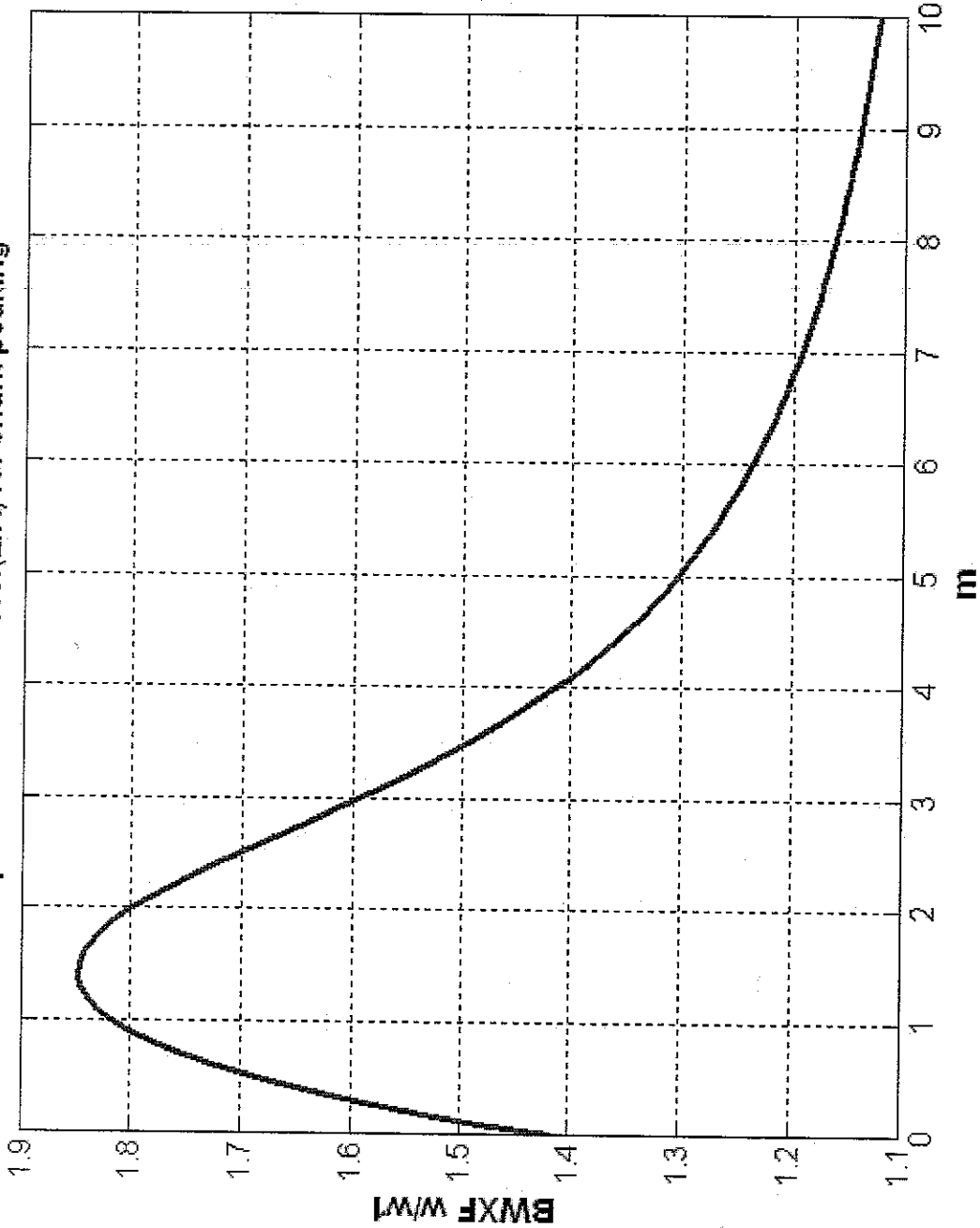Optimization of $m = RC/(L/R)$ for shunt peaking



$\frac{|Z(j\omega)|}{R}$ is shown as a function of the normalized frequency for various values of m . Also plotted is the % peaking as a function of m .

- Note that for the optimum $m (= 1.4)$, the peaking is about 20%, with a BWXF = 1.85. This is often unacceptable
- If we set $m=2$, we still get BWXF ≈ 1.8 , but the peaking is only 3%. \Leftarrow frequently used "optimum"

(b) Optimization for maximally flat response (Butterworth)

\rightarrow used when peaking is absolutely unacceptable.

\Rightarrow Form expression for $\frac{|Z(j\omega)|}{R}$ and maximize

the number of derivatives w.r.t ω that are zero at DC

$$\Rightarrow m = 1 + \sqrt{2} \approx 2.41$$

From the graph of BWXF vs m ,

when $m = 2.41$, BWXF = 1.72

(c) Optimization for minimum group-delay distortion (Bessel)

- Important in optical communication application
- Ideally, phase response of wideband amp. must increase linearly with frequency. In this case, we get equal delay on all frequency components of the signal. $\Rightarrow d\phi(\omega)/d\omega = \text{constant}$ at all frequencies.
- Non-linear phase response causes unequal delay of the frequency components and causes "group-delay distortion"
- Impossible to obtain group delay flatness over infinite BW with a finite order network

⇒ compromise → optimize for maximally flat group delay:

Define $T_D(\omega) = -\frac{d\phi(\omega)}{d\omega}$


→ Maximize number of derivatives of $T_D(\omega)$ whose value is zero at DC

→ $M = 3.10$ & $BW \times F = 1.6$

(different result from optimization for maximally flat magnitude response)!

- Group delay distortion causes inter-symbol interference and hence closes the eye opening at the sampling instant. This is often the limiting factor in high data-rate digital communication systems (eg. optic fibre communication; wireless UWB)

B Design

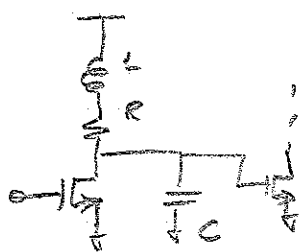


— Given the DC gain, load cap C, ω_{3dB} and an optimization constraint (max. BW, maximally flat magnitude or minimum group-delay distortion)

Find $\omega_1 = \frac{\omega_{3dB}}{BW \times F} = \frac{1}{RC} \Rightarrow$ Find R

→ From $|A(0)| = g_m R$, find g_m


→ Find L using $m = \frac{RC}{L/R} \Rightarrow L = \frac{R^2 C}{m}$

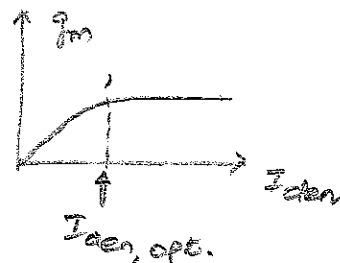- For power-efficient design: recall!
- Usually, C is not known at the beginning of the design, and is dictated by other constraints
- Can use crummy, low-Q inductors:



Since R is in series with it anyway, we can absorb the series resistance of L into the total resistance.

2) Zero-peaked c-s amplifier:

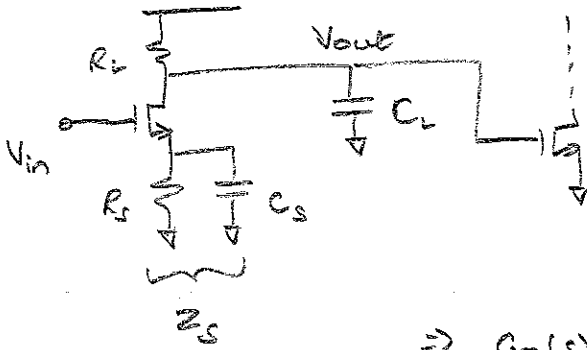

Effective transconductance:

$$G_m(s) = \frac{g_m}{1 + g_m Z_s}$$

$$Z_s = R_s \parallel \frac{1}{sC_s} = \frac{R_s}{1 + sC_s R_s}$$

$$\Rightarrow G_m(s) = \frac{g_m}{1 + g_m R_s} \cdot \frac{1 + sC_s R_s}{1 + sC_s \left(\frac{R_s}{1 + g_m R_s} \right)}$$

$$\approx G_{mo} \frac{1 + sC_s R_s}{1 + sC_s / g_m}$$

$$A_v(s) = G_m(s) \cdot Z_L(s)$$




$$= G_{mo} \frac{1 + sC_s R_s}{1 + sC_s / g_m} \cdot \frac{R_L}{1 + sC_L R_L}$$

$$= \underbrace{(G_{mo} R_L)}_{\text{D.C gain (I)}} \cdot \underbrace{\left(\frac{1 + sC_s R_s}{1 + sC_L R_L} \right)}_{\text{Pole-zero cancellation (II)}} \cdot \underbrace{\left(\frac{1}{1 + sC_s / g_m} \right)}_{\text{high-frequency pole (III)}}$$

D.C gain

Pole-zero cancellation

high-frequency pole

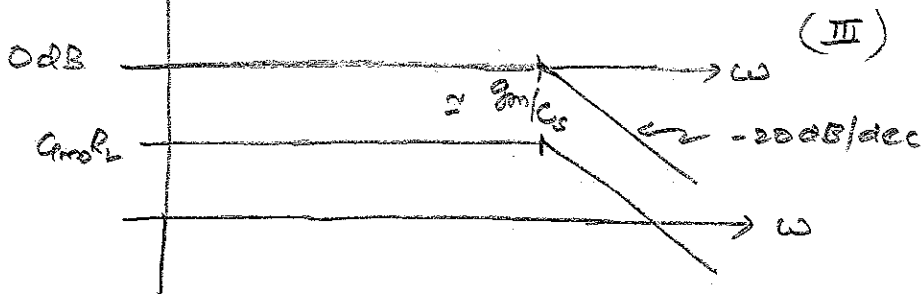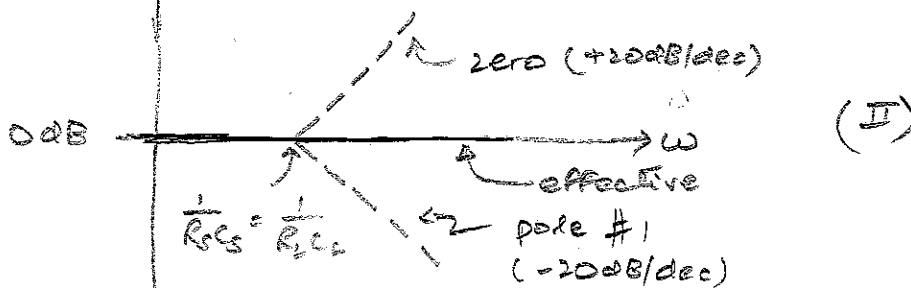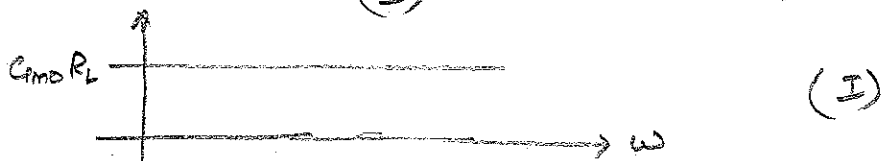

Total response