

Mixers: Used for frequency translation


- upconversion of baseband signals to RF (or IF)
- downconversion of RF signals to IF or baseband

Two major types - non-linear mixers:

- linear, periodically time-varying mixers (LPTV)
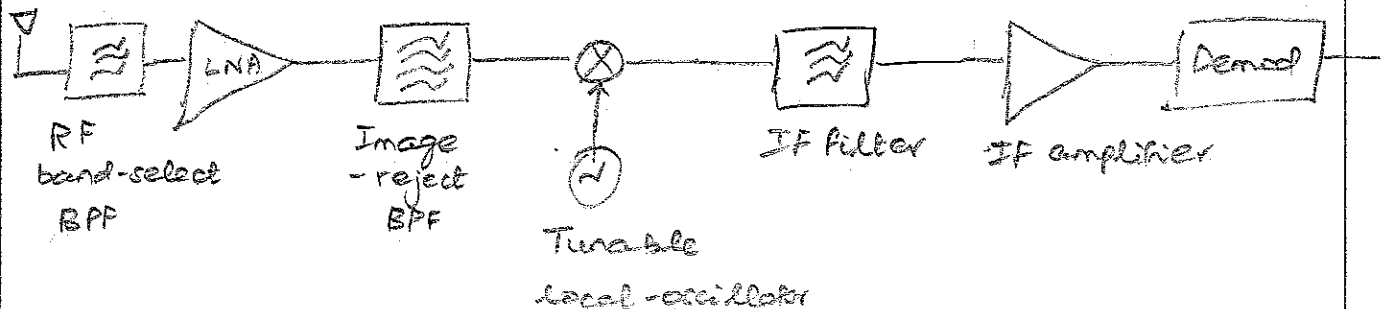
### ① Downconversion mixers (Receive mixers)

Consider a typical super-heterodyne receiver:



- Recall that the signal power at the antenna is very low ( $-100 \text{ dBm} = 10^{-13} \text{ W}$  or  $3.16 \mu\text{V}$  into  $50 \Omega$ )
- Overall receiver gain must be  $\sim 100 \text{ dB}$ , distributed over RF, IF and baseband stages.
- Consider a simple mixer:

$$\text{RF} \rightarrow \begin{array}{c} \text{X} \\ \uparrow \\ \text{LO} \end{array} \rightarrow \text{IF}$$

$$\text{RF: } x_{\text{RF}}(t) = A_{\text{RF}} \cos \omega_{\text{RF}} t$$


$$\text{LO: } x_{\text{LO}}(t) = A_{\text{LO}} \cos \omega_{\text{LO}} t$$

Mixer performs time-domain multiplication:

$$\begin{aligned} x_{\text{IF}}(t) &= x_{\text{RF}}(t) \cdot x_{\text{LO}}(t) = A_{\text{RF}} A_{\text{LO}} \cos \omega_{\text{RF}} t \cos \omega_{\text{LO}} t \\ &= \frac{1}{2} A_{\text{RF}} A_{\text{LO}} \left[ \underbrace{\cos(\omega_{\text{RF}} - \omega_{\text{LO}}) t}_{\text{desired IF term}} + \underbrace{\cos(\omega_{\text{RF}} + \omega_{\text{LO}}) t}_{\text{up-conversion mixing term}} \right] \end{aligned}$$

- For more general modulated RF signals, recall that time-domain multiplication  $\equiv$  frequency-domain convolution

22-140 100 sheets  
 CAMPAL

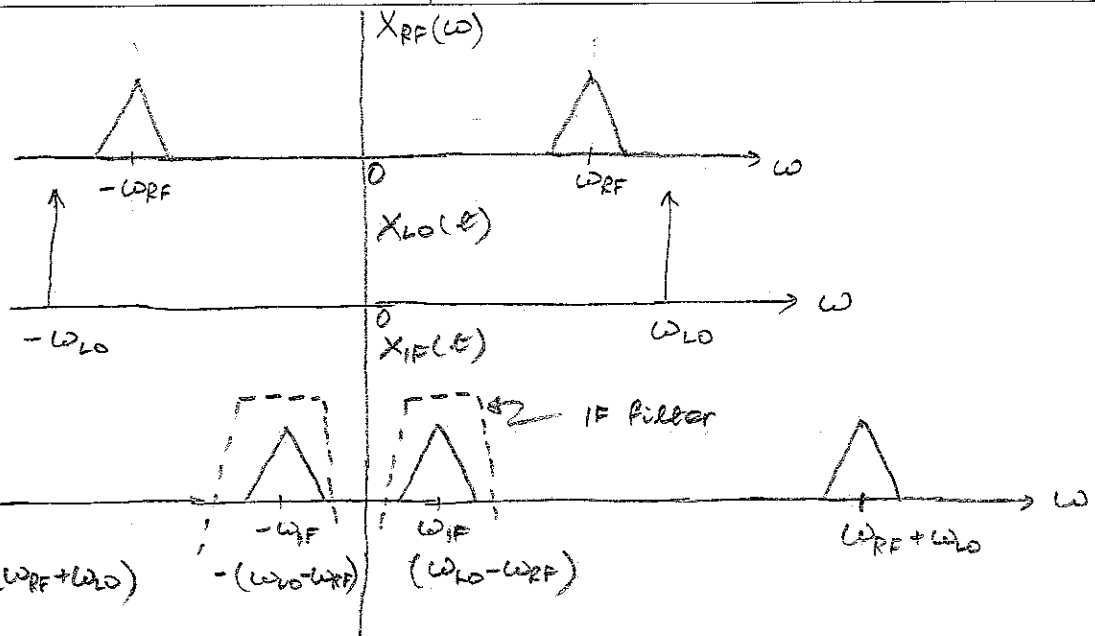

(a) Conversion gain:  $G_c = \frac{\text{Amplitude of desired IF output}}{\text{Amplitude of RF input}}$


$$= \frac{\frac{1}{2} A_{RF} \cdot A_{LO}}{A_{RF}} = \frac{1}{2} A_{LO}$$

$\uparrow$   
 LO amplitude

Active mixers:  $G_c > 1$  (generally)

Passive mixers:  $G_c < 1$


(b) Image-frequency problem:

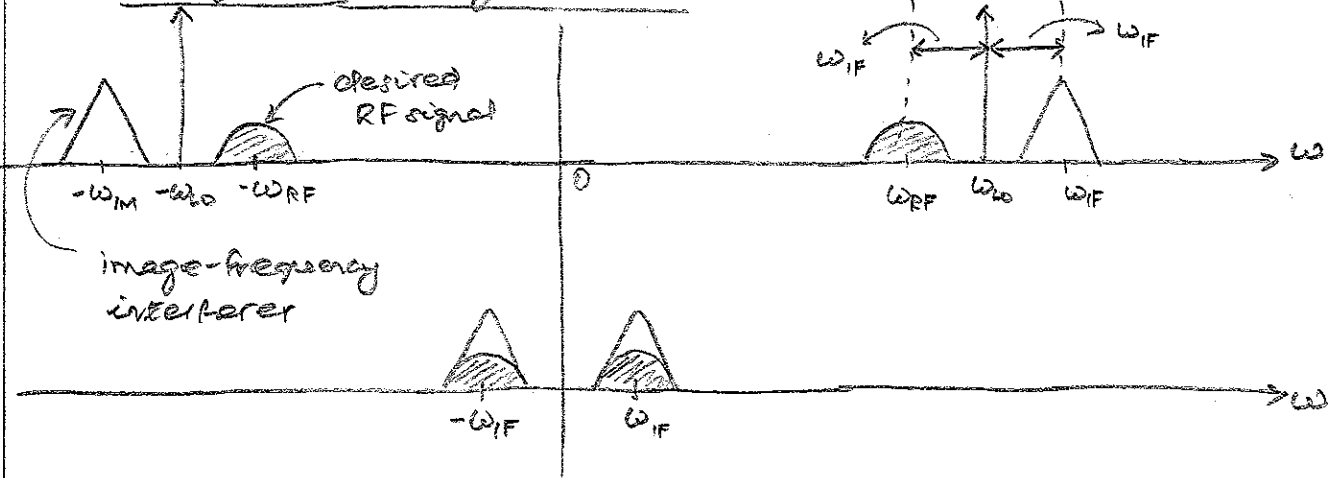

- No filtering of image prior to mixer;
- ⇒ image folds down to the same IF → can't separate signal from image-frequency interferer after mixing.


- Solutions to the image problem:
  - image reject filter (super-heterodyne / high-IF receiver)
  - image-reject architectures (Hartley receiver, Weaver receiver)

(c) Noise figure of mixers:

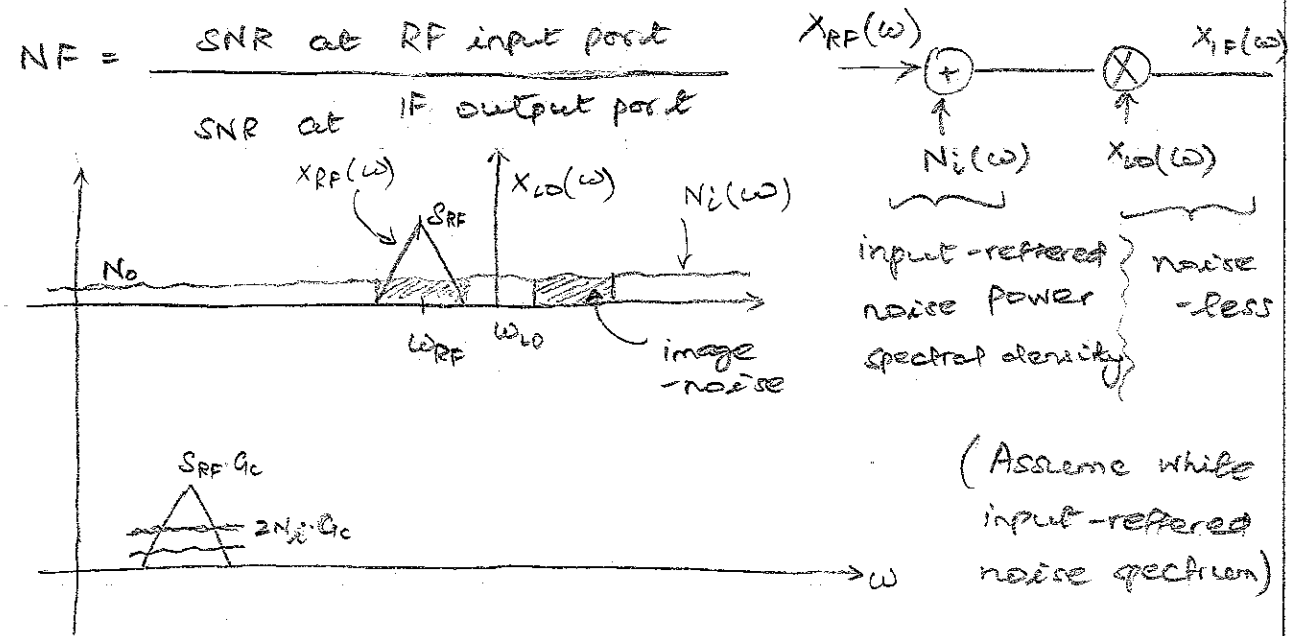

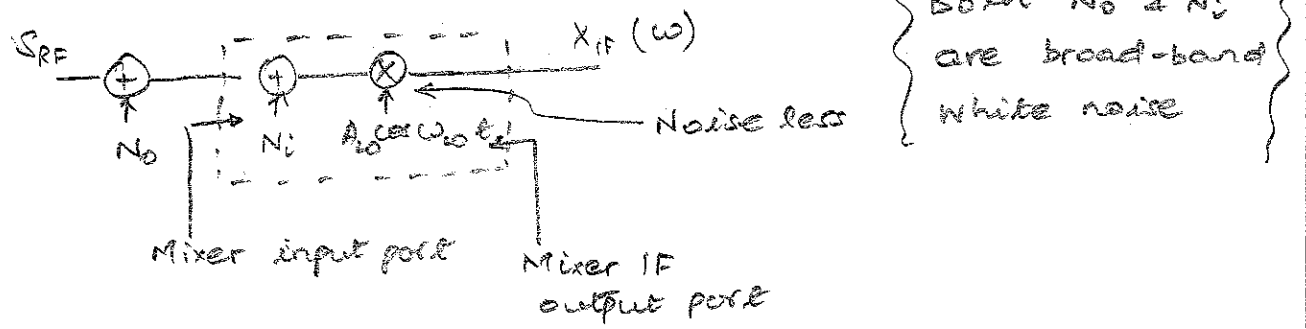(i) Single-sideband noise figure: ( $NF_{SSB}$ )

Assume that a "useful" RF signal is present only on one side of  $\omega_{LO}$ :




Input SNR =  $\frac{S_{RF}}{N_0}$  & Output SNR =  $\frac{S_{RF} \cdot G_c}{(2N_0 + 2N_i) G_c}$

$\Rightarrow NF_{SSB} = \frac{2(N_0 + N_i)}{N_0} = 2 + \frac{2N_i}{N_0}$

→ Even if mixer were noiseless,  $N_{F_{DSB}} = 3dB!!$

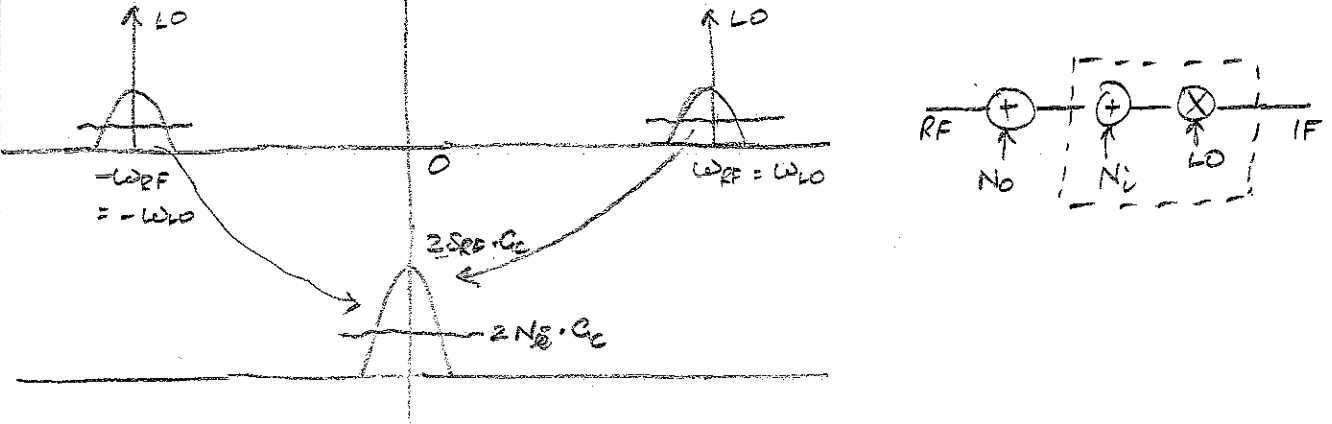(ii) Double-sideband noise figure ( $N_{F_{DSB}}$ )


Now consider a direct-conversion receiver:



$$N_{F_{DSB}} = \frac{SNR_{IN}}{SNR_{OUT}} = \frac{S_{RF}/N_0}{2S_{RF} \cdot G_C / (2N_0 + 2N_i)G_C} = \frac{N_0 + N_i}{N_0}$$

→ Now, if mixer were noiseless ( $N_i = 0$ );  $N_{F_{DSB}} = 0dB$ .

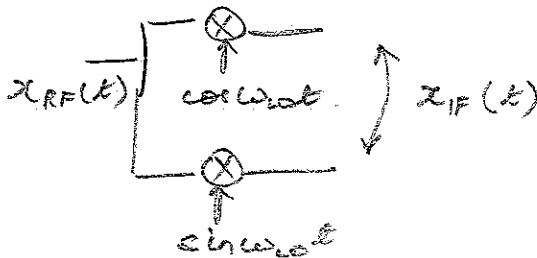Note that in general, we cannot use just one mixer for direct conversion. We need quadrature downconversion!




(More later!)

Mixers are generally noisy; need to precede with LNA to keep overall receiver NF low.

→  $N_{F_{DSB}} = N_{F_{SSB}} - 3dB$

(d) Power Isolation:

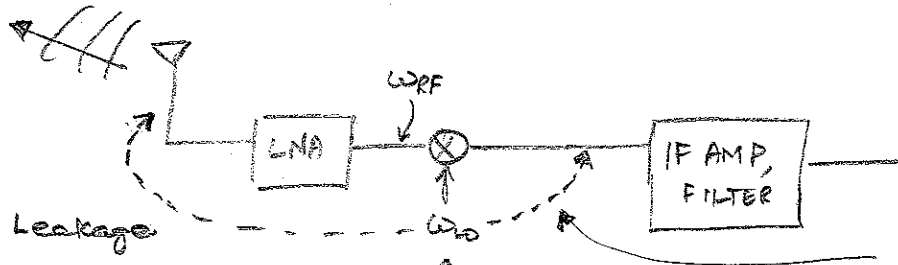


Leakage radiates out through antenna

LO amplitude usually much greater than RF

high LO-to-IF leakage + small IF signal ⇒ desensitization & saturation of IF amp.

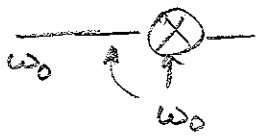
In a direct conversion receiver;  $\omega_{LO} = \omega_{RF} = \omega_0$



- We want RF signal only to be down converted to baseband
- If LO leaks to RF port and mixes with the LO, we get a low-frequency term that depends on the LO only. This can be much larger than the down converted RF.  
→ called self-mixing.

(e) Linearity & Spurious response

(i) RF path non-linearity:

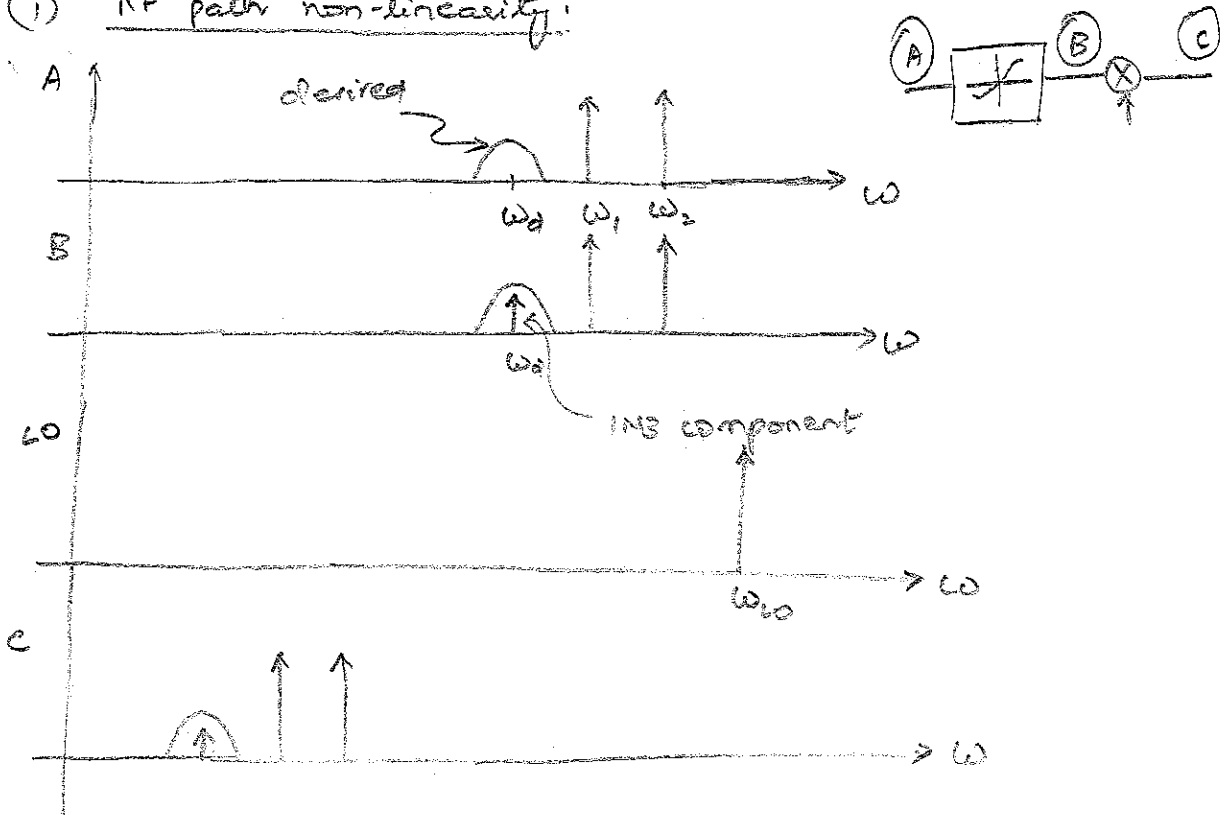

- Both signal & distortion component get downconverted
- Can define IIP3 for mixers similar to LNA's.

(ii) Spurs & effect of square-wave LO:

Example: Consider  $\omega_{RF} = 900\text{MHz}$

$$\omega_{IF} = 70\text{MHz}$$


High-side injection:  $\omega_{LO} = \omega_{RF} + \omega_{IF} = 970\text{MHz}$ .

→ Suppose that the LO is a square wave; it will contain harmonics at  $2\omega_{LO}, 3\omega_{LO}, \dots$ . An interferer could mix with these LO harmonics.

→ If an interferer were present at freq. such that  $2\omega_{LO} \pm \omega_x = \omega_{IF} = \omega_{RF} - \omega_{LO}$ , then these would mix with the second LO harmonic down to  $\omega_{IF}$ :  
 $\Rightarrow \omega_x = 2\omega_{LO} \pm \omega_{IF} = 2010\text{MHz}$  or  $1870\text{MHz}$ .

⇒ In general we want only input frequencies at  $|\omega_{LO} - \omega_{IF}|$  to be folded down to IF.

(f) Linearity of cascaded stages:

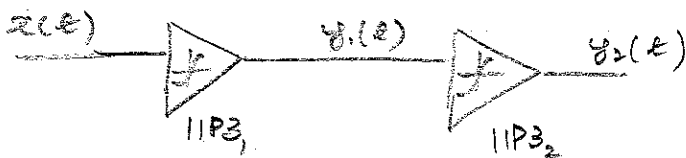

$$V_{IIP3} = \sqrt{\frac{4\alpha_1}{3\alpha_3}}$$

$$y_1(t) = \alpha_1 x(t) + \alpha_3 x^3(t) \quad (\text{ignore 2nd order N.L.})$$

$$y_2(t) = \beta_1 y_1(t) + \beta_3 y_1^3(t)$$

$$= \beta_1 [\alpha_1 x(t) + \alpha_3 x^3(t)] + \beta_3 [\alpha_1 x(t) + \alpha_3 x^3(t)]^3$$

$$= \alpha_1 \beta_1 x(t) + [\alpha_3 \beta_1 + \beta_3 \alpha_1^3] x^3(t) + \dots$$


$$\Rightarrow A_{IIP3} = \left[ \frac{4\alpha_1 \beta_1}{3(\alpha_3 \beta_1 + \beta_3 \alpha_1^3)} \right]^{1/2} = \left[ \frac{1}{\frac{3\alpha_3}{4\alpha_1} + \left(\frac{3\beta_3}{4\beta_1}\right)\alpha_1^2} \right]^{1/2}$$

$$\Rightarrow A_{IP3} = \left[ \frac{1}{\frac{1}{A_{IP3,1}^2} + \frac{\alpha_1^2}{A_{IP3,2}^2}} \right]^{\frac{1}{2}}$$

If fundamental gain of preceding stage is large, we need large  $A_{IP3,2}$  for good linearity.


⇒ For good linearity, need more gain at back end  
 For good noise performance, need more gain in front end.

② Single-balanced mixer:

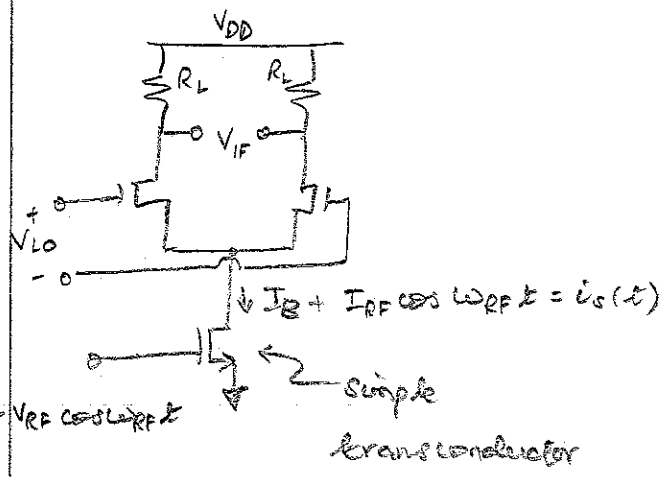

- Assume that  $V_{Lo}$  switches the "tail" current  $i_s(t)$  from one side to the other.
- The input voltage is converted to a current by a transconductor, which is a single NMOS here.
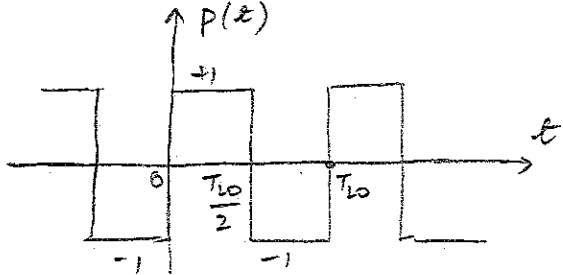
$$\rightarrow i_s(t) = I_B + g_m V_{RF} \cos w_{RF} t.$$



$p(t)$  = switching function  
 → square wave with period  $T_{Lo}$   
 → expand into Fourier series:

$$p(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos n\omega_{Lo} t + b_n \sin n\omega_{Lo} t] \quad (\omega_{Lo} = \frac{2\pi}{T_{Lo}})$$

$$\frac{a_0}{2} = \text{DC average} = 0; \quad a_n = \frac{2}{T_{Lo}} \int_0^{T_{Lo}} p(t) \cos n\omega_{Lo} t dt$$

= 0 for all n since  $p(t)$  is an odd function

$$b_n = \frac{2}{T_{Lo}} \int_0^{T_{Lo}} p(t) \sin n\omega_{Lo} t dt = 2 \cdot \frac{2}{T_{Lo}} \int_0^{T_{Lo}/2} \sin n\omega_{Lo} t dt$$

$$\Rightarrow b_n = \frac{4}{T_{L0}} \cdot \frac{1}{n\omega_{L0}} \left[ -\cos n\omega_{L0}t \right]_0^{T_{L0}/2} = \frac{4}{n\pi} [1 - \cos n\pi]$$

$$\Rightarrow b_n = \begin{cases} 0 & \text{for } n = 2, 4, 6, \dots \\ \frac{4}{n\pi} & \text{for } n = 1, 3, 5, \dots \end{cases}$$

$$\Rightarrow p(t) = \frac{4}{\pi} \left[ \sin \omega_{L0}t + \frac{1}{3} \sin 3\omega_{L0}t + \frac{1}{5} \sin 5\omega_{L0}t + \dots \right]$$


$$\therefore V_{IF}(t) = (I_B + I_{RF} \cos \omega_{RF}t) \cdot \frac{4}{\pi} \left[ \sin \omega_{L0}t + \frac{1}{3} \sin 3\omega_{L0}t + \dots \right]$$

$$= I_B \cdot \frac{4}{\pi} \left[ \sin \omega_{L0}t + \frac{1}{3} \sin 3\omega_{L0}t + \dots \right] \leftarrow \text{LO + LO harmonics feedthrough}$$

$$+ \frac{4}{\pi} I_{RF} \cos \omega_{RF}t \cdot \left[ \sin \omega_{L0}t + \frac{1}{3} \sin 3\omega_{L0}t + \frac{1}{5} \sin 5\omega_{L0}t + \dots \right]$$

$$= (\text{LO feedthrough terms})$$
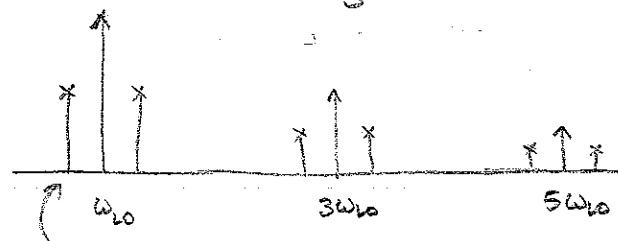
$$+ \frac{2I_{RF}}{\pi} \left[ \sin(\omega_{L0} - \omega_{RF})t + \sin(\omega_{L0} + \omega_{RF})t + \frac{1}{3} \sin(3\omega_{L0} - \omega_{RF})t + \frac{1}{3} \sin(3\omega_{L0} + \omega_{RF})t + \dots \right]$$



$\omega_{L0} - \omega_{RF}$   
(desired)




In upconversion, because the desired output, mixing terms and LO feedthrough terms are spaced closely in frequency, filtering to isolate the desired term is difficult.

Note: This spectrum is for an upconversion mixer whose input  $\omega_{RF} \ll \omega_{L0}$


→ poor isolation between LO & output ports can be problematic here.

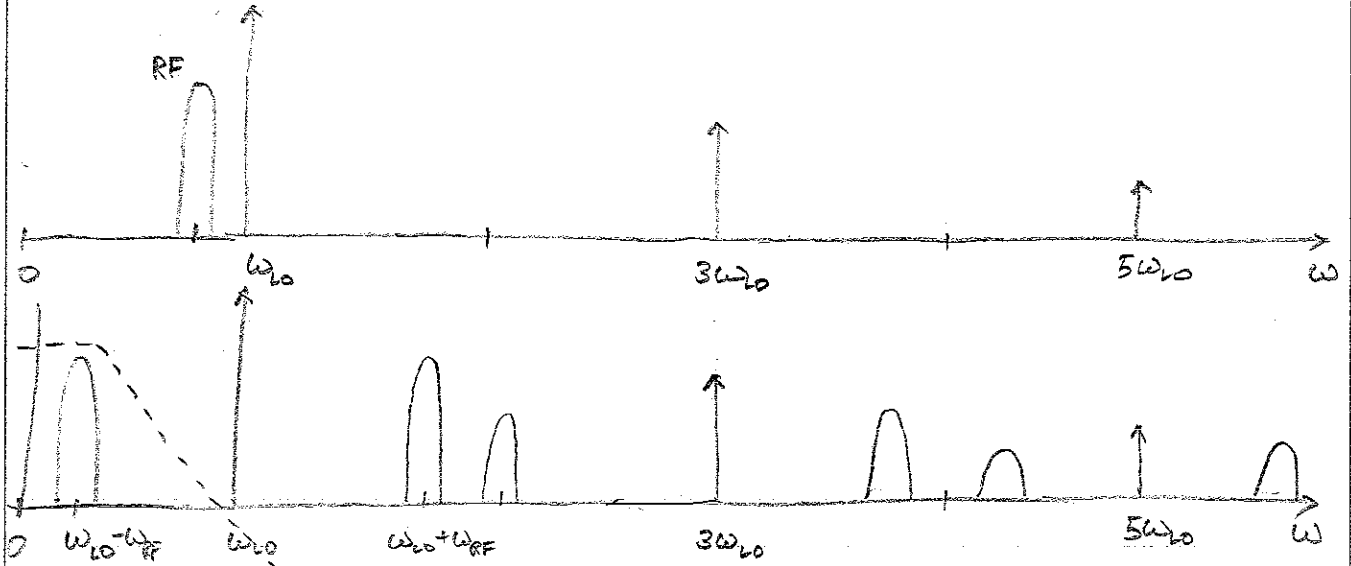(ii) Downconversion:  $\omega_{RF}$  and  $\omega_{LO}$  close together in frequency.




mixing terms + LO feedthrough far away from IF  $\Rightarrow$  easy filtering.

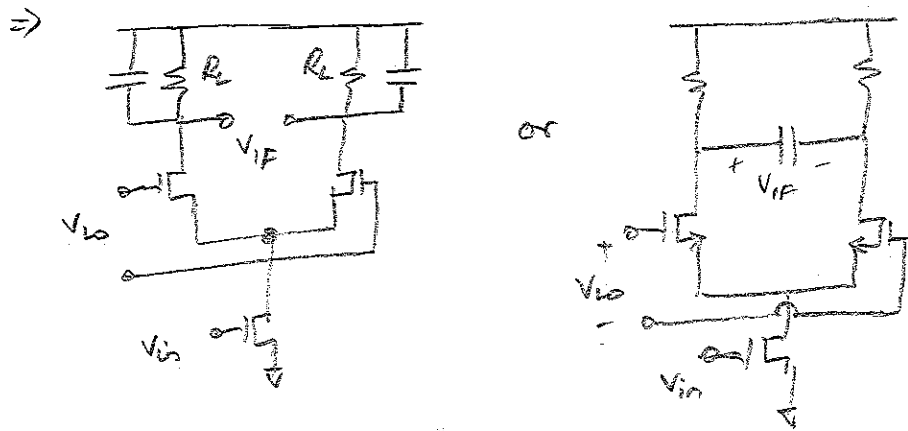LO-to-IF port isolation not very problematic



Conversion gain  $G_c = \frac{\text{IF amplitude}}{\text{RF amplitude}} = \frac{2 g_m V_{RF} / \pi \cdot R_L}{V_{RF}}$

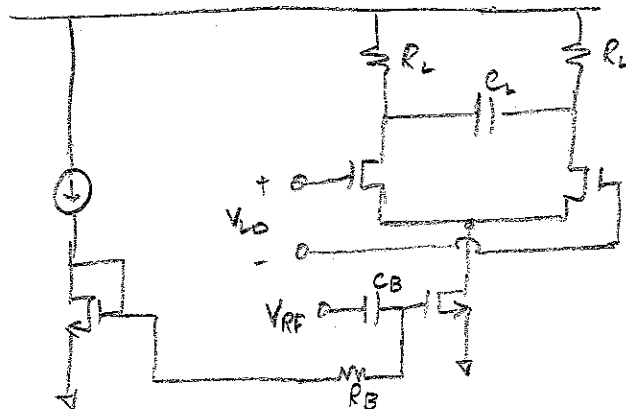
$$\Rightarrow G_c = \frac{2}{\pi} g_m R_L$$



Complete single-balanced mixer with biasing details
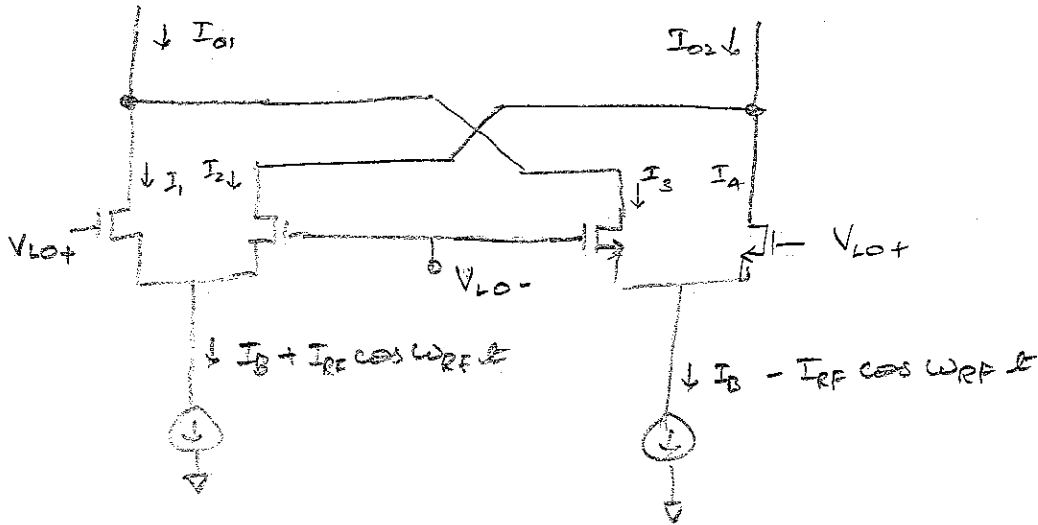
## Double-balanced mixer:

- Use a differential (or balanced) RF input, along with two cross-connected single-balanced mixers to cancel LO feedthrough terms:



$$I_1 - I_2 = (I_B + I_{RF} \cos \omega_{RF} t) p(t)$$


$$I_3 - I_4 = -(I_B - I_{RF} \cos \omega_{RF} t) p(t)$$

$$\begin{aligned} \text{Differential output current } I_d &= (I_1 + I_3) - (I_4 + I_2) \\ &= (I_1 - I_2) + (I_3 - I_4) \end{aligned}$$

$$I_d = 2 I_{RF} \cos \omega_{RF} t \cdot p(t)$$

$$\begin{aligned} &= \frac{4 I_{RF}}{\pi} \left[ \sin(\omega_{LO} - \omega_{RF})t + \sin(\omega_{LO} + \omega_{RF})t \right. \\ &\quad \left. + \frac{1}{3} \sin(3\omega_{LO} - \omega_{RF})t + \frac{1}{3} \sin(3\omega_{LO} + \omega_{RF})t + \dots \right] \end{aligned}$$
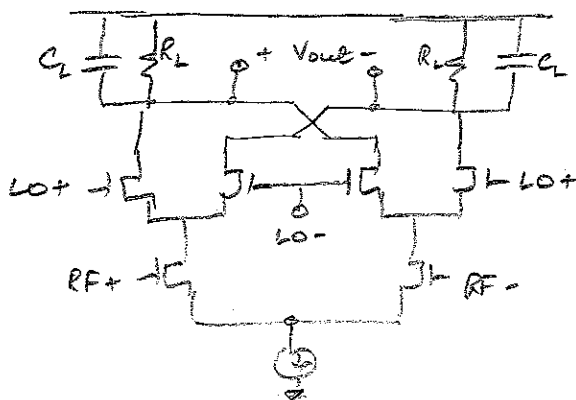
$$\Rightarrow G_c = \frac{4 g_m R_L}{\pi}$$



Gilbert cell mixer