

I

Preliminaries:

Any real modulated bandpass signal can be represented in one of three forms:

(a) Polar form:  $s(t) = a(t) \cos(\omega_c t + \phi(t))$

amplitude modulation
phase-modulation (excess phase)

total phase

Total phase  $\theta(t) = \omega_c t + \phi(t)$

Instantaneous frequency (in Hz)  $f_i(t) = \frac{1}{2\pi} \frac{d\theta_i(t)}{dt} = \frac{1}{2\pi} \frac{d\phi_i(t)}{dt}$

(b) Cartesian / Rectangular form:

$$s(t) = s_I(t) \cos \omega_c t - s_Q(t) \sin \omega_c t$$

$$= a(t) \cos \phi(t) \quad a(t) \sin \phi(t)$$

(In-phase component)
(quadrature component)

(c) Complex envelope (or analytic signal) representation

$$s(t) = \text{Re}[\tilde{s}(t) e^{j\omega_c t}]$$

$$\tilde{s}(t) = s_I(t) + j s_Q(t) \leftarrow \text{lowpass complex envelope (or analytic signal)}$$

$$= a(t) e^{j\phi(t)}$$

• Note that  $s_I(t)$  and  $s_Q(t)$  are real signals

⇒ Their Fourier transforms are conjugate symmetric  
(i.e. magnitude is an even function  
phase is an odd function)

$$\therefore s_I(t) \iff S_I(f) \quad \text{and} \quad S_I(f) = S_I^*(-f)$$


• Although signals inside a radio are real voltages or currents, pairs of signals taken together can be considered "complex" if satisfy the addition and multiplication rules of complex numbers.

ie.  $C_1 = a + jb$  &  $C_2 = p + jq$

$\Rightarrow C_1 + C_2 = (a+p) + j(b+q)$


and  $C_1 C_2 = (ap - bq) + j(bp - aq)$

Simple direct conversion transmitter:

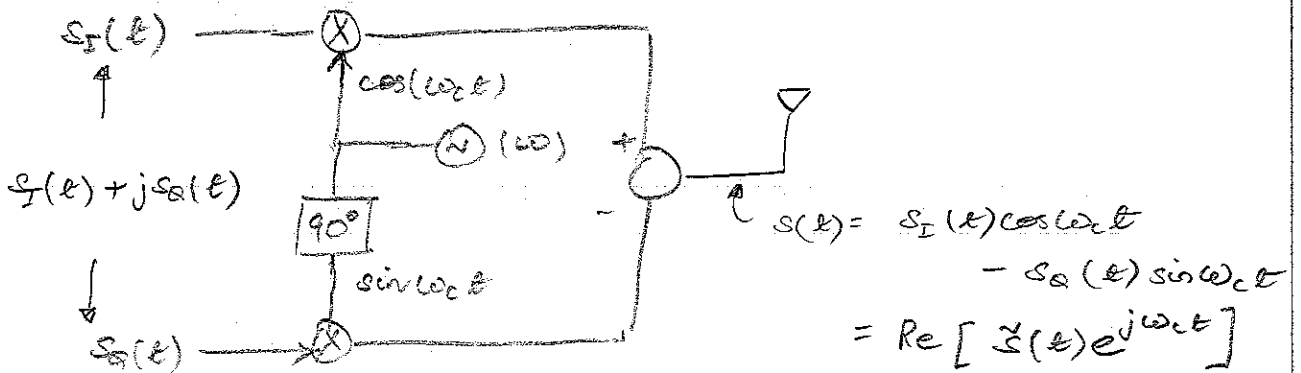

II

Simple Direct Conversion Receiver:

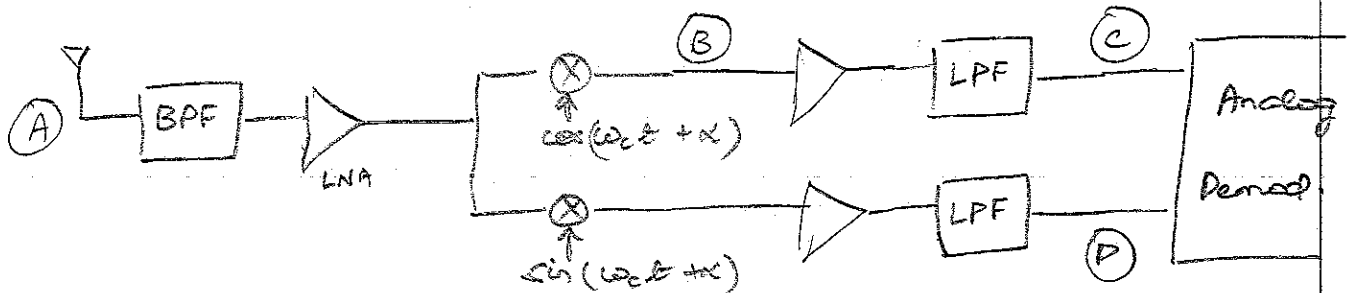

Assume  $\alpha = 0$  and trace signals through the receiver:


- Rx. signal (A) :  $g(t) = a(t) \cos(\omega_c t + \phi(t))$
- At (B) :  $g(t) \cos(\omega_c t + \alpha) = \frac{1}{2} a(t) [\cos(\phi(t) + \alpha) + \cos(2\omega_c t + \phi(t) + \alpha)]$
- At (C) :  $\frac{1}{2} a(t) \cos\{\phi(t)\}$  ( $\alpha = 0$ )

Similarly, at (D) :  $-\frac{1}{2} a(t) \sin\{\phi(t)\}$

Simple demodulation algorithm:

$\Rightarrow \sqrt{C^2 + D^2} = \frac{1}{2} a(t)$

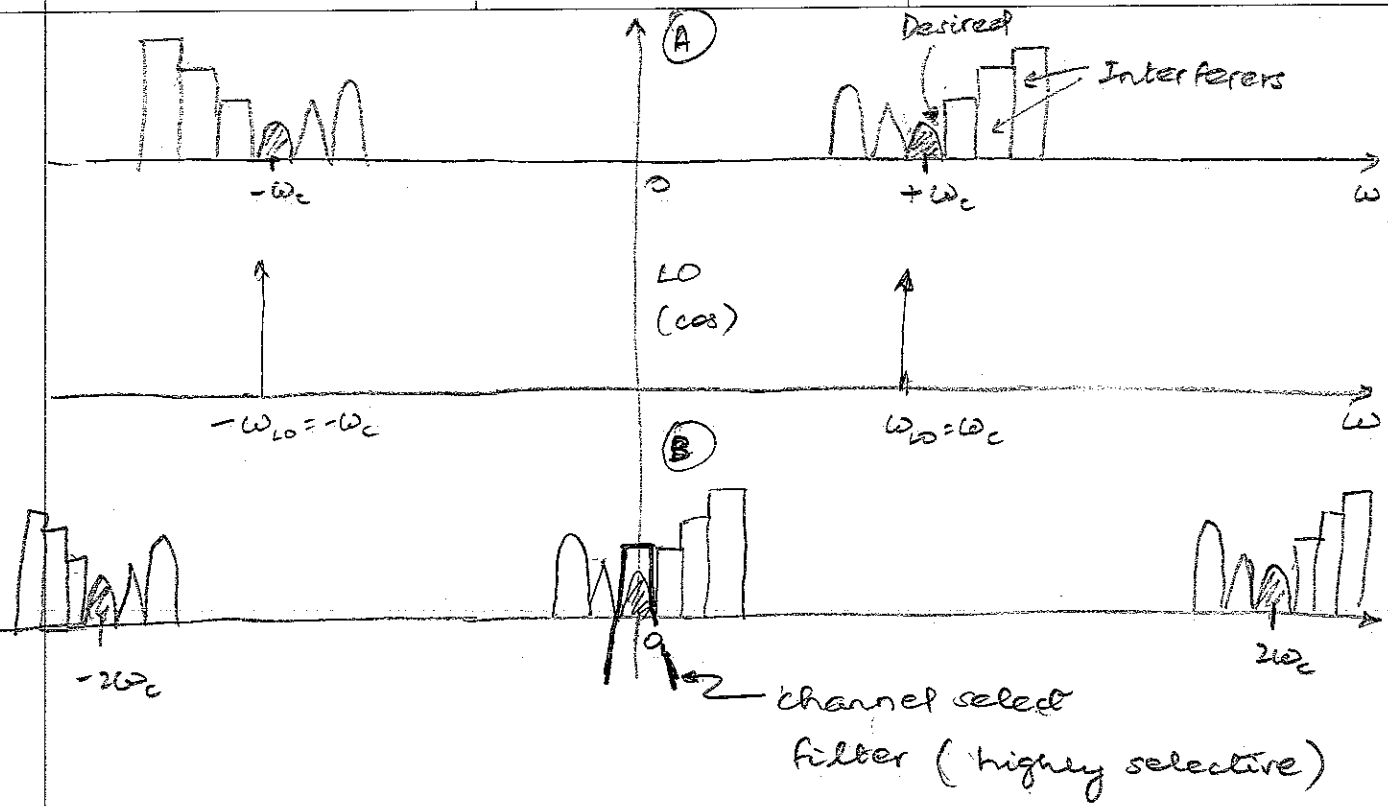$-\text{atan2}\left(\frac{D}{C}\right) = \phi(t)$  (4-quadrant arc tangent)




Note: The spectra are not quite accurate here because this cartoon shows (B) to have an unsymmetrical spectrum about DC although it is a real signal.

- Advantages:
  - 1) No image problem
  - 2) Easy prefiltering since components exist only about DC &  $2\omega_c$

Disadvantage: Highly selective analog channel-select filter required + problematic on-chip

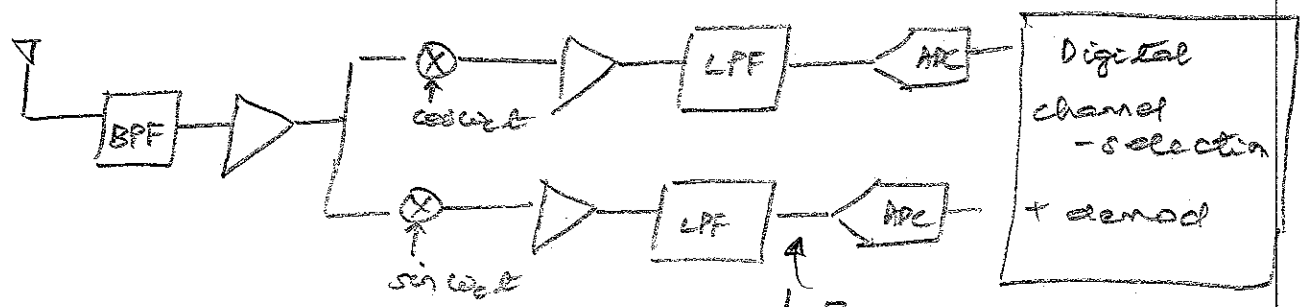Alternative: Digitize signals at (C) and (D) & then use a digital channel-select filter



ADC has to digitize desired signal + large blockers

⇒ • High dynamic range required for ADC.

• Also, need anti-aliasing filter for ADC


⇒ There is an inherent trade-off here:

high-order filter ⇒ low DR ADC

low-order filter ⇒ high DR ADC (In this case, the filter must provide adequate anti-aliasing for the ADC)

Why do we need I and Q in direct conversion?

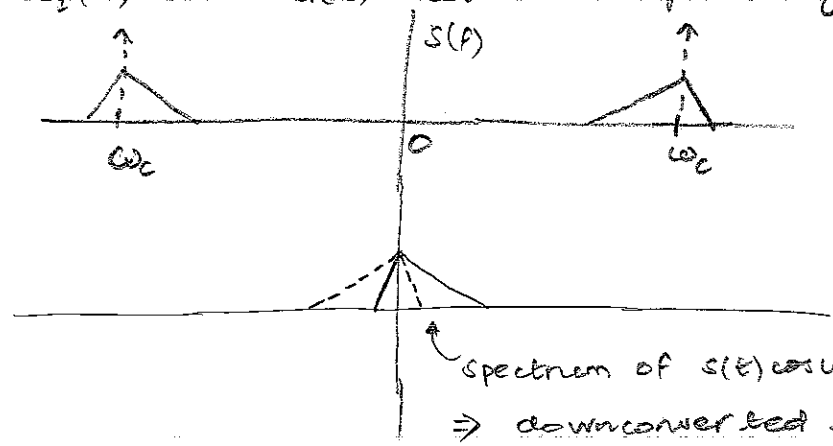(i)  $s_I(t)$  and  $s_Q(t)$  can be independently modulated data




(Input signal magnitude symmetric about DC, but not about  $\pm \omega_c$ )

(ii) RF-LO is not generally synchronized to carrier ( $\alpha \neq 0$ )

Consider AM only i.e.  $\phi(t) = 0$

⇒  $s(t) = a(t) \cos \omega_c t$

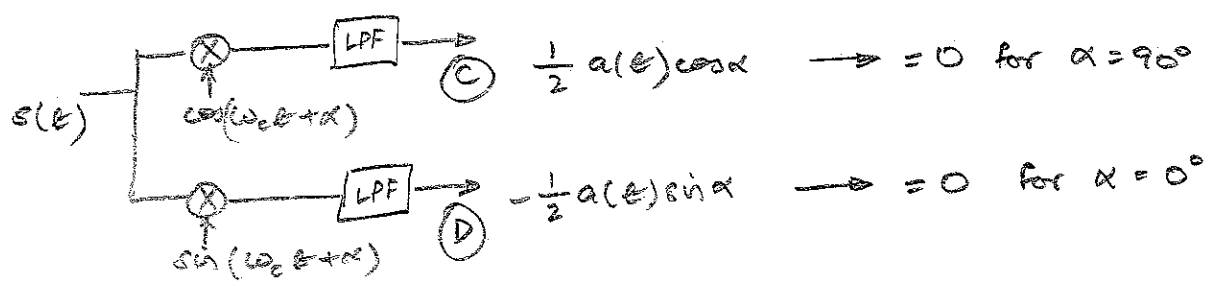

⇒ Suppose we had I-channel only, the output at (C) = 0 for  $\alpha = 90^\circ$  ⇒ signal lost completely

⇒ With I and Q, we have non-zero output at (C) or (D) or both.


(iii) Consider PM or FM signal with perfectly synchronized LO :  
 ( $\alpha=0$ )

$$s(t) = A \cos(\omega_c t + \phi(t))$$


$$\Rightarrow g_I(t) = A \cos \phi(t)$$

$$g_Q(t) = A \sin \phi(t)$$

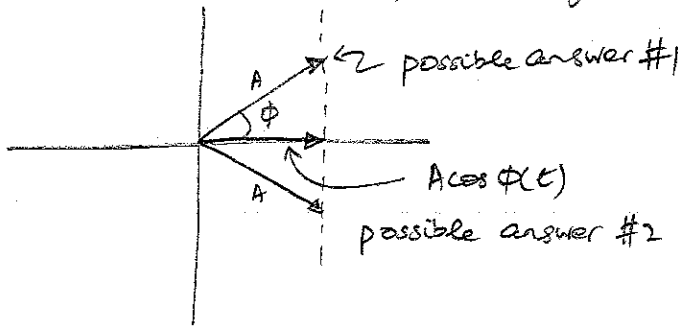Can't recover  $\phi(t)$  from  $g_I(t)$  alone or  $g_Q(t)$  alone :



Knowledge of  $g_I(t)$  only.

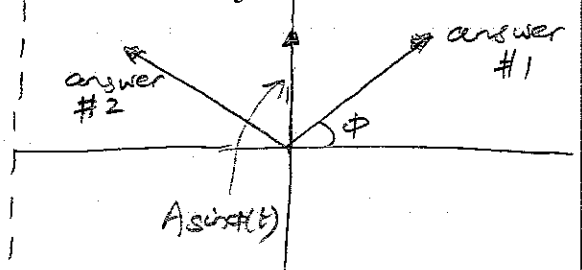


Knowledge of  $g_Q(t)$  only.


$\Rightarrow$  If  $\cos \phi(t)$  and  $\sin \phi(t)$  are both known, we can determine  $\phi(t)$  uniquely ( $\equiv$  four-quadrant arc-tangent)
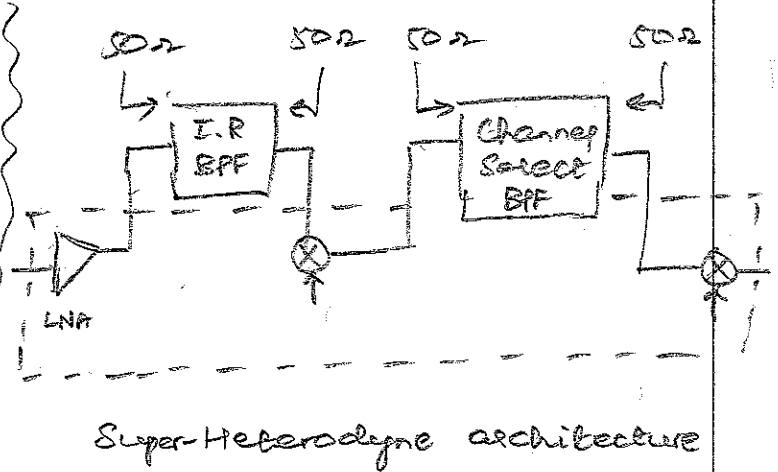
### DCR Advantages

- Highly integratable  
 $\rightarrow$  no off-chip filters except RF BPF
- No off-chip image reject filter  $\Rightarrow$  don't need to drive 50 $\Omega$
- No need for on-chip channel select BPF  
 $\Rightarrow$  LNA and mixer need not drive 50 $\Omega$ .
- Low-order LPF + high DR ADC  
 $\Rightarrow$  digital channel-select filter + demodulation  
 $\Rightarrow$  multi-standard radios.
- Relaxed I-Q matching requirements




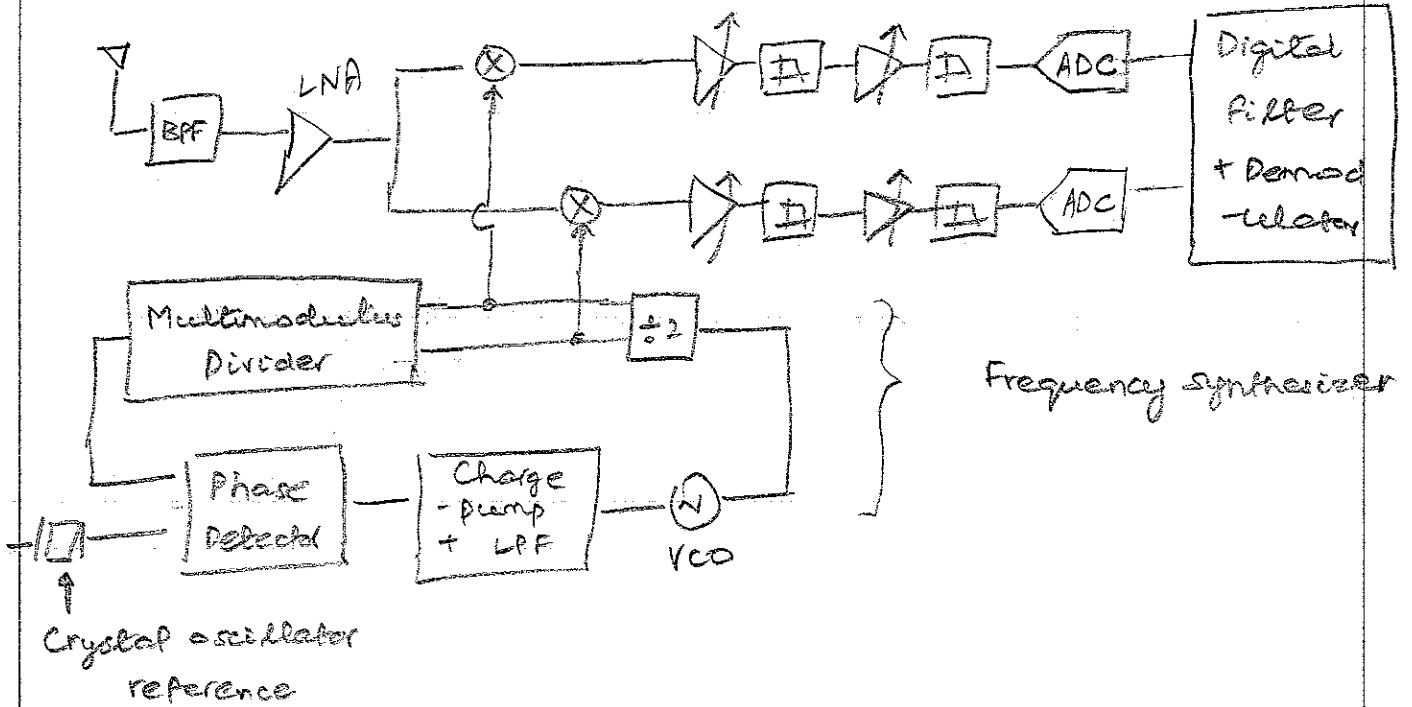- Only one frequency synthesis PLL required:



Problems with Direct Conversion receivers

(i) DC offsets:

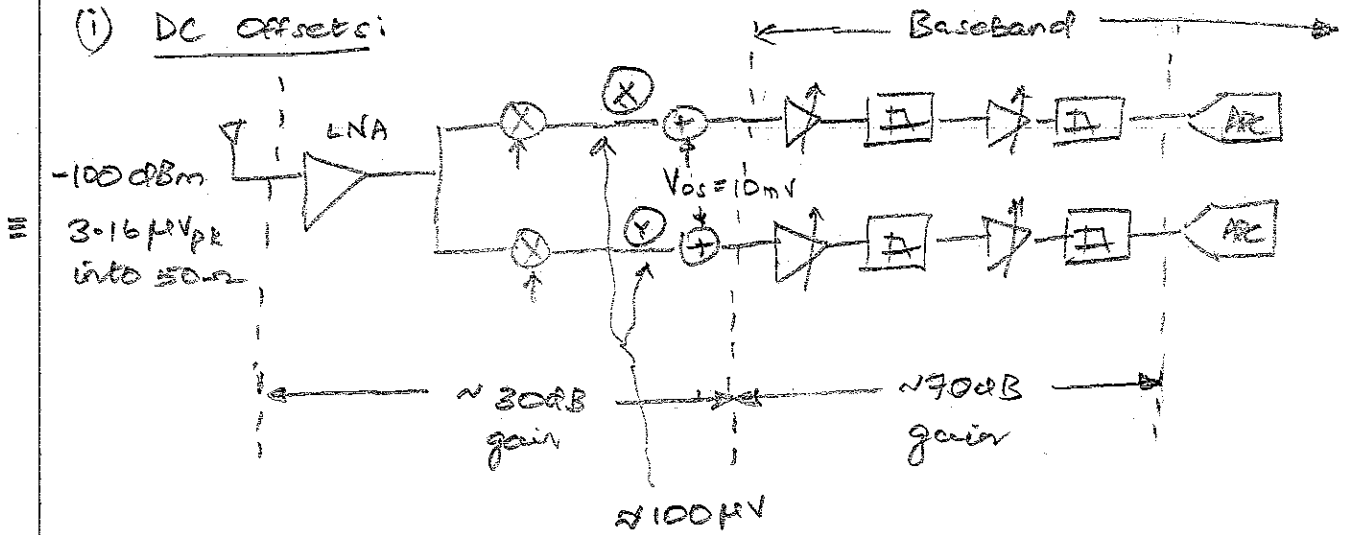


- At (X) and (Y), signal of 100 μV amplitude competes with offset of 10 mV amplitude
- Baseband circuits can have large gain (~70 dB)
- Small signal + large undesired offset at input to large gain strip ⇒ desensitization, saturation
- DC offsets can be time varying ⇒

(ii) 1/2 noise from mixer & baseband circuits  
 → same effect as time varying DC offsets.

→ Mixer 1/2 noise is main bottleneck in CMOS DCR's.

(iii) LO self-mixing:

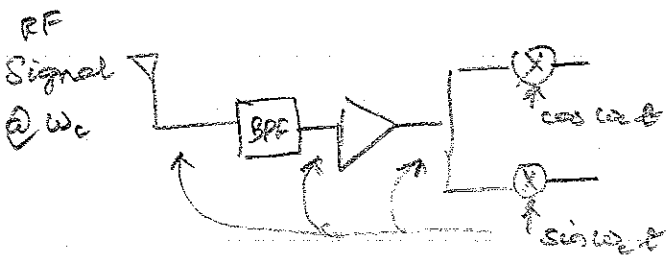

Simple model

- Suppose mixer has 60dB LO-to-RF port isolation
- ⇒ Leakage LO component @ RF port =  $E A \cos \omega_c t$

Self-mixing ⇒ Downconverted signal  
 $= A \cos \omega_c t \cdot E A \cos \omega_c t$

$$= \frac{EA^2}{2} + \frac{EA^2}{2} \cos 2\omega_c t$$


$E = \frac{1}{1000}, A = 1V \Rightarrow$  LO-self mixing component = 500μV

→ competes with 100μV RF signal

(iv) LO pulling: Suppose RF signal is large, then. Imperfect RF-to-LO port isolation causes "LO pulling", i.e., modulation on RF signal modulates LO.

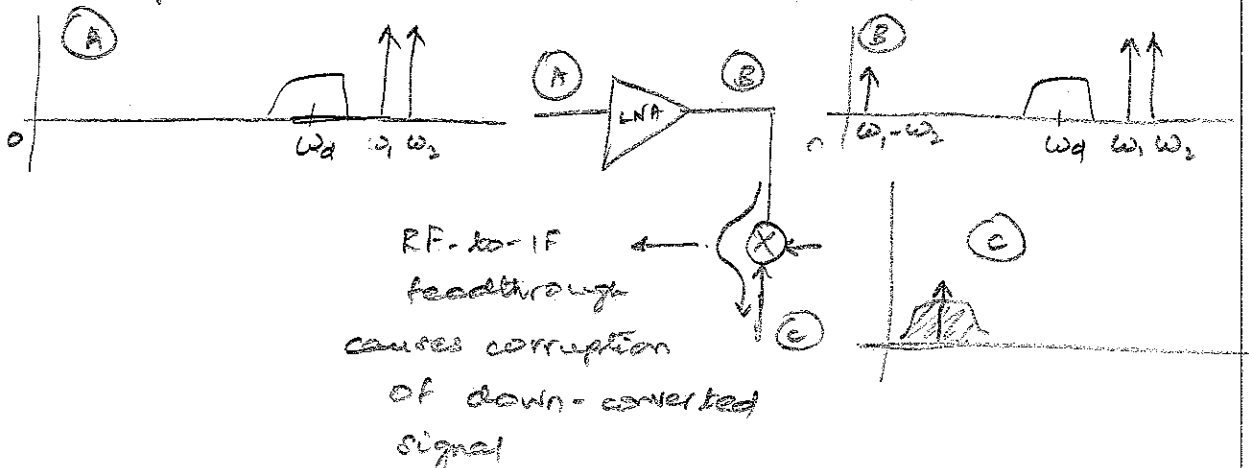(v) Even order distortion:

- LNA produces even order distortion components;




- Even order distortion in mixer's RF port has the same effect as above
- Even-order distortion in baseband circuits important.
- Even-order intermodulation specified by IIP2 (similar to IIP3).
- Differential circuits improve IIP3, but higher power dissipation


(VI) I-Q mismatch → causes higher BER.

III

Single-IF heterodyne receiver:

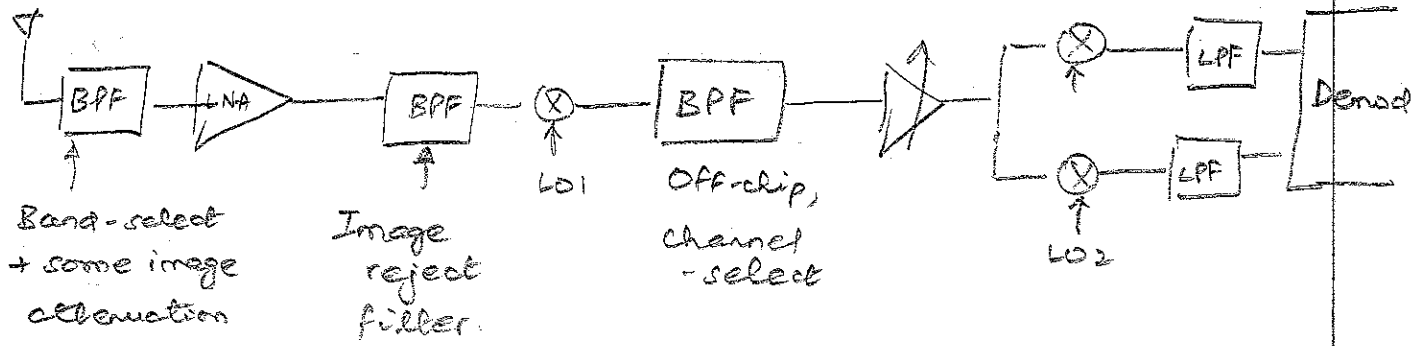

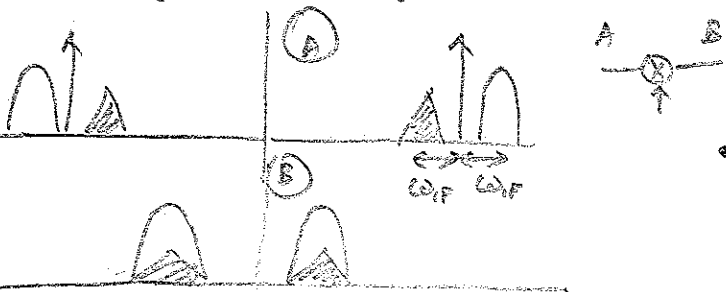- Originally developed because high gain and high selectivity were difficult to achieve at high frequencies.
- Downconvert to IF, where high gain & high selectivity are easier.
- No DC problems.
- Image frequency is a big issue!



• Image can be much larger than signal (>40dB).

## Solutions to image problem:


(i) Filtering: Filter image out before mixing

Consider an extreme example:

$$f_{RF} = 1\text{ GHz}$$

$$\text{channel BW} = 200\text{ kHz}$$

$$f_{IF} = 100\text{ kHz}$$

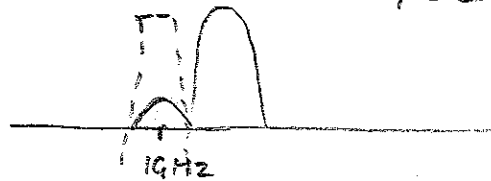

$$\text{Recall } Q = \frac{f_c}{\Delta f}$$


To get 40dB image attenuation, we need a  $Q \geq 40,000$  with a second order BPF.

— impractical on-chip or off-chip (more so because it must be tunable!)

(ii) Choose IF carefully:

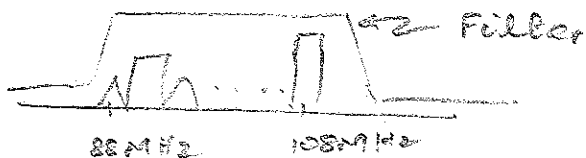Example: Broadcast FM:

$$\text{Typical } f_{IF} = 10.7\text{ MHz}$$



Worst-case  $f_{\text{image}}$  for high-side LO injection

$$= 88\text{ MHz} + 2 \times 10.7\text{ MHz} = 109.4\text{ MHz}$$

which is outside the FM frequency band  $\Rightarrow$  image channel doesn't exist.

Note: The 109.4 MHz falls in the "Aeronautical Radionavigation" band. Spectral emissions in this band are very tightly regulated.


(iii) Choose a high-IF  $\Rightarrow$  Large separation between signal & image  $\Rightarrow$  highly selective filter may not be required for image rejection

• Band select filter may provide the required image rejection

(iv) Use signal cancellation (image-reject architectures)
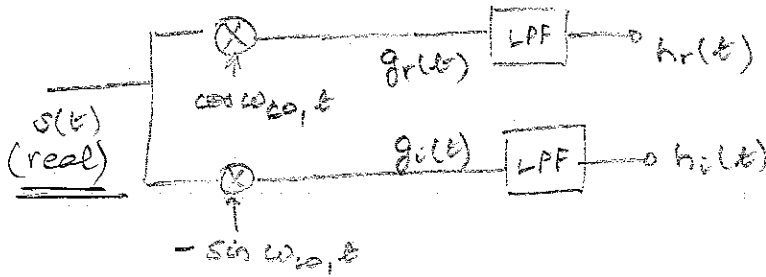
# IV Complex signal representation in receivers:

Consider a quadrature downconverting front end:



$$s(t) = \text{Re} [\tilde{s}(t) e^{j\omega_c t}]$$

$$= \frac{\tilde{s}(t) e^{j\omega_c t} + \tilde{s}^*(t) e^{-j\omega_c t}}{2}$$

$$g_r(t) = s(t) \cos \omega_c t \quad \text{and} \quad g_i(t) = -s(t) \sin \omega_c t$$

$$\Rightarrow g_r(t) + j g_i(t) = s(t) [\cos \omega_c t - j \sin \omega_c t]$$

$$\Rightarrow g(t) = s(t) e^{j\omega_c t}$$

- We can conceptually think of the pair of real signals  $\{g_r(t), g_i(t)\}$  as a complex signal.


$$\therefore g(t) = \frac{\tilde{s}(t) e^{j\omega_c t} + \tilde{s}^*(t) e^{-j\omega_c t}}{2} \cdot e^{j\omega_c t} \quad (\omega_{IF} = \omega_c - \omega_{LO})$$

$$= \frac{1}{2} \tilde{s}(t) e^{j\omega_{IF} t} + \frac{1}{2} \tilde{s}^*(t) e^{-j(\omega_c + \omega_{LO})t}$$

↑ desired complex IF term
 ↑ complex high-frequency mixing terms


subscript "d" denotes desired signal

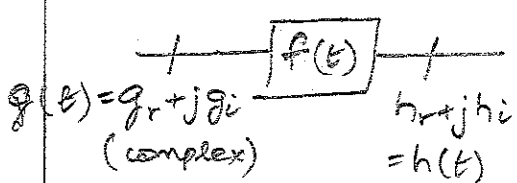- Filter off the complex H.F terms using a filter with a real-valued impulse response. How do we do this?



Convolution:  $h(t) = g(t) * f(t)$

$$= [g_r(t) + j g_i(t)] * f(t)$$

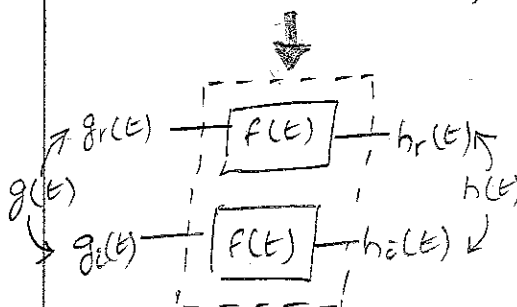


$\Rightarrow$  by linearity,

$$h(t) = \underbrace{g_r(t) * f(t)}_{h_r(t)} + j \underbrace{g_i(t) * f(t)}_{h_i(t)}$$

$\Rightarrow$  filter real & imaginary parts separately.

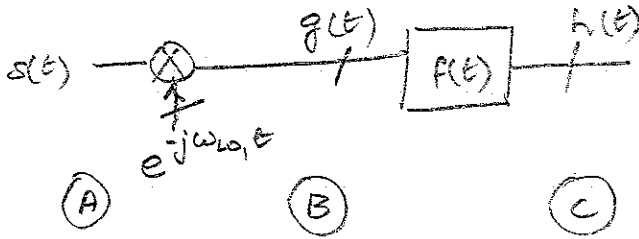
⇒ Quadrature down conversion in complex notation:



$$s(t) = \text{Re} [ \tilde{s}(t) e^{j\omega_c t} ]$$


$$g(t) = s(t) e^{-j\omega_{LO} t}$$
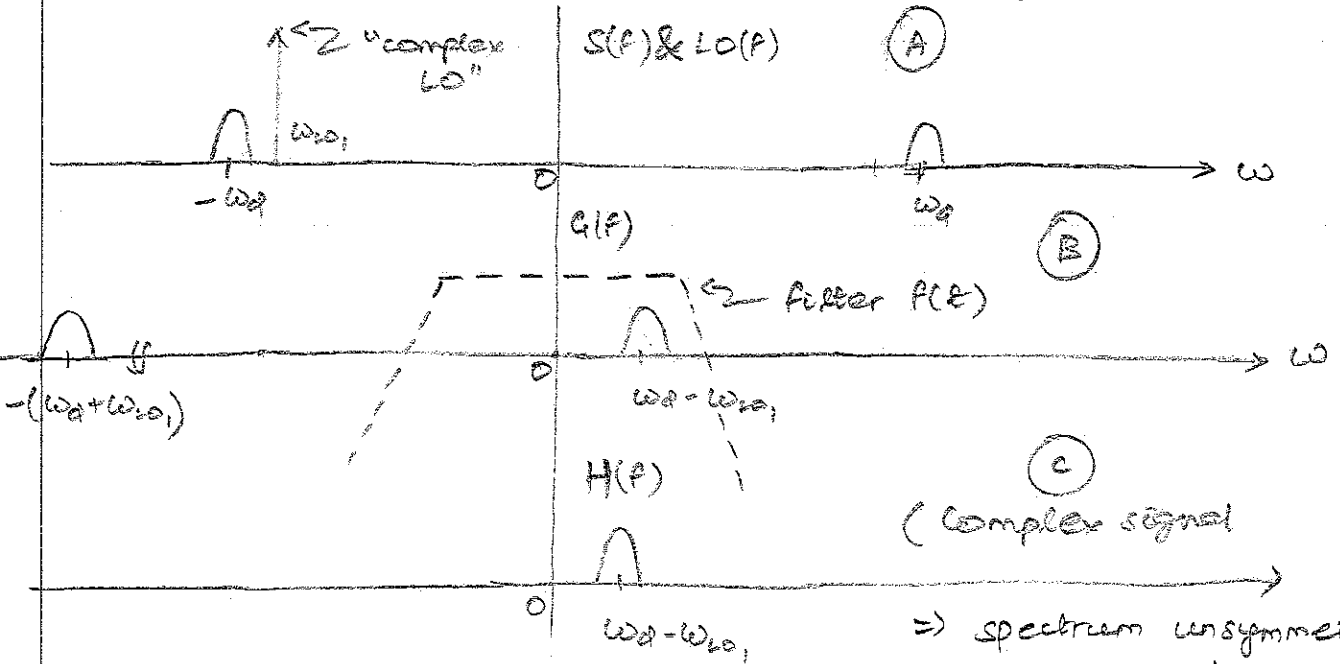
$$h(t) = \frac{1}{2} \tilde{s}(t) e^{j\omega_{IF} t}$$



⇒ spectrum unsymmetric about DC

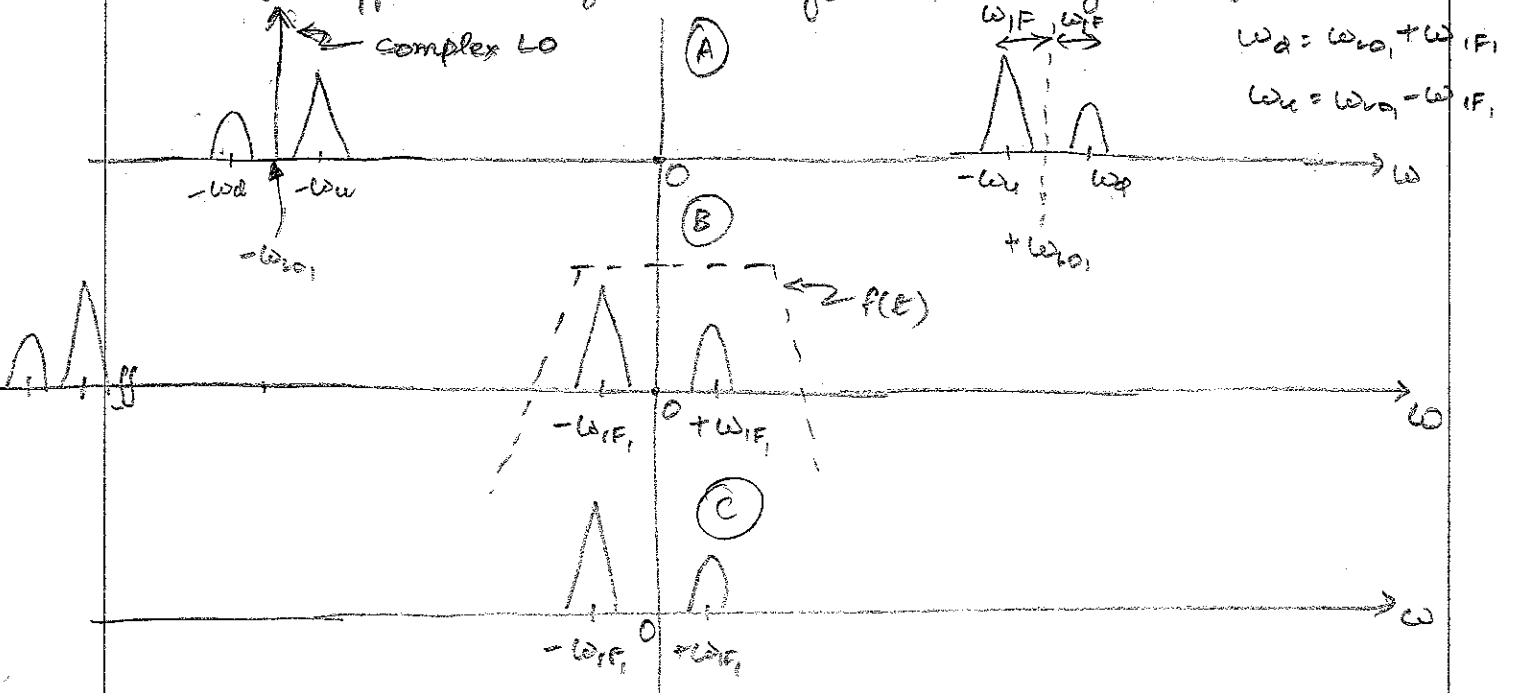• What happens if signal + image arrive together?



$$\omega_c = \omega_{LO} + \omega_{IF}$$

$$\omega_c = \omega_{LO} - \omega_{IF}$$

⇒ Signal and image are down converted to opposite sides of DC!