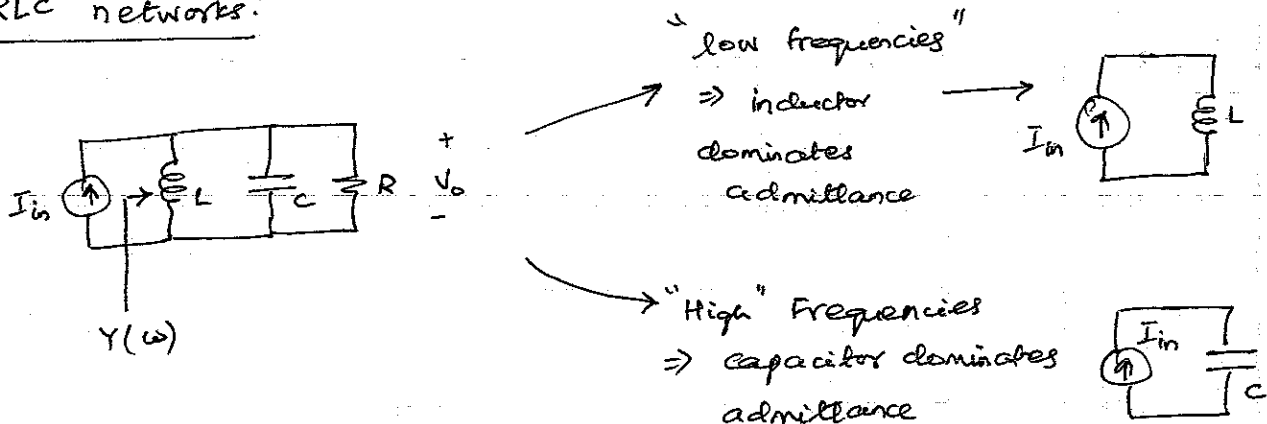


Agenda:

- Passive RLC networks (review)
  - impedance transformations
  - power matching networks
- } Ref: Lee, PP 74-87

RLC networks:




What separates "high" and "low" frequencies?  $\rightarrow$  resonance frequency

Admittance:  $Y(\omega) = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$


At resonance:  $\omega_0 C = \frac{1}{\omega_0 L} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$

Equivalent circuit @ resonance:

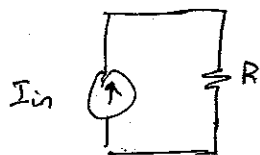

Purely resistive

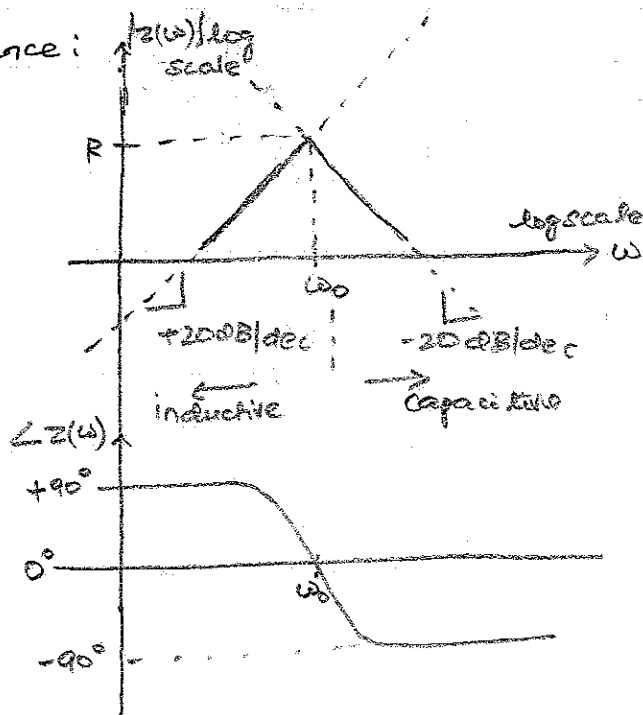Define  $Z(\omega)$  = impedance of parallel RLC tank




- At resonance  
 Magnitude  $|Z(\omega_0)| = R$   
 Phase  $\angle Z(\omega_0) = 0^\circ$

### Quality Factor Q

- Measure of how well a system stores energy

Analogy of pendulum:

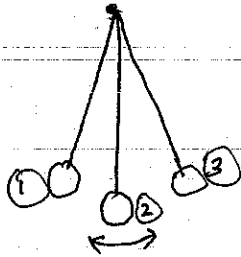

At position 2: pendulum has only kinetic energy & no potential energy

At ① and ③: pendulum has only potential energy, no kinetic energy

For a lossless pendulum:  $KE + PE = \text{constant for ever}$   
 → no dissipation


Lossy pendulum: Energy dissipates until pendulum stops oscillating.

⇒ Quality is high if energy is dissipated very slowly:

For RLC circuits (or any circuit or system for that matter)

$$Q = \omega \frac{\text{Energy stored}}{\text{Average power dissipated}}$$

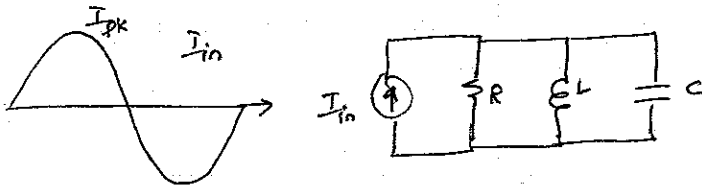RLC tank → energy sloshes between L and C with a constant sum at resonance.



When current reaches  $I_{pk}$ , voltage across capacitor (at resonance)

$$V_c = I_{pk} \cdot R$$

⇒ energy in capacitor reaches a peak at this instant & the energy in the inductor at this instant is zero.

⇒ Peak energy stored  $E_{pk} = \frac{1}{2} C V_{pk}^2 = \frac{1}{2} C (I_{pk} R)^2$

Also, at resonance, all the current from the current source flows into the resistor

$$\Rightarrow \text{Average power dissipated } P_{avg} = \frac{1}{2} I_{pk}^2 R$$

$$\Rightarrow Q = \frac{\omega_0 \cdot E_{pk}}{P_{avg}} = \frac{1}{\sqrt{LC}} \cdot \frac{1}{2} C (I_{pk} R)^2 \cdot \frac{1}{\frac{1}{2} I_{pk}^2 R} = \frac{R}{\sqrt{L/C}}$$

$\sqrt{\frac{L}{C}}$   $\rightarrow$  called characteristic impedance (analogy with transmission lines)

$$Q = \frac{R}{\sqrt{L/C}} \rightarrow \text{As } R \rightarrow \infty, Q \rightarrow \infty$$

$\Rightarrow$  intuitively correct

At resonance,

$$\left. \begin{aligned} |Z_C| &= \frac{1}{\omega_0 C} = \frac{\sqrt{LC}}{C} = \sqrt{\frac{L}{C}} \\ |Z_L| &= \omega_0 L = \frac{L}{\sqrt{LC}} = \sqrt{\frac{L}{C}} \end{aligned} \right\} \Rightarrow \text{characteristic impedance}$$

Three forms of Q for parallel RLC networks:

$$Q = \frac{R}{\sqrt{L/C}}$$

$$Q = \frac{R}{|Z_L|} = \frac{R}{\omega_0 L}$$

$$Q = \frac{R}{|Z_C|} = \omega_0 R C$$

Branch currents at resonance:

$$|I_L| = \frac{|I_{in}| R}{\omega_0 L} = Q |I_{in}|$$

$$|I_C| = |I_{in}| R \cdot \omega_0 C = Q |I_{in}|$$

Beware  $\rightarrow$  for very high Q we have very large branch currents.

$\rightarrow$  To say that the inductor and capacitor "cancel" at resonance is dangerously incorrect!

### Relationship between bandwidth and Q

→ What happens @ frequencies near resonance?

$$\omega = \omega_0 + \Delta\omega$$

$$Y(\omega) = G + j\left(\omega C - \frac{1}{\omega L}\right) = G + j\left[\frac{(\omega_0 + \Delta\omega)C}{1} - \frac{1}{(\omega_0 + \Delta\omega)L}\right]$$

$$= G + \frac{j}{(\omega_0 + \Delta\omega)L} \left[ (\omega_0 + \Delta\omega)^2 LC - 1 \right]$$

$$= G + \frac{j}{\left(1 + \frac{\Delta\omega}{\omega_0}\right)\omega_0 L} \left[ \left\{ \omega_0^2 + 2\frac{\omega_0}{\Delta\omega}\Delta\omega + (\Delta\omega)^2 \right\} LC - 1 \right]$$

$$\omega_0^2 LC = 1$$

$$\rightarrow = G + \frac{j}{\left(1 + \frac{\Delta\omega}{\omega_0}\right)\omega_0 L} \left[ 2\omega_0\Delta\omega LC + (\Delta\omega)^2 LC \right]$$

$$= G + \frac{j \Delta\omega LC}{\left(1 + \frac{\Delta\omega}{\omega_0}\right)\omega_0 L} \left[ 2\omega_0 + \Delta\omega \right]$$

$$= G + \frac{j \Delta\omega \cdot LC}{\left(1 + \frac{\Delta\omega}{\omega_0}\right)\omega_0 L} \left[ 2 + \frac{\Delta\omega}{\omega_0} \right] \cdot \omega_0$$

Use  $\frac{1}{1+x} \approx 1-x$  for  $x \ll 1$   $\left\{ \begin{aligned} &= G + j\Delta\omega \cdot C \left(1 - \frac{\Delta\omega}{\omega_0}\right) \left(2 + \frac{\Delta\omega}{\omega_0}\right) \end{aligned} \right.$


$$= G + j\Delta\omega C \left[ 2 - \frac{\Delta\omega}{\omega_0} - \left(\frac{\Delta\omega}{\omega_0}\right)^2 \right]$$

neglect  $\ll 1$

$$\Rightarrow Y(\omega) \approx G + j2\Delta\omega C$$

⇒ Equivalent circuit @ resonance → 

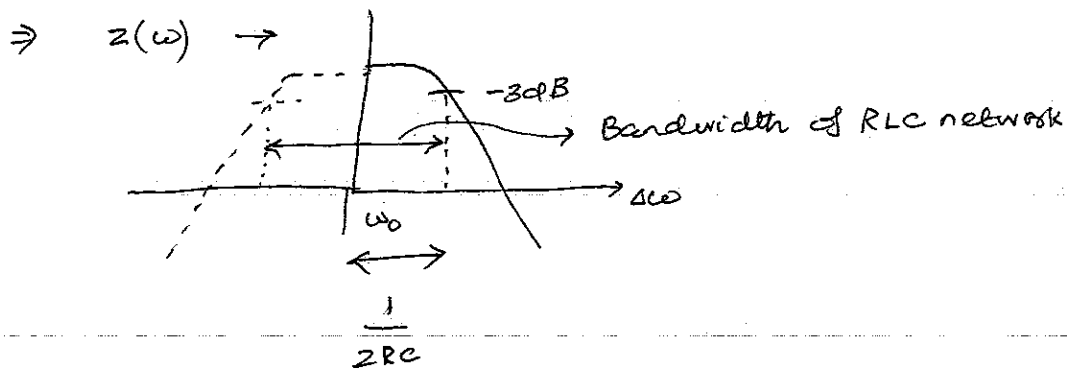Near  
→ ~~At~~ resonance, we can replace the original circuit with this equivalent circuit, and replace absolute frequency by frequency offset with respect to  $\omega_0$ .




⇒ BW of RLC network =  $2 \cdot \frac{1}{2RC} = \frac{1}{RC}$

→ Normalize w.r.t  $\omega_0 \rightarrow \frac{\Delta\omega}{\omega_0} = \frac{1/RC}{1/\sqrt{LC}} = \frac{1}{R} \cdot \sqrt{\frac{L}{C}}$


⇒  $\frac{\omega_0}{\Delta\omega} = \frac{R}{\sqrt{L/C}} = Q \Rightarrow$  higher the  $Q$ , narrower the frequency.

Series RLC network:

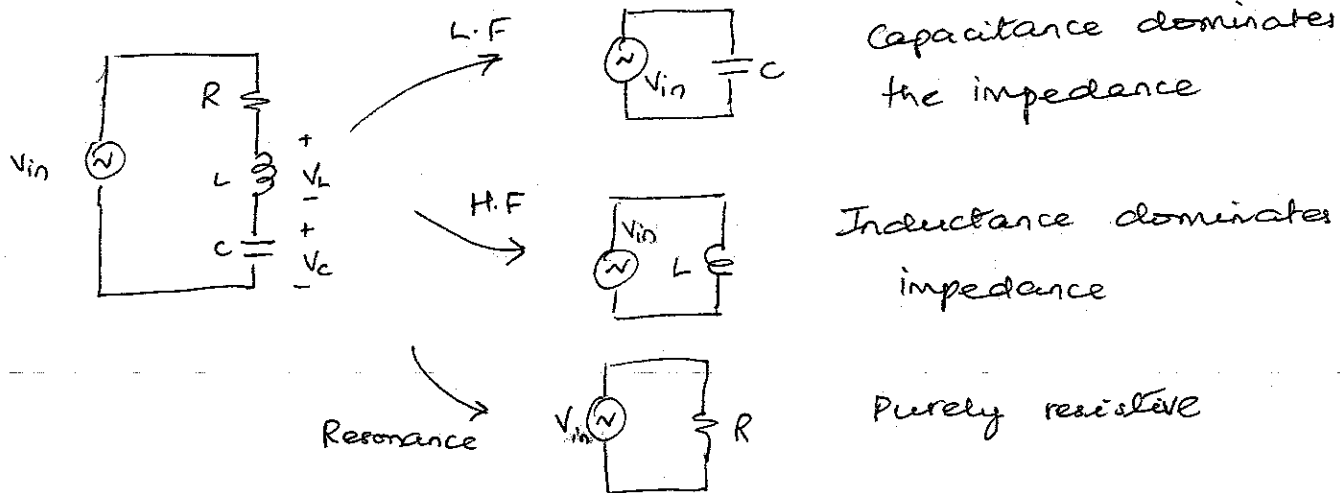

At resonance -  $V_C + V_L = 0$

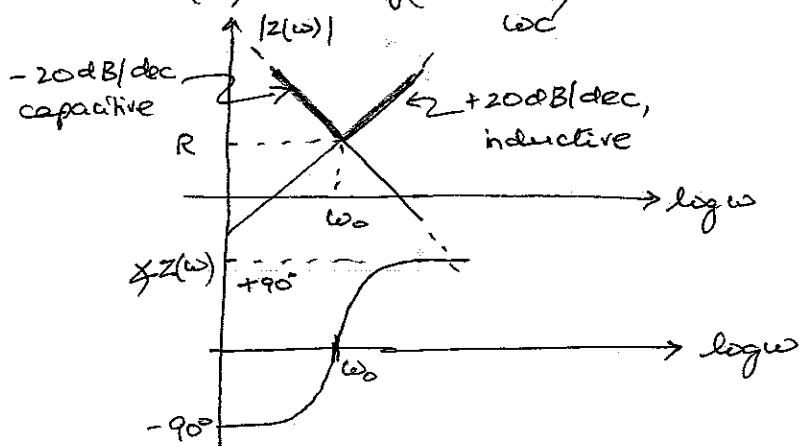$Z(\omega) = R + j(\omega L - \frac{1}{\omega C}) \rightarrow$  resonance @  $\omega_0 = \frac{1}{\sqrt{LC}}$



$$Q = \omega \cdot \frac{\text{Energy stored}}{\text{Avg. power dissipated}}$$

At resonance, when voltage reaches its peak, the current is  $I_{pk} = \frac{V_{pk}}{R} \Rightarrow$  peak magnetic energy in the inductor at this instant

& zero capacitive energy at that instant

$$\Rightarrow E_{pk} = \frac{1}{2} L I_{pk}^2 = \frac{1}{2} L \left( \frac{V_{pk}}{R} \right)^2$$

Avg. power dissipated  $P_{avg} = \frac{I_{pk}^2 R}{2} = \frac{V_{pk}^2}{2R}$

$$\Rightarrow Q = \frac{\omega_0 \cdot \frac{1}{2} \left( \frac{V_{pk}}{R} \right)^2 L}{\frac{1}{2} \frac{V_{pk}^2}{R}} = \frac{\omega_0 L}{R} = \frac{\sqrt{LC}}{R} \rightarrow \text{characteristic impedance}$$

$$Q = \frac{\sqrt{LC}}{R} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

$Q \rightarrow \infty$  as  $R \rightarrow 0$   
intuitively correct

Branch voltages at resonance:  $|V_L| = |I_{in}| \cdot \omega_0 L = \frac{|V_{in}| \omega_0 L}{R} = Q |V_{in}|$


$$|V_C| = |I_{in}| \cdot \frac{1}{\omega_0 C} = \frac{|V_{in}|}{\omega_0 RC} = Q |V_{in}|$$

$\Rightarrow$  High branch voltages at resonance  $\rightarrow$  breakdown  
 $\rightarrow$  useful for voltage amplification in LNAs.


Bandwidth near resonance

For  $\omega = \omega_0 + \Delta\omega$  for  $\Delta\omega \ll \omega_0$ :
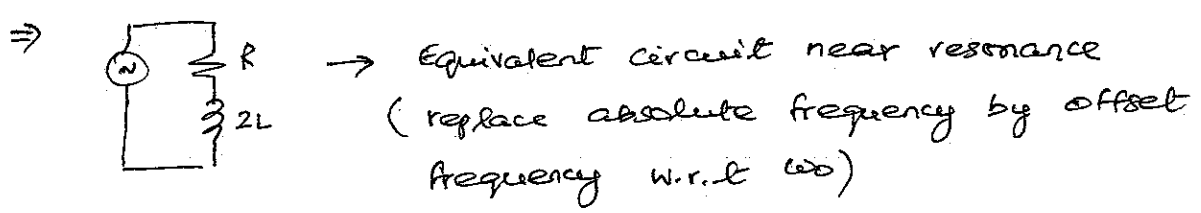
$$Z(\omega) \approx R + j2\Delta\omega L \quad (\text{PROVE THIS!})$$



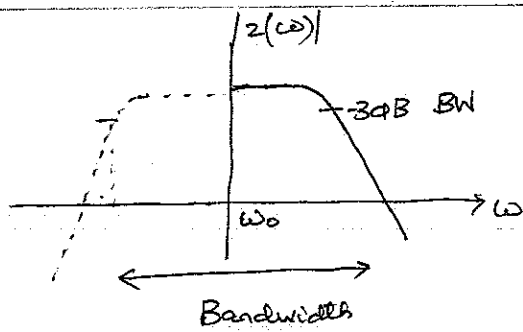3dB BW of equivalent circuit  $\approx \frac{R}{2L}$



$$BW = 2\omega_{3dB} = R/L$$


$$\text{Normalized BW} = \frac{BW}{\omega_0} = \frac{R/L}{1/\sqrt{LC}} = \frac{R}{\sqrt{L/C}} = \frac{1}{Q}$$

$$\Rightarrow Q = \frac{\omega_0}{BW} \quad \text{or} \quad \boxed{BW = \frac{\omega_0}{Q}}$$

Series-parallel transformations:

- Ubiquitous in RF design
- Can we use what we know about pure-series or pure-parallel RLC networks to analyze networks that are not pure series or parallel?
- On-chip RF circuits → inductors are a lot more lossy than capacitors

LC tank with a lossy inductor:

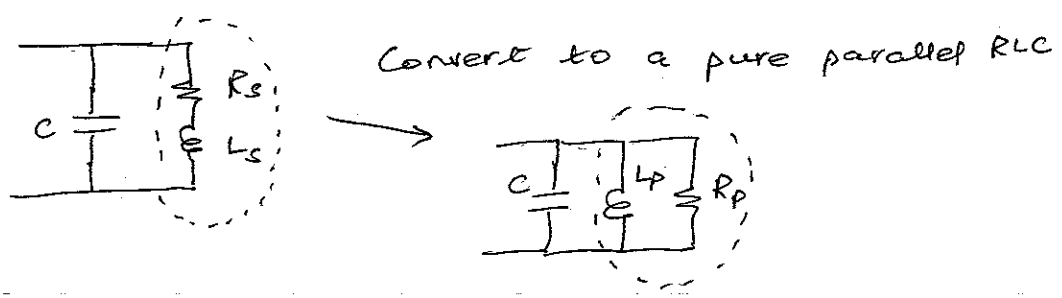

Equate impedances at resonance:

$$R_s + j\omega_0 L_s = R_p \parallel j\omega_0 L_p = \frac{R_p j\omega_0 L_p}{R_p + j\omega_0 L_p} \cdot \frac{R_p - j\omega_0 L_p}{R_p - j\omega_0 L_p}$$

$$= \frac{(\omega_0 L_p)^2 R_p + j\omega_0 L_p R_p^2}{R_p^2 + (\omega_0 L_p)^2}$$

Equate real and imaginary parts:

$$R_s = \frac{(\omega_0 L_p)^2 R_p}{R_p^2 + (\omega_0 L_p)^2} \quad \left| \quad \omega_0 L_s = \frac{\omega_0 L_p \cdot R_p^2}{R_p^2 + (\omega_0 L_p)^2}$$

Note  $Q = \frac{\omega_0 L_s}{R_s} = \frac{R_p}{\omega_0 L_p}$  ( $Q$ 's must be the same after transformation if we want the circuits to be identical)

$$R_s = \frac{R_p}{1 + \left(\frac{R_p}{\omega_0 L_p}\right)^2}$$

$$\omega_0 L_s = \frac{R_p^2 / (\omega_0 L_p)^2 \cdot (\omega_0 L_p)}{1 + \left(\frac{R_p}{\omega_0 L_p}\right)^2}$$


$$\Rightarrow R_s = \frac{R_p}{Q^2 + 1}$$

$$\Rightarrow L_s = \frac{L_p \cdot Q^2}{Q^2 + 1}$$

$$\Rightarrow R_p = (Q^2 + 1) R_s$$

$$L_p = \left(\frac{Q^2 + 1}{Q^2}\right) L_p$$

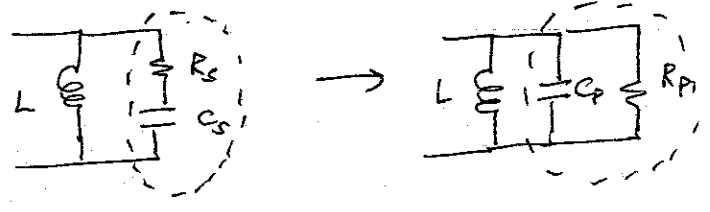Similarly, to transform series-RC to parallel-RC :



$$R_p = R_s (Q^2 + 1)$$

$$C_p = \frac{Q^2}{Q^2 + 1} C_s$$

Generally:


$$R_p = R_s (Q^2 + 1)$$

$$X_p = X_s \left(\frac{Q^2 + 1}{Q^2}\right)$$

$$Q = \frac{X_s}{R_s} = \frac{R_p}{X_p}$$

Note that these transformations holds only in a narrow band centered about  $\omega_0$ .

## The Maximum power transfer theorem:

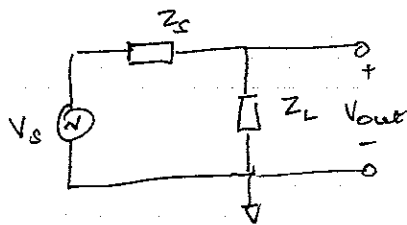

Suppose that we have a source with a source impedance  $Z_s$ , at what value of load impedance will maximum (real) power be delivered to the load?

$$\rightarrow \boxed{Z_L = Z_s^*} \text{ (complex conjugate)}$$

$$\text{or } \begin{cases} R_L = R_s \\ X_L = -X_s \end{cases}$$

called a conjugate match. Other types of "matchers" are reflection matching and noise matching.

Derivation (good refresher in basics!)

Power delivered to load  $P_L = \frac{1}{2} \operatorname{Re}[V_L I_L^*]$  (peak phasors!)

$$V_L = \frac{Z_L}{Z_L + Z_s} V_s, \quad I_L = \frac{V_s}{Z_L + Z_s}$$

$$\therefore P_L = \frac{1}{2} \operatorname{Re} \left[ \frac{Z_L}{Z_L + Z_s} V_s \cdot \frac{V_s^*}{(Z_L + Z_s)^*} \right] = \frac{|V_s|^2}{2|Z_L + Z_s|^2} \cdot \operatorname{Re}(Z_L)$$

$$\Re P_L = \frac{|V_s|^2 R_L}{2|Z_L + Z_s|^2} = \frac{|V_s|^2 R_L}{2[(R_L + R_s)^2 + (X_L + X_s)^2]}$$

Note that the source impedance is fixed & we are allowed to vary only the load impedance.

For maximum power,  $\frac{\partial P_L}{\partial X_L} = 0$  and  $\frac{\partial P_L}{\partial R_L} = 0$

$$\frac{\partial P_L}{\partial X_L} = \frac{|V_s|^2}{2} \cdot \frac{(R_L)[-2(X_L + X_s)]}{[(R_L + R_s)^2 + (X_L + X_s)^2]^2} = 0 \Rightarrow X_L + X_s = 0$$

$$\text{or } \boxed{X_L = -X_s}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{|V_s|^2}{2} \left[ \frac{1}{(R_L + R_s)^2 + (X_L + X_s)^2} - \frac{2R_L(R_L + R_s)}{\{(R_L + R_s)^2 + (X_L + X_s)^2\}^2} \right] = 0$$

$$\Rightarrow (R_L + R_s)^2 + \underbrace{(X_L + X_s)^2}_{=0} = 2R_L(R_L + R_s)$$

since  $X_L = -X_s$


$$\therefore R_L + R_s = 2R_L \quad \text{or} \quad \boxed{R_L = R_s}$$

The power delivered to the load when  $Z_L = Z_s^*$  is defined as the "available" power from a source.

$$P_{avs} = P_{Lmax} = \frac{|V_s|^2}{8R_s}$$

RLC Networks as impedance transformers:

1) Upward transformation:

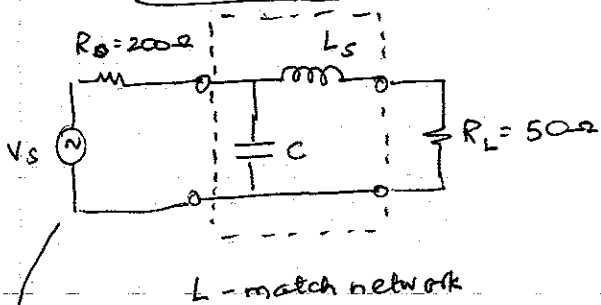

- Find  $L_s$  and  $C$  to match the load to the source at 5GHz

• Series-to-parallel transformation:

Suppose  $L_p$  &  $C$  resonate at 5GHz,

then  $R_p = 200 \Omega$  @ 5GHz

$$R_p = R_L(Q^2 + 1)$$


$$R_L = 50 \Omega, R_p = 200 \Omega \Rightarrow Q = \sqrt{\frac{R_p}{R_L} - 1}$$

$$\text{or } Q = \sqrt{3} = 1.732$$

$$\text{But } Q = \frac{\omega L_s}{R_L} = \frac{R_p}{\omega L_p} \Rightarrow L_s = \frac{Q \cdot R_L}{\omega} = \frac{\sqrt{3} \cdot 50}{2\pi \cdot 5\text{GHz}}$$

$$\text{or } \boxed{L_s = 2.75 \text{ nH}}$$

(A)

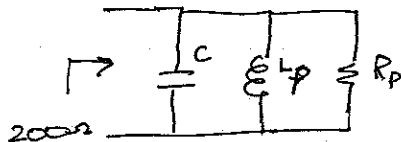

$$\therefore L_p = \frac{R_p}{\omega_0 Q} = \frac{200}{2\pi \cdot 59\text{Hz} \cdot \sqrt{3}} = 3.68\text{nH}$$

(Alternatively, we can use the formula  $L_p = \frac{L_s (Q^2 + 1)}{Q^2}$ )


Finally,  $L_p$  &  $C$  must resonate at 59Hz

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{L_p C}} = \frac{1}{\sqrt{3.66\text{nH} \cdot C}} = 2\pi \cdot 59\text{Hz}$$

or  $C = 276.83\text{fF}$  ←

This network has a low pass response from the source to the load. We can design another network with a high pass response:

(B)

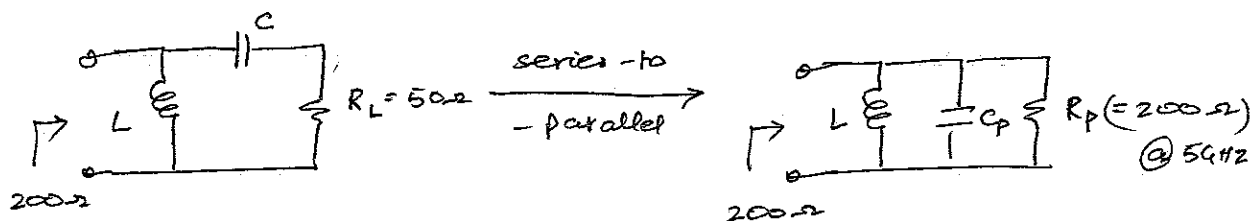

$$R_p = R_L (Q^2 + 1) \Rightarrow Q = \sqrt{\frac{R_p}{R_L} - 1} = \sqrt{3}$$

$$Q = \frac{1}{\omega_0 R_L C} \Rightarrow C = \frac{1}{\omega_0 R_L Q} = \frac{1}{2\pi \cdot 59\text{Hz} \cdot 50 \cdot \sqrt{3}}$$

or  $C = 367.55\text{fF}$  ←

$$C_p = C \cdot \frac{Q^2}{Q^2 + 1} = 275.66\text{fF}$$

We want  $L$  and  $C_p$  to reach resonance @ 59Hz

$\Rightarrow L = \frac{1}{\omega_0^2 C_p} = 3.67\text{nH}$  ←

Which network to choose (A) or (B)?


- High-pass vs. Low pass response
- Usually want the network with the smallest inductor (larger inductors have more loss and area)
- Parasitics

Bandwidth: Match exact only at 5GHz. At other frequencies, we will have an impedance mismatch.

Basic microwave theory: if an impedance mismatch causes power to be "reflected" back to the source


Mismatch quantified by reflection coefficient ( $= S_{11}$  for a 1-port network)
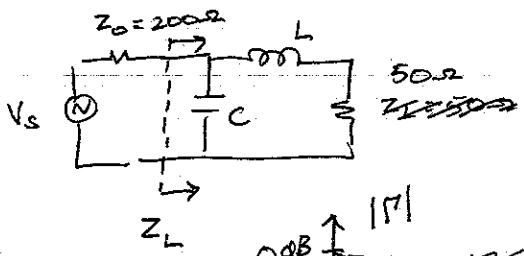
$$S_{11} = \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$



Rule-of-thumb  $|\Gamma| \sim -10\text{dB}$

is generally a good number.

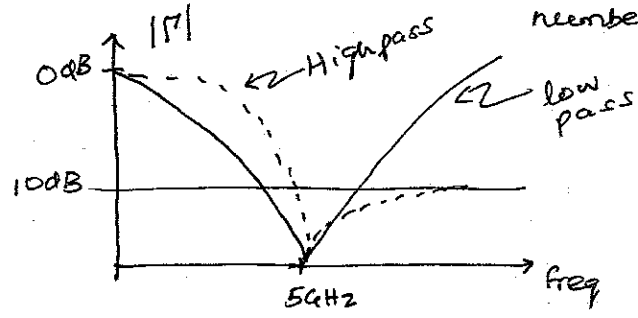


Note: For a mismatch  $|\Gamma|$  between the load & source impedances, the power delivered to the load is

$$P_L = P_{av}(1 - |\Gamma|^2) \text{ when source impedance is real.}$$


↑ "available power" from source.

2) Downward transformation

Match @ 5GHz

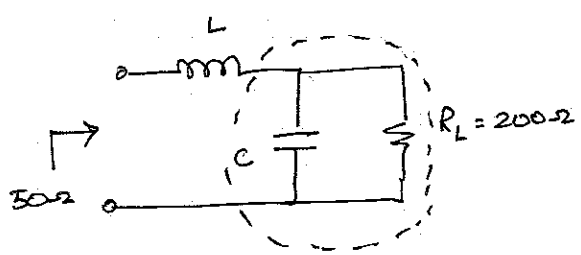

Parallel-to-series transformation

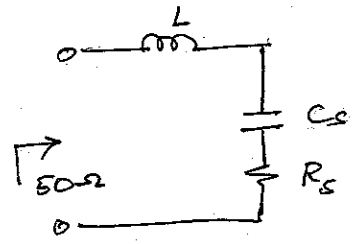

If we resonate  $L$  &  $C_s$  @ 5GHz, then  $R_s = 50\Omega$  @ 5GHz

$$R_s = \frac{R_p}{Q^2 + 1} \Rightarrow Q = \sqrt{\frac{R_p}{R_s} - 1} = \sqrt{3}$$

$$Q = \frac{1}{\omega_0 R_s C_s}$$

$$\Rightarrow C_s = \frac{1}{2\pi \cdot 5\text{GHz} \cdot 50 \cdot \sqrt{3}} = 367.55\text{fF}$$

$$C_s = C_0 \left( \frac{Q^2 + 1}{Q^2} \right) \Rightarrow C = C_0 \left( \frac{Q^2}{Q^2 + 1} \right) = \frac{(\sqrt{3})^2}{(\sqrt{3})^2 + 1} \cdot 367.5 \text{ pF}$$

or  $C = 275.5 \text{ pF}$  ←


Since L and C<sub>s</sub> resonate @ 5GHz,

$$\omega_0^2 = \frac{1}{LC_s} \Rightarrow L = \frac{1}{(2\pi \times 5 \text{ GHz})^2 (367.55 \text{ pF})} = 2.75 \text{ nH}$$


or  $L = 2.75 \text{ nH}$  ←

(Not surprisingly, the values are the same as the upward transformation case looking backwards)

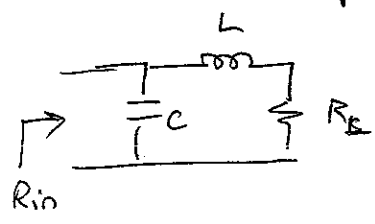Mnemonic: How to find if an L-match network gives an upward or downward transformation?



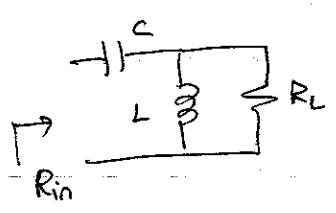← since we add L in series, we expect  $R_{in} > R_L \Rightarrow$  upward tr.



← add "something" (i.e., L here) in parallel  $\Rightarrow R_{in} < R_L \Rightarrow$  downward transformation