
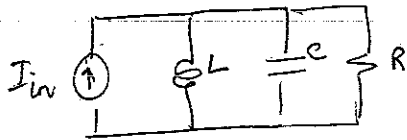


Parallel RLC tank

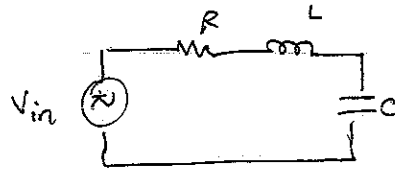

Series RLC tank



Resonant Frequency $\omega_0 = \frac{1}{\sqrt{LC}}$

characteristic Impedance $Z_0 = \sqrt{\frac{L}{C}}$

$Q = \omega \frac{\text{Energy stored}}{\text{Power Dissipated}}$

$$\begin{aligned}
 Q &= \frac{R}{\sqrt{L/C}} \\
 &= \frac{R}{\omega_0 L} \\
 &= \omega_0 RC \\
 &= \frac{\omega_0}{\Delta\omega_{-3dB}}
 \end{aligned}$$

$$\begin{aligned}
 Q &= \frac{\sqrt{L/C}}{R} \\
 &= \frac{\omega_0 L}{R} \\
 &= \frac{1}{\omega_0 RC} \\
 &= \frac{\omega_0}{\Delta\omega_{-3dB}}
 \end{aligned}$$

At $\omega = \omega_0$ $|Z_C| = |Z_L| = \sqrt{\frac{L}{C}}$

$|Z_C| = |Z_L| = \sqrt{\frac{L}{C}}$

$|I_C| = |I_L| = Q |I_{in}|$

$|V_C| = |V_L| = Q |V_{in}|$

Series - Parallel conversions (Narrowband only)




$Q_s = Q_p = Q$

$R_p = R_s (1 + Q^2)$

$X_p = X_s \left(\frac{Q^2 + 1}{Q^2} \right)$

Lowpass L-match (Upward transformation)

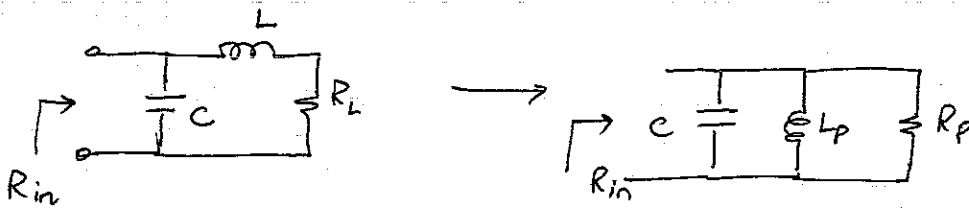

At $\omega = \omega_0$


$$1) \quad R_p = R_{in} = R_L (\mathcal{Q}^2 + 1) \Rightarrow \mathcal{Q} = \sqrt{\frac{R_{in}}{R_L} - 1}$$

$$2) \quad \mathcal{Q}_p = \mathcal{Q} = \frac{R_p}{\omega_0 L_p} \Rightarrow L_p = \frac{R_{in}}{\mathcal{Q} \omega_0}$$

$$3) \quad L_p = \left(\frac{\mathcal{Q}^2 + 1}{\mathcal{Q}^2} \right) L \Rightarrow L = \left(\frac{\mathcal{Q}^2}{\mathcal{Q}^2 + 1} \right) L_p$$

$$4) \quad \omega_0 = \frac{1}{\sqrt{L_p C}} \Rightarrow C = \frac{1}{\omega_0^2 L_p}$$

Highpass ^{upward} transformation:

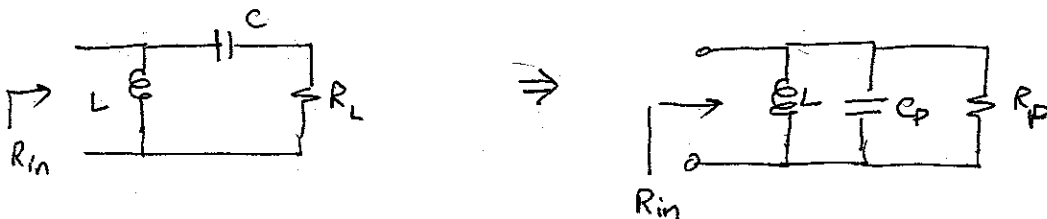

MNEMONIC

Add "something" in series with load \Rightarrow upward transform.

At $\omega = \omega_0$

$$1) \quad R_p = R_L (\mathcal{Q}^2 + 1) \Rightarrow \mathcal{Q} = \sqrt{\frac{R_p}{R_L} - 1}$$


$$2) \quad \mathcal{Q} = \omega_0 R_p C_p \Rightarrow C_p = \frac{\mathcal{Q}}{\omega_0 R_p}$$

$$3) \quad C_p = \frac{\mathcal{Q}^2}{\mathcal{Q}^2 + 1} C \Rightarrow C = \frac{\mathcal{Q}^2 + 1}{\mathcal{Q}^2} C_p$$

$$4) \quad \omega_0 = \frac{1}{\sqrt{L C_p}} \Rightarrow L = \frac{1}{\omega_0^2 C_p}$$

L-match Downward Transformation

(a) Lowpass:

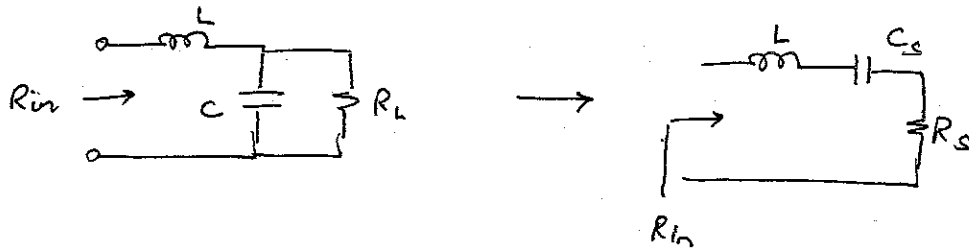

At $\omega = \omega_0$


$$1) \quad R_S = R_{in} = \frac{R_L}{Q^2 + 1} \Rightarrow Q = \sqrt{\frac{R_L}{R_{in}} - 1}$$

$$2) \quad Q = \frac{1}{\omega_0 R_S C_S} \Rightarrow C_S = \frac{1}{\omega_0 R_{in} Q}$$

$$3) \quad C_S = \left(\frac{Q^2 + 1}{Q^2}\right) C \Rightarrow C = \left(\frac{Q^2}{Q^2 + 1}\right) C_S$$

$$4) \quad \omega_0 = \frac{1}{\sqrt{L C_S}} \Rightarrow L = \frac{1}{\omega_0^2 C_S}$$

(b) Highpass:

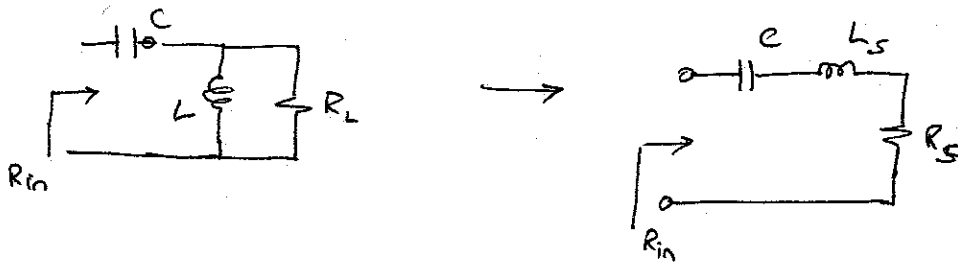

At $\omega = \omega_0$

$$1) \quad R_S = R_{in} = \frac{R_L}{Q^2 + 1} \Rightarrow Q = \sqrt{\frac{R_L}{R_{in}} - 1}$$

$$2) \quad Q = \frac{\omega_0 L_S}{R_S} \Rightarrow L_S = \frac{Q R_S}{\omega_0}$$

$$3) \quad L_S = \frac{Q^2}{Q^2 + 1} L \Rightarrow L = \left(\frac{Q^2 + 1}{Q^2}\right) L_S$$

$$4) \quad \omega_0 = \frac{1}{\sqrt{L_S C}} \Rightarrow C = \frac{1}{\omega_0^2 L_S}$$


Limitations of L-matching networks

- Only 2 degrees of freedom L & C
- We know $R_{in}, R_L \Rightarrow Q$ is fixed. (usually the case)
- Among $\omega_0, \frac{R_{in}}{R_L}$ and Q , we can specify only 2 of 3 parameters


To add a 3rd degree of freedom, add one extra element

- Π -match
- T -match

Π -Match :

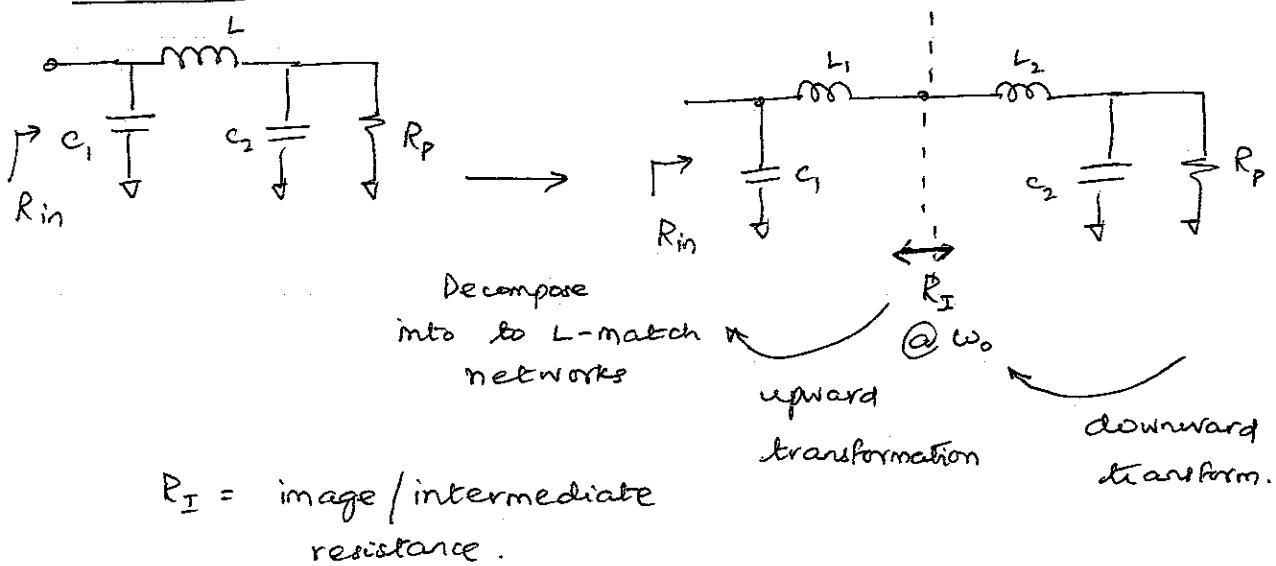


→ For the right-hand section:

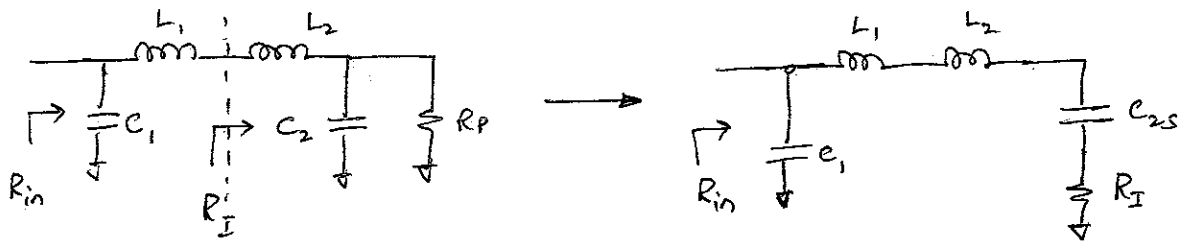

$$Q_{right} = \sqrt{\frac{R_P}{R_I} - 1} = \frac{\omega_0 L_2}{R_I}$$

→ Left-hand section:

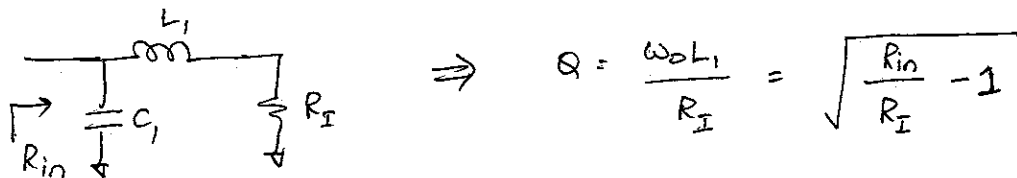

$$\text{Overall } Q = Q_{\text{left}} + Q_{\text{right}}$$

$$\Rightarrow Q = \frac{\omega_0 L_1}{R_I} + \frac{\omega_0 L_2}{R_I} = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_P}{R_I} - 1}$$

Design procedure — Given R_P , R_{in} , Q and ω_0

- Use the above equation for Q and solve for R_I (iterative)
- Design the right-hand section as a downward L-match from R_P to R_I
- Design the left-hand section as an upward match from R_I to R_{in}

Example: Match $R_P = 200\Omega$ to $R_{in} = 50\Omega$ @ $\omega_0 = 5\text{GHz}$
with $Q = 10$

$$Q = 10 = \sqrt{\frac{50}{R_I} - 1} + \sqrt{\frac{200}{R_I} - 1}$$

Iterate: Start with $R_I = 10\Omega \Rightarrow Q = 6.35 (\neq 10)$

$$R_I = 5\Omega \Rightarrow Q = 9.24$$

$$R_I = \text{~~10~~ } 4.3\Omega$$

$$Q_{\text{right}} = \sqrt{\frac{R_P}{R_I} - 1} = 6.75$$



$$Q_{\text{left}} = \sqrt{\frac{R_{in}}{R_I} - 1} = 3.26$$

$$Q_{\text{right}} = \frac{\omega_0 L_2}{R_I} \Rightarrow L_2 = 0.923\text{nH}$$

$$Q_{\text{left}} = \frac{\omega_0 L_1}{R_I} \Rightarrow L_1 = 0.446\text{nH}$$


$$L = 1.37\text{nH}$$

LHS:

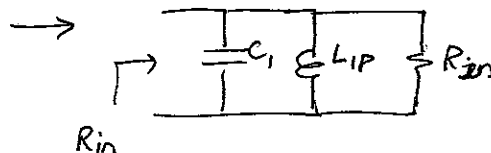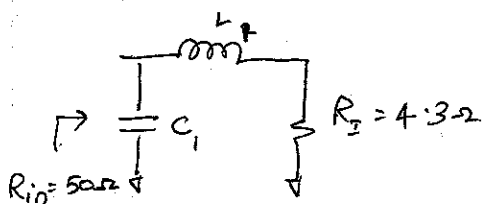

$$L_{1P} = \left(\frac{Q_{left}^2 + 1}{Q_{left}^2} \right) L_1 = 0.488 \text{ nH} \Rightarrow \boxed{C_1 = \frac{1}{\omega_0^2 L_{1P}} = 2.07 \text{ pF}}$$

RHS:

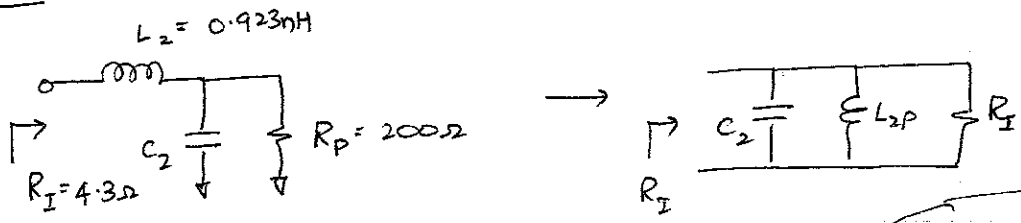


$$L_{2P} = L_2 \left(\frac{Q_{right}^2 + 1}{Q_{right}^2} \right) = 0.943 \text{ nH}$$

$$\Rightarrow \boxed{C_2 = \frac{1}{\omega_0^2 L_{2P}} = 1.074 \text{ pF}}$$

Advantage of lowpass pi-network
 → shunt caps. to ground
 ⇒ absorb parasitics

Generalized Π -matching network:

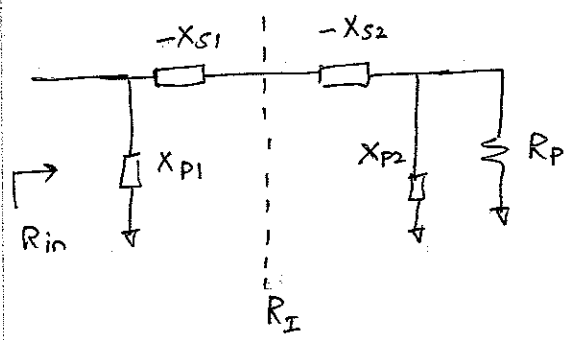

General idea:

- Once we use $Q = \sqrt{\frac{R_p}{R_I} - 1} + \sqrt{\frac{R_{in}}{R_2} - 1}$ to find R_I , the problem boils down to the design of two separate L-match networks.
- For each L-match, we only require that the two reactive elements be of opposite sign.
- Four combinations:

RHS	LHS	Σ
LP	LP	
LP	HP	
HP	LP	
HP	HP	

A practical note: In many amateur radio designer resources, you will find a different INACCURATE procedure for Π -match design.

Here, Q is defined as $Q = \sqrt{\frac{R_H}{R_L} - 1}$ where $R_H = \max(R_{in}, R_P)$

Using this definition,

For our previous example where $R_P = 200\Omega$ & $R_{in} = 50\Omega$,

$$Q = \sqrt{\frac{200}{50} - 1} = 10 \Rightarrow R_L = 1.98\Omega$$


Since the right-hand section contains R_H (the larger value),

$$Q_{right} = Q = \omega_0 R_P C_2$$


$$\Rightarrow C_2 = 1.59 \text{ pF}$$

$$\text{and } L_2 = \frac{R_L}{\omega_0^2 (Q_{right}^2 + 1) C_2}$$

$$L_2 = 0.63 \text{ nH}$$

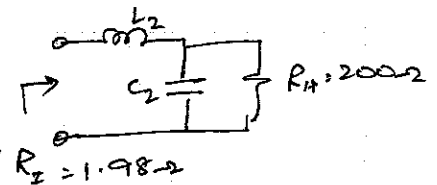

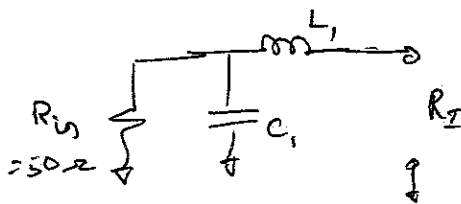For the left-hand section, calculate Q as you would in an upward L-match:




$$Q_{left} = \sqrt{\frac{R_H}{R_L} - 1} = 4.92$$

$$\Rightarrow L_1 = Q_{left} \frac{\omega_0 L}{R_L}$$

$$\Rightarrow L_1 = 0.31 \text{ nH}$$


$$\text{and } C_1 = 3.13 \text{ pF}$$

The Π -match is then:

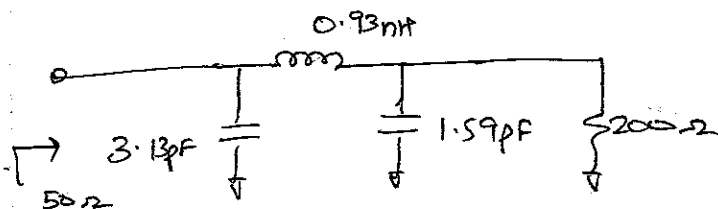

Notice how different these values are from the ones that we calculated previously.

T-match

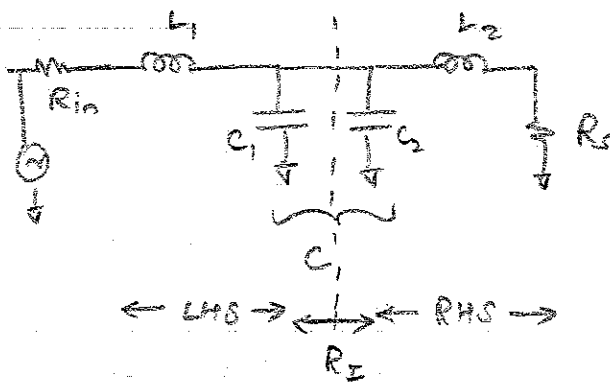


• Usually, we are given R_L , R_{in} , ω_0 and Q

• Split the center cap. C into C_1 and C_2 , so that we have two L-match sections

• RHS \rightarrow transforms R_L UP to R_I (the image resistance)


LHS \rightarrow transforms R_I DOWN to R_{in}

• What is R_I ?

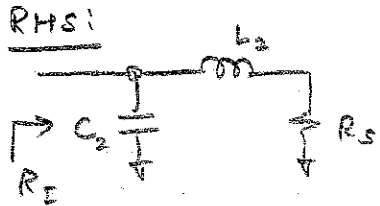

$$Q_{right} = \omega_0 R_L C_2$$

$$= \sqrt{\frac{R_I}{R_L} - 1}$$

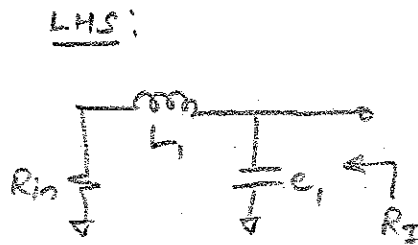

$$Q_{left} = \omega_0 R_I C_1$$

$$= \sqrt{\frac{R_L}{R_{in}} - 1}$$

Overall $Q = Q_{left} + Q_{right}$ (remember Q is specified to us)

• Find R_I by solving

$$Q = \sqrt{\frac{R_I}{R_L} - 1} + \sqrt{\frac{R_L}{R_{in}} - 1} \quad (\text{usually solved iteratively})$$


• Use $Q = \omega_0 R_I (C_1 + C_2) \Rightarrow C = C_1 + C_2 = \frac{Q}{\omega_0 R_I}$

• Find $Q_{right} = \sqrt{\frac{R_I}{R_L} - 1}$ and $Q_{left} = \sqrt{\frac{R_L}{R_{in}} - 1}$

• $Q_{right} = \frac{\omega_0 L_2}{R_L}$ and $Q_{left} = \omega_0 L_1 / R_{in}$


$\Rightarrow L_2 = \frac{Q_{right} R_L}{\omega_0}$ and $\Rightarrow L_1 = \frac{Q_{left} R_{in}}{\omega_0}$

Tapped - capacitor match:

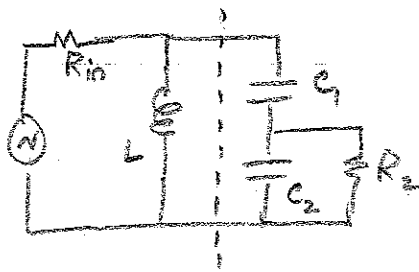

• As in Π - and T -matching networks, we can set $\frac{R_{in}}{R_2}$ (the transformation ratio), Q and ω_0 independently.

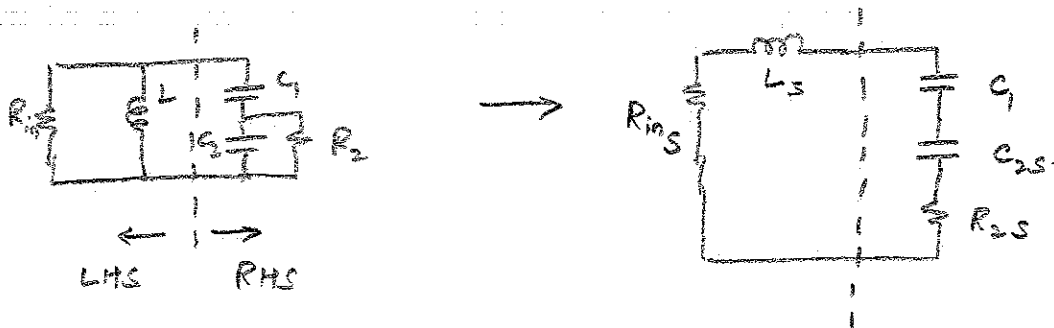• To design, we again use series-parallel transformations:



LHS Overall $Q = \frac{R_{in}}{\omega_0 L} \Rightarrow \boxed{L = \frac{R_{in}}{\omega_0 Q}}$

$$R_{in_s} = \frac{R_{in}}{Q^2 + 1} \quad \text{and} \quad L_s = \frac{Q^2}{Q^2 + 1} L$$

RHS: $R_{2_s} = \frac{R_2}{Q_2^2 + 1}$ ($Q_2 =$ quality factor of R_2 - C_2 parallel network)

For match, we want $R_{in_s} = R_{2_s}$

$$\Rightarrow \frac{R_{in}}{Q^2 + 1} = \frac{R_2}{Q_2^2 + 1} \Rightarrow$$

$$\boxed{Q_2 = \sqrt{\frac{R_2}{R_{in}} (Q^2 + 1) - 1}}$$

But $Q_2 = \omega_0 R_2 C_2$

$$\Rightarrow \boxed{C_2 = \frac{Q_2}{\omega_0 R_2}}$$

To find C_1 : the equivalent cap. of the C_1 - C_{2_s} series combination

$$\text{is } C_{eq} = \frac{C_1 C_{2_s}}{C_1 + C_{2_s}}$$

But $Q = \frac{1}{\omega_0 R_{2_s} C_{eq}} \Rightarrow$ After some algebra

$$\boxed{C_1 = \frac{C_2 (Q_2^2 + 1)}{Q Q_2 - Q_2^2}}$$