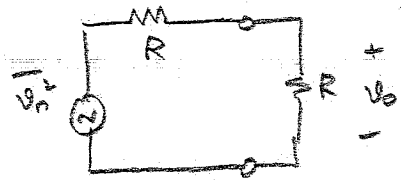


Available noise power: = maximum noise power that can be delivered to a load.



⇒ conjugate match

Power delivered to load resistor } = $\frac{(\overline{V_n}/2)^2}{R} = \frac{\overline{V_n^2}}{4R}$ (W/Hz)
in a 1-Hz BW

⇒ $P_{avn} = \frac{4kTR}{4R} \cdot B = kTB$ Watts.

- Available noise power independent of resistance
- proportional to absolute temperature
- proportional to bandwidth.

⇒ For low noise, keep minimum BW and temp. possible.


Available noise power per unit BW = kT W/Hz

$P_{avn}/\text{Hz} = 4.143 \times 10^{-21}$ W/Hz
= -174 dBm /Hz

Worst case

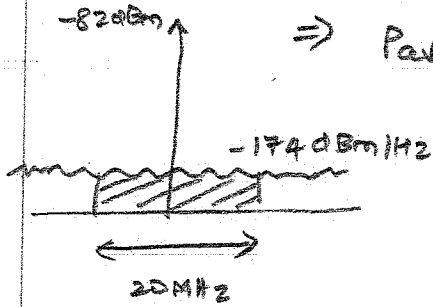802.11a : Received signal power = -82 dBm @ 20MHz BW

⇒ $P_{avn} = 4.143 \times 10^{-21} \frac{W}{Hz} \times 20\text{MHz} = 8.29 \times 10^{-14} W$



or $P_{avn} = -100 \text{ dBm}$

⇒ Max. possible SNR = -82 dBm - (-100 dBm)
= 18 dBm

- This is the best we can do with a 20MHz BW at room temperature ⇒ ideal receiver
- A real receiver will add noise of its own.

• With $P_{avn} = -100 \text{ dBm}$, the rms noise voltage across a 50Ω resistor is $\overline{V_n} = 2.23 \mu V$.

If we applied a sine-wave signal with this amplitude to an oscilloscope, we would barely be able to see it ⇒ called MINIMUM DETECTABLE SIGNAL


② Noise in MOSFETs:

④

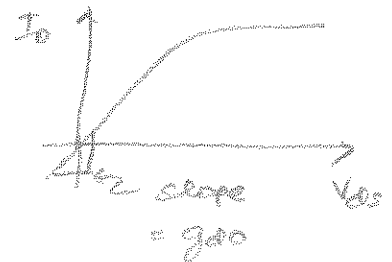A) Thermal noise

Case (i) MOSFET as resistor (triode region)


$$I_d = K_n' \left(\frac{W}{L} \right) \left[(V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right] \rightarrow$$



$$g_d = \frac{\partial I_d}{\partial V_{ds}} = K_n' \left(\frac{W}{L} \right) (V_{gs} - V_t - V_{ds})$$

$$\Rightarrow \boxed{g_{do} = K_n' \left(\frac{W}{L} \right) (V_{gs} - V_t)}$$

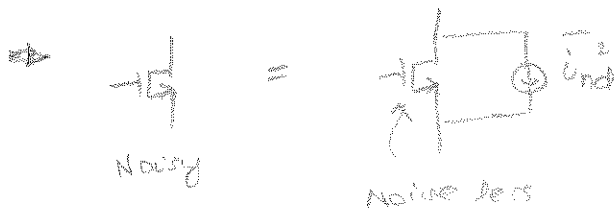
Since MOSFET behaves like a resistor in the triode region it exhibits thermal noise due to Brownian motion of carriers.



$$\boxed{\overline{i_{nd}^2} = 4kT \gamma g_{do} \Delta f}$$

γ = empirical parameter
= 1 in this case

Case (ii) Saturated long-channel MOSFET

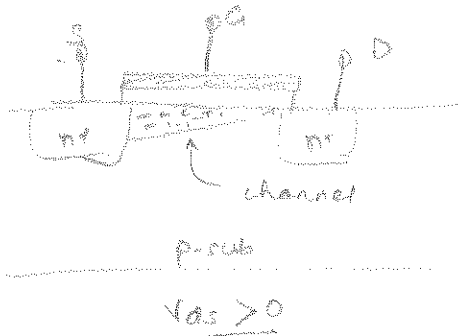

Cause: When a positive V_{ds} is applied, charge carriers get accelerated by the E-field through the resistive channel.




$$\boxed{\begin{aligned} \overline{i_{nd}^2} &= 4kT \gamma g_{do} \Delta f \\ \gamma &= 2/3 \end{aligned}}$$

Recall $I_d = \frac{K_n'}{2} \left(\frac{W}{L} \right) (V_{gs} - V_t)^2$

\Rightarrow Transconductance $g_m = \frac{\partial I_d}{\partial V_{gs}} = K_n' \left(\frac{W}{L} \right) (V_{gs} - V_t) = g_{do}$

$\Rightarrow \boxed{\overline{i_{nd}^2} = 4kT \cdot \frac{2}{3} g_m \Delta f}$ ← (Common form)

Case (ii) Saturated short-channel MOSFET

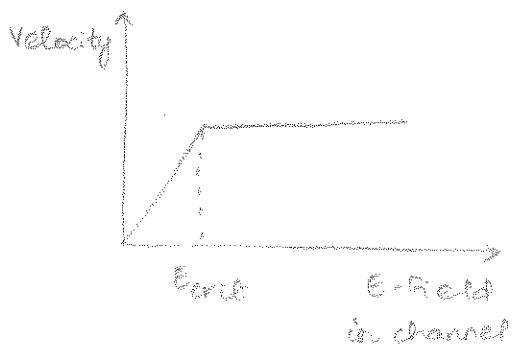

- charge carriers get accelerated from source to drain by the E-field
- velocity of the carrier at drain end $v = \begin{cases} \mu E & E < E_{crit} \\ v_{sat} & E > E_{crit} \end{cases}$

→ velocity saturation

- (Excess noise due to HOT CARRIERS)


- As E-field is increased beyond E_{crit} , the carrier velocity, and hence the kinetic energy saturates.

⇒ Work done by E-field is dissipated as heat.

$$\overline{i_{dn}^2} = 4kT \gamma g_{m0} \Delta f \quad A^2/Hz$$


$$\gamma \approx 2-3$$

(B) Gate-induced noise in MOSFETS

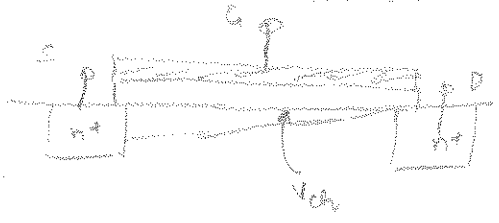

- Because of thermal noise in the drain current, the voltage in the channel fluctuates

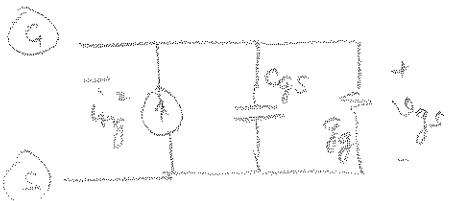• Consequently the gate-channel voltage also fluctuates. Since the gate is capacitive, a noise displacement current flows through the gate.



(Van der Ziel Model)

$$\overline{i_{ng}^2} = 4kT \delta g_g \Delta f$$

$\delta = 2\gamma$ for long-channel MOSFETs

$$g_g = \frac{\omega^2 C_{gs}^2}{5g_{m0}}$$

⇒ Gate-induced noise can be important at high freq. Not an issue at low frequencies

Induced gate noise is not white. To convert to an equivalent white noise model, perform series-parallel conversion (narrowband only!)



$$r_g' = \frac{1}{g_g(\omega^2 + 1)} \approx \frac{1}{g_g \omega^2} = \frac{1}{g_g \left(\frac{\omega C_{gs}}{g_g}\right)^2} \approx \frac{1}{5g_{d0}}$$

$$r_g' = \frac{1}{5g_{d0}} \quad C_{gs}' \approx C_{gs}$$

To find $\overline{v_n^2}$, equate short-circuit currents:




$$i_{sc} = i_{ng} = \frac{v_n}{r_g' + sC_{gs}'} = \frac{v_n'}{r_g'} \cdot \frac{1}{1 + \frac{sC_{gs}'}{r_g'}}$$

$$\Rightarrow \overline{i_{sc}^2} = \overline{i_{ng}^2} = \frac{\overline{v_n^2}}{r_g'^2} \cdot \frac{1}{1 + \frac{\omega^2 C_{gs}'^2}{r_g'^2}} \approx \frac{\overline{v_n^2}}{\omega^2 C_{gs}'^2}$$

$$\Rightarrow \overline{v_n^2} \approx 4kT\delta r_g' \Delta f$$

(c) Flicker noise:

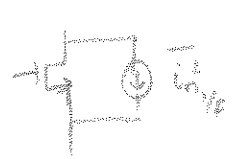


$$\overline{i_{n/f}^2} = \frac{K_{1f}}{f} \cdot \frac{g_m^2}{\omega C_{ox}}$$

A^2/Hz



$$\overline{v_{n/f}^2} = \frac{K_{1f}}{f} \cdot \frac{1}{\omega C_{ox}} \quad V^2/Hz$$

$$f_c \approx \frac{K_{1f}}{4kT} P_T$$

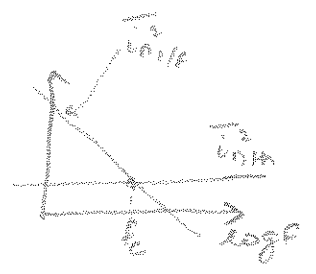

$f_c = g_m/C_{gs}$ = transition freq. of process \Rightarrow faster process \Rightarrow more 1/f noise for equal area