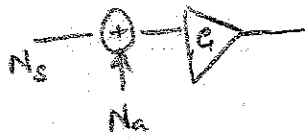


Noise figure - another definition



Consider an amplifier with input-referred noise power N_n and available power gain G .


$$\text{Noise factor } F = \frac{\text{Total noise power}}{\text{Noise power from source}} = \frac{N_n + N_s}{N_s} = 1 + \frac{N_n}{N_s}$$

Let S = signal power; Input $\text{SNR} = \text{SNR}_{in} = \frac{S}{N_s}$

$$\text{Output SNR, } \text{SNR}_{out} = \frac{GS}{G(N_n + N_s)}$$

$$\Rightarrow \frac{\text{SNR}_{in}}{\text{SNR}_{out}} = \frac{S/N_s}{GS/G(N_n + N_s)} = \frac{N_n + N_s}{N_s} = F \Rightarrow \boxed{F = \frac{\text{SNR}_{in}}{\text{SNR}_{out}}}$$

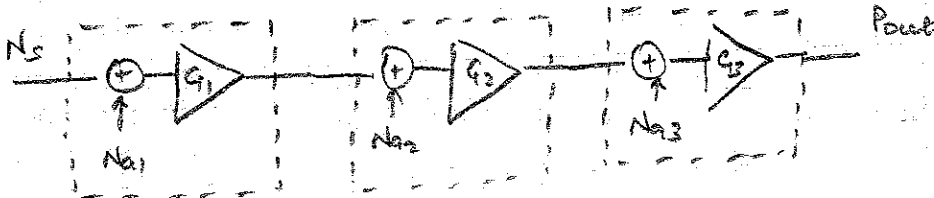Fris equation: Cascaded Noise figure (simple derivation, assume all impedances equal)



Total output noise power

$$P_{out, tot} = \left\{ \left[(N_s + N_{n1}) G_1 + N_{n2} \right] G_2 + N_{n3} \right\} G_3$$

Noise power due to source

$$P_{out, s} = N_s \cdot G_1 \cdot G_2 \cdot G_3$$

$$\Rightarrow F_{tot} = \frac{P_{out, tot}}{P_{out, s}} = 1 + \frac{N_{n1}}{N_s} + \frac{N_{n2}}{N_s G_1} + \frac{N_{n3}}{N_s \cdot G_1 G_2}$$

$$\boxed{F_{tot} = 1 + (F_1 - 1) + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}}$$

At $P_{in} = P_{inmax}$, $P_{inmin} = R$ (noise floor)

$$\Rightarrow P_{inmax} = \frac{2P_{IP3} + R}{3}$$


$$\Rightarrow SFDR = P_{inmax} - P_{inmin} = \left(\frac{2P_{IP3} + R}{3} \right) - (R + SNR_{min})$$

$$\Rightarrow \boxed{SFDR = \frac{2(P_{IP3} - R)}{3} - SNR_{min} \quad (dB)}$$


Where noise floor $R = (-174 \text{ dBm/Hz} + 10 \log_{10} B + NF) \text{ dBm}$

Low-noise amplifiers - Input matching

1) Resistor match:

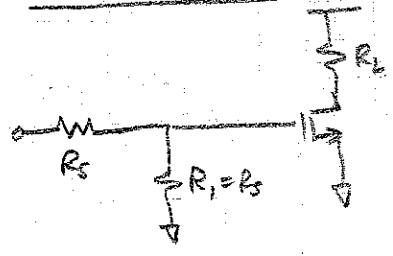

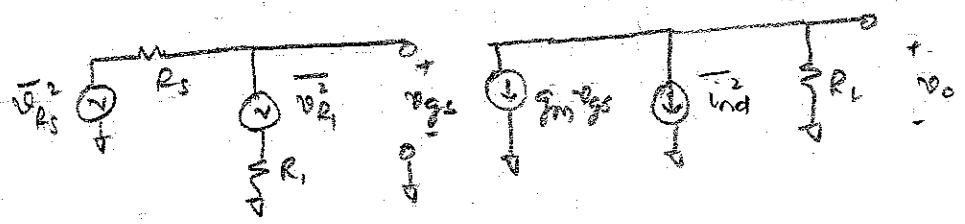- Broadband match
- attenuates signal
- R_1 adds noise
- Estimate noise factor F :
(ignore $1/f$ and induced gate noise)



$$v_o = \left[\frac{R_1}{R_1 + R_s} (\overline{v_{RS}} + \overline{v_{R1}}) g_m + i_{nd} \right] R_L$$

$$\Rightarrow \overline{v_{o, tot}^2} = \left[\left(\frac{R_1}{R_1 + R_s} \right)^2 (\overline{v_{RS}^2} + \overline{v_{R1}^2}) g_m^2 + \overline{i_{nd}^2} \right] R_L^2$$

$$\overline{v_{o, s}^2} = \left(\frac{R_1}{R_1 + R_s} \right)^2 \overline{v_{RS}^2} g_m^2 R_L^2$$

$$\Rightarrow F = 1 + \frac{\overline{v_{R1}^2}}{\overline{v_{RS}^2}} + \left(\frac{R_1 + R_s}{R_1} \right)^2 \frac{1}{g_m^2} \frac{\overline{i_{nd}^2}}{\overline{v_{RS}^2}}$$

$R_i = R_s$, $\overline{i_{nd}^2} = 4kT\gamma g_{do} \Delta f$ and $\overline{v_{ps}^2} = 4kTR_s \Delta f$

$\Rightarrow F = 1 + \frac{R_i}{R_s} + \frac{4}{g_m^2} \cdot \frac{4kT\gamma g_{do} \Delta f}{4kTR_s \Delta f}$

$\Rightarrow F = 2 + \frac{4}{g_m R_s} \cdot \frac{\gamma g_{do}}{g_m}$


Define $\alpha = \frac{g_m}{g_{do}}$

Long-channel $\Rightarrow \alpha \approx 1$
Typically, $\frac{\gamma}{\alpha} \approx \frac{1}{1.8}$ due to short-channel effects


$\Rightarrow F = 2 + \frac{4}{g_m R_s} \frac{\gamma}{\alpha}$

$\Rightarrow NF = 10 \log_{10}(2 + \dots) > 3dB!$

2 Common-gate stage:

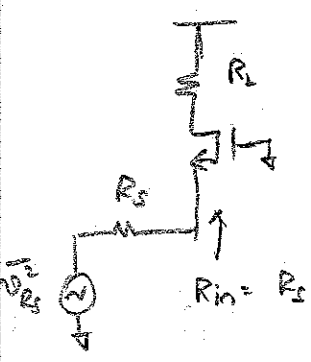

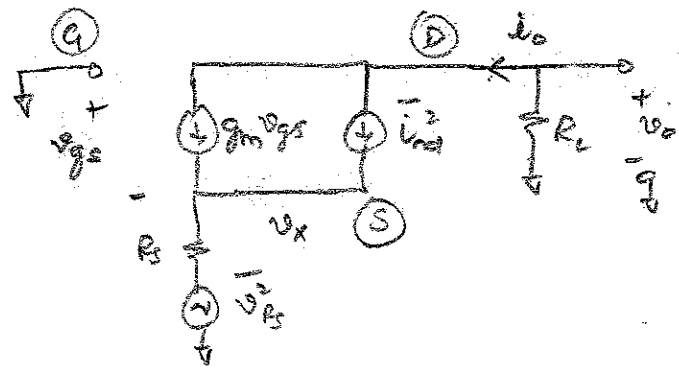- \rightarrow Broadband match
- \rightarrow No input attenuation
- \rightarrow no extra noise sources
- \rightarrow Estimate F due to thermal noise only!



$i_o = \frac{v_x - v_{ps}}{R_s} = -g_m v_x + i_{nd}$


$\Rightarrow v_x = i_o R_s + v_{ps}$

$\therefore i_o = -g_m (v_{ps} + i_o R_s) + i_{nd}$

$\Rightarrow i_o (1 + g_m R_s) = -g_m v_{ps} + i_{nd}$

$\Rightarrow i_o = - \frac{g_m}{1 + g_m R_s} v_{ps} + \frac{i_{nd}}{1 + g_m R_s}$

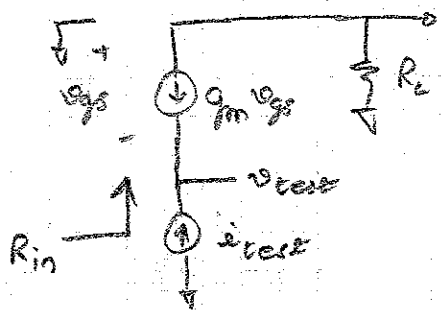Calculate input impedance for power match:



$$i_{test} = -g_m v_{gs} = g_m v_{test}$$

$$\Rightarrow R_{in} = \frac{v_{test}}{i_{test}} = \frac{1}{g_m}$$

\Rightarrow Set $R_{in} = R_s = \frac{1}{g_m}$ for power match

$$i_o = - \frac{g_m}{1 + g_m R_s} v_{R_s} + \frac{i_{nd}}{1 + g_m R_s}$$


$$= - \frac{v_{R_s}}{2 R_s} + \frac{i_{nd}}{2}$$

$$\Rightarrow F = \frac{\overline{i_{out}^2}}{\overline{i_{in}^2}} = \frac{\frac{\overline{v_{R_s}^2}}{4 R_s^2} + \frac{\overline{i_{nd}^2}}{4}}{\frac{\overline{v_{R_s}^2}}{4 R_s^2}} = 1 + R_s^2 \frac{\overline{i_{nd}^2}}{\overline{v_{R_s}^2}}$$

$$\Rightarrow F = 1 + R_s^2 \frac{4kTYg_{d0}\Delta f}{4kTR_s\Delta f} = 1 + \gamma g_{d0} R_s = 1 + \frac{\gamma g_{d0}}{g_m}$$

$$\Rightarrow \boxed{F = 1 + \frac{\gamma}{\alpha}} \leftarrow \text{Long-channel lower bound} = 2.2 \text{ dB}$$

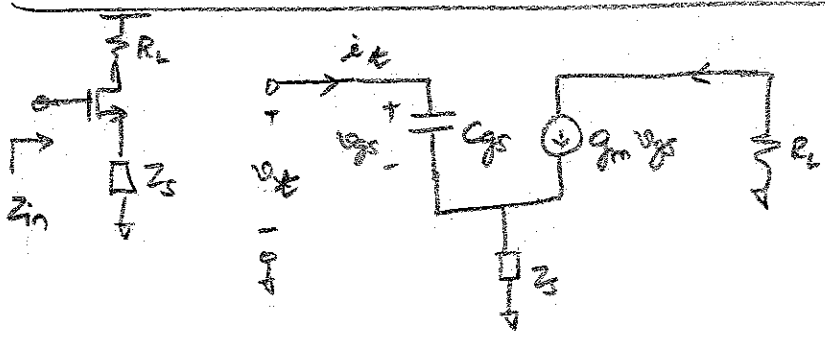3) Obtain resistive input without resistors or C-G input:



$$v_{gs} = \frac{i_e}{s C_{gs}}, \quad \frac{v_{test} - v_{gs}}{Z_s} = i_e + g_m v_{gs}$$


$$\Rightarrow v_E = i_E Z_S + (1 + g_m Z_S) v_{gs}$$

$$= i_E Z_S + (1 + g_m Z_S) \cdot \frac{i_E}{s C_{gs}}$$

$$\Rightarrow Z_{in} = \frac{v_E}{i_E} = Z_S + \frac{1}{s C_{gs}} + \frac{g_m Z_S}{s C_{gs}}$$

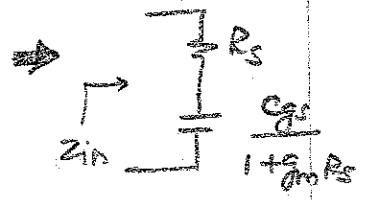(a) $Z_S = R_S$ (resistor degeneration)


$$Z_{in} = R_S + \frac{g_m R_S}{s C_{gs}} + \frac{1}{s C_{gs}} = R_S + \frac{1 + g_m R_S}{s C_{gs}}$$



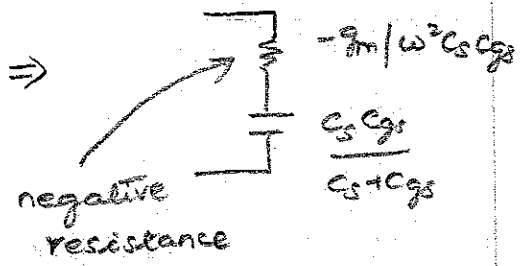
(b) Capacitive degeneration $Z_S = \frac{1}{s C_S}$

$$\Rightarrow Z_{in} = \frac{1}{s C_S} + \frac{1}{s C_{gs}} + \frac{g_m}{s C_{gs}} \cdot \frac{1}{s C_S}$$

$$= \frac{1}{s C_S} \left(1 + \frac{C_S}{C_{gs}} \right) - \frac{g_m}{\omega^2 C_S C_{gs}}$$




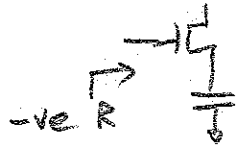- Used in oscillators
- Beware of parasitic cap. in amplifiers → can oscillate



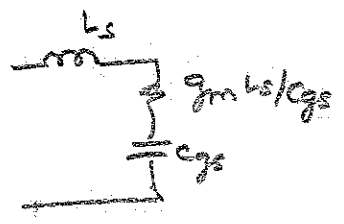(c) Inductive degeneration: $Z_S = s L_S$

$$\Rightarrow Z_{in} = s L_S + \frac{1}{s C_{gs}} + \frac{g_m L_S}{C_{gs}}$$



- we have created a real part in Z_{in} without a resistor
- ⇒ low-noise power match.

Set $\frac{g_m L_S}{C_{gs}} \approx 50 \Omega$ (R_{source})

$\underbrace{\hspace{2cm}}_{\omega T L_S}$