

18-100 Lecture 21: Boolean Logic

James C. Hoe
Dept of ECE, CMU
April 7, 2015

Today's Goal: Introduce Boolean logic

Announcements: Read Rizzoni 12.3 and 11.5
HW8 due Thursday
Office Hours: Wed 12:30~2:30


Handouts: Lab 11 (on Blackboard)

To Wrap up AVR

- ◆ To be a hacker, you also need to know
 - subroutine calls, in particular recursive calls
 - exception handling
 - I/O
 - how to hand optimize code


Feel free to read the AVR documents on Blackboard
- ◆ Big picture to keep in mind
 - you will see assembly programming in much greater detail in 213/240/34{8,9}/447 etc.
 - most of you will not code in assembly for a living; this is more about understanding the underlying concepts
 - once you learn one ISA you can learn the rest
 - some ISAs are uglier than others
 - AVR is not a pretty one.

Recall the 3 aspects of a “computer”

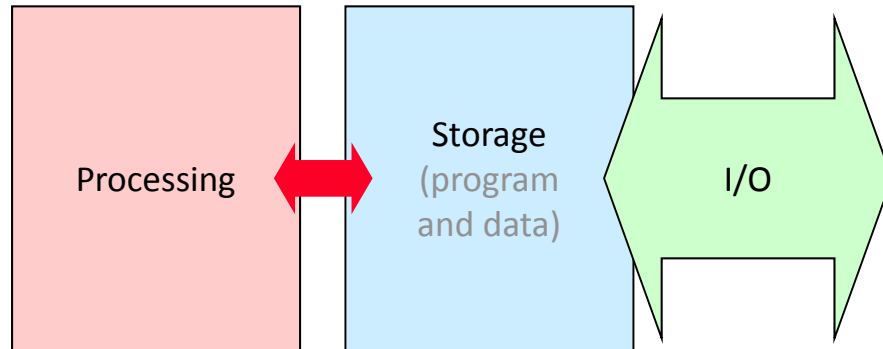

In General

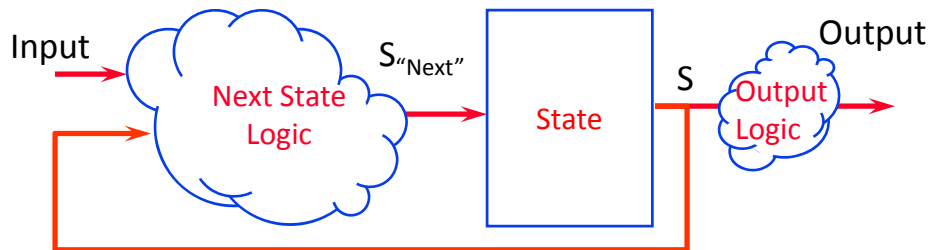- ◆ All “sequential” digital systems comprise



- input and output
- state stuff that remembers
- “combinational” stuff that computes a function (has no memory)
- ◆ In an execution, state is updated to a “next state” based on a function of the current state


First things first: Combinational Logic



The same In value always leads to the same Out value regardless of history

Combinational Logic

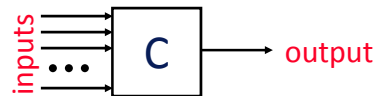
- ◆ A combinational logic circuit has an output that is a “function” of its inputs



- ◆ What do you mean by “function”?
 - unique mapping from input values to output values
 - in this context implies
 - the same input values produce the same output value every time
 - same output for different input values is okay
 - no memory (does not depend on the history of input values)
- ◆ Later on we will learn, a “sequential” circuit’s output depends on the current and the history of its inputs


Examples: and / or / not

AND: Z is true iff both X and Y are true

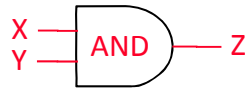


X	Y	Z
F	F	F
F	T	F
T	F	F
T	T	T

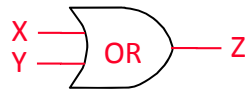OR: Z is true iff X or Y or both are true



X	Y	Z
F	F	F
F	T	T
T	F	T
T	T	T

NOT: X' is the complement of X

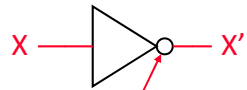


X	X'
F	T
T	F

bubble means invert;
triangle is "buffer"

Any logical function can be constructed using only AND and NOT gates, or only OR and NOT gates

Boolean Algebra: Big Picture

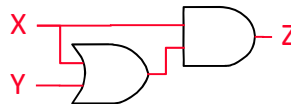- ◆ An algebra on
 - two values (usually denoted as True vs False or 1 vs 0)
 - the operators AND (\cdot), OR ($+$), NOT
- ◆ A useful formalism to represent and reason about combinational logic functions
- ◆ For example,



- combinational logic above can be expressed as $Z = X \cdot (X + Y)$
- using rules of Boolean algebra, the above expression can be simplified to $Z = X$

Rules of Boolean Algebra (Table 12.11)

- | | | |
|-------------------------------------|--|-------------------------------|
| 1. $0+X=X$ | 6. $1\cdot X=X$ | “.” means AND
“+” means OR |
| 2. $1+X=1$ | 5. $0\cdot X=0$ | |
| 3. $X+X=X$ | 7. $X\cdot X=X$ | |
| 4. $X+X'=1$ | 8. $X\cdot X'=0$ | |
| 9. $(X')'=X$ | | |
| 10. $X+Y=Y+X$ | 11. $X\cdot Y=Y\cdot X$ | (commutativity) |
| 12. $X+(Y+Z)=(X+Y)+Z$ | 13. $X\cdot(Y\cdot Z)=(X\cdot Y)\cdot Z$ | (associativity) |
| 14. $X\cdot(Y+Z)=X\cdot Y+X\cdot Z$ | (14). $X+(Y\cdot Z)=(X+Y)\cdot(X+Z)$ | (distributive) |

- ◆ The above is a standard set of rules that can be easily shown by “perfect induction”
- ◆ Notice the symmetry between the left and right columns with respect to substitutions of 0 by 1, + by \cdot and vice versa

Does $X+(Y\cdot Z)=(X+Y)\cdot(X+Z)$?

X	Y	Z	$(Y\cdot Z)$	$X+(Y\cdot Z)$	$(X+Y)$	$(X+Z)$	$(X+Y)\cdot(X+Z)$
F	F	F	F	F	F	F	F
F	F	T	F	F	F	T	F
F	T	F	F	F	T	F	F
F	T	T	T	T	T	T	T
T	F	F	F	T	T	T	T
T	F	T	F	T	T	T	T
T	T	F	F	T	T	T	T
T	T	T	T	T	T	T	T

Enumerate all possible patterns; n variables have 2^n patterns



Evaluate the expressions in question for each case, possibly with the help of intermediate expressions like $(Y\cdot Z)$

Duality

- ◆ Is that a truth table for AND or OR?
 - Ans. depends on \Rightarrow means true or false
 - if \Rightarrow means true then OR
 - if \Rightarrow means false then AND

X	Y	Z
\Rightarrow	\Rightarrow	\Rightarrow
\Rightarrow	\Rightarrow	\Rightarrow
\Rightarrow	\Rightarrow	\Rightarrow
\Rightarrow	\Rightarrow	\Rightarrow

- ◆ AND and OR are duals

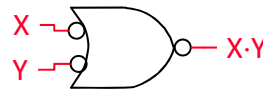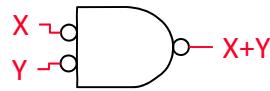

\Rightarrow De Morgan's Theorem

$$X' \cdot Y' = (X+Y)'$$

$$X'+Y' = (X \cdot Y)'$$

\Rightarrow For every rule, there is a "dual" rule where AND and OR are exchanged and 0 and 1 are exchanged

Does $X+XY=X$?

- ◆ Instead of perfect induction, we can also prove algebraically using proven rules, e.g.,

$$\begin{aligned}
 & X+X \cdot Y \\
 = & 1 \cdot X+X \cdot Y && \text{rule 6} \\
 = & X \cdot 1+X \cdot Y && \text{rule 11} \\
 = & X \cdot (1+Y) && \text{rule 14} \\
 = & X \cdot 1 && \text{rule 2} \\
 = & 1 \cdot X && \text{rule 11} \\
 = & X && \text{rule 6}
 \end{aligned}$$

Does $XY+YZ+X'Z=XY+X'Z$?

Rules of Boolean Algebra (Table 12.11)

- | | |
|---|---|
| 15. $X+X \cdot Y=X$ | 16. $X \cdot (X+Y)=X$ (absorption) |
| 17. $(X+Y)(X+Z)=X+YZ$ | (17). $XY+XZ=X(Y+Z)$ |
| 18. $X+X'Y=X+Y$ | (18). $X \cdot (X'+Y)=XY$ |
| 19. $XY+YZ+X'Z=XY+X'Z$ | (19). $(X+Y)(Y+Z)(X'+Z)=(X+Y)(X'+Z)$ |
| DM. $(A+B+C+\dots)' = A' \cdot B' \cdot C' \dots$ | (DM). $(A \cdot B \cdot C \cdot \dots)' = A'+B'+C'+\dots$ |

- ◆ The above and other rules can be derived from the basic set, as we did for Rules 15 and 19

Application in Logic Minimization

- ◆ Given $f = X'Y'Z' + X'Y'Z + X'YZ + XYZ$ simplify the expression by algebraic manipulation

$$\begin{aligned} & X'Y'Z' + X'Y'Z + X'YZ + XYZ \\ &= X'Y'(Z' + Z) + (X' + X)YZ && \text{rule 14} \\ &= X'Y' \cdot 1 + 1 \cdot YZ && \text{rule 4} \\ &= X'Y' + YZ && \text{rule 6} \end{aligned}$$
- ◆ Original expression required one 4-input OR gate and four 3-input AND gates
- ◆ Simplified expression requires one 2-input OR gate and two 2-input AND gates
- ◆ Can we do any better? If not, can we know for sure?

Minimize $f = A'B'D + A'BD + BCD + ACD$

(Example 12.3 from Rizzoni)

Quick Peek Below the Digital Abstraction

Physical Representations of 1s and 0s


- ◆ Many ways in electronics
 - voltage level (high vs low)
 - voltage change (delta up vs down)
 - relative current drive on a differential pair
 - on-off keying in various transmissions

e.g., harddrive read back




Objective: must be hard to confuse between 1 vs 0

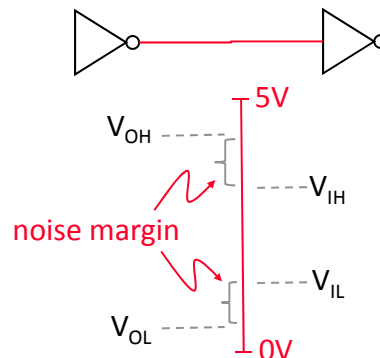- ◆ Voltage level noise margin
 - output devices guarantee min V_{OH} and max V_{OL}
 - input devices insist on a min V_{IH} and max V_{IL} ; if violated does not register correctly as high or low




Example: NMOS Resistor-Transistor Logic

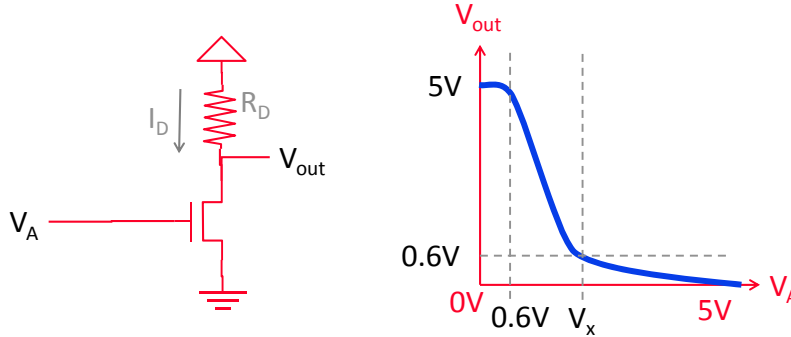


- ◆ I/O voltage levels
 - $V_{IL-max} < \text{turn-on} \approx 0.6V, V_{IH-min} > (\text{by how much?}) V_x$
 - $V_{OH} \approx 5V$ (without any load), $V_{OL} \approx ??$
- ◆ Noise margin: full-swing output even if input is not perfect
- ◆ But, in output-low state, $I_D > 0 \Rightarrow$ leaking power

Inverting Logic

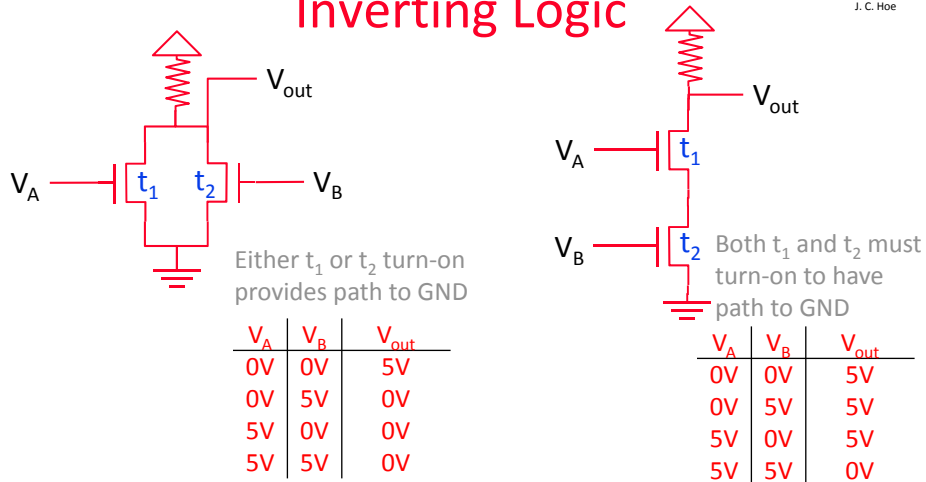


- ◆ Instead of AND and OR we have NAND and NOR!!
 - we can always stick an inverter on the output
 - fortunately either NAND or NOR is all we really need


Complex Inverted Function Gates

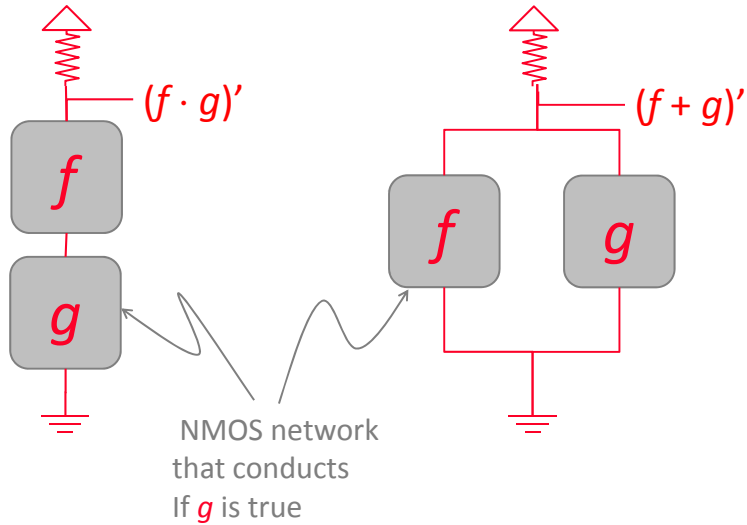

Complex Gate Example: Exclusive OR (XOR)

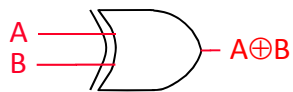


A	B	$A \oplus B$
F	F	F
F	T	T
T	F	T
T	T	F

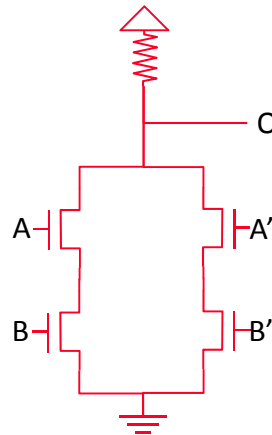

$$O = A \oplus B = (AB + A'B')'$$



Complex Function Gate Example

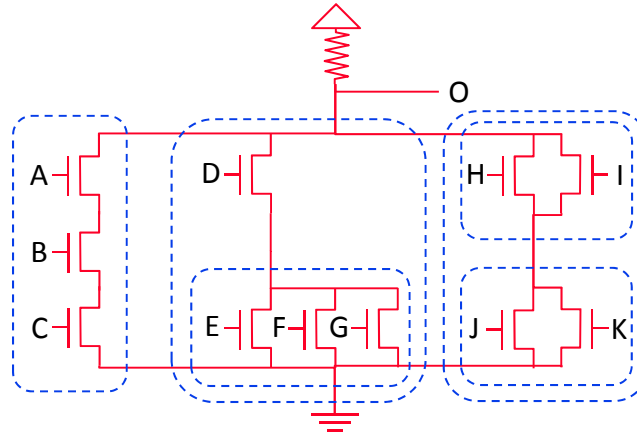

$$O = \{ [A \cdot B \cdot C] + [D \cdot (E + F + G)] + [(H + I) \cdot (J + K)] \}'$$


Don't really build something this complex in one gate. Too clunky.

Complementary MOS (CMOS) Logic

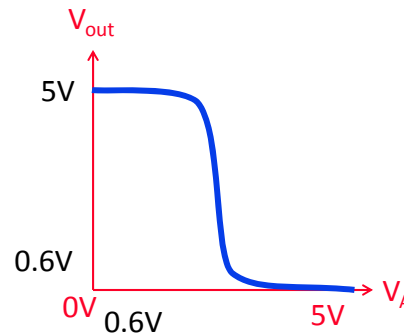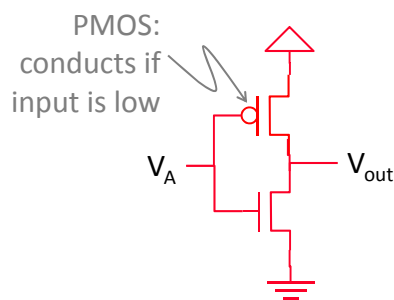


- ◆ Almost ideal inverter transfer curve
 - ◆ large, balanced noise margin; strong signal restorations
- ◆ Only 1 transistor (NMOS or PMOS) is conducting at a time
 - ideally no (very little) static leakage current/power

CMOS NANDs and NORs

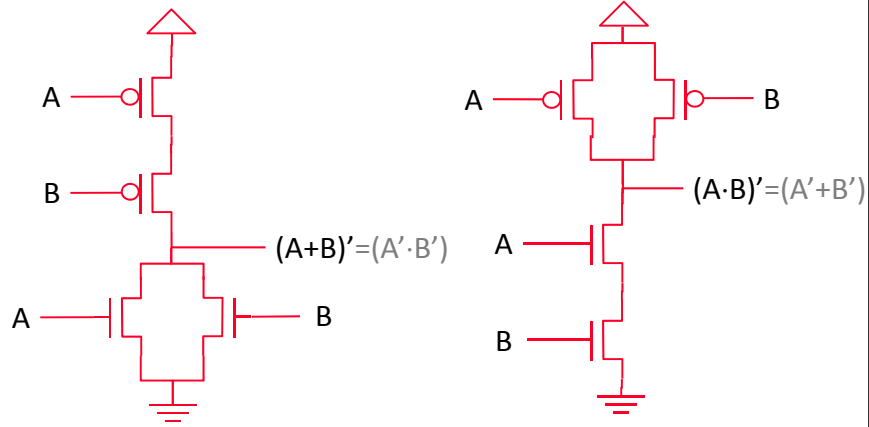

- ◆ PMOS and NMOS networks are De Morgan duals
 ⇒ output either connected to VCC or GND, never both
- ◆ NANDs are better than NORs (take 320 to find out why)

CMOS Complex Gate Example

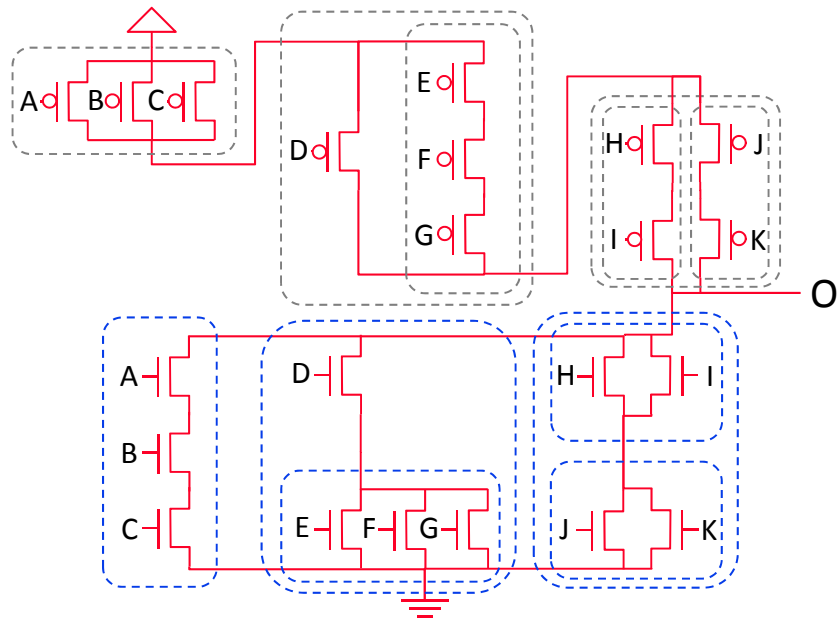

Minimize $f=A'B'D+A'BD+BCD+ACD$ (Example 12.3)

$$\begin{aligned}
 & A'B'D+A'BD+BCD+ACD \\
 = & A'D(B'+B)+BCD+ACD && \text{rule 14} \\
 = & A'D+BCD+ACD && \text{rule 4 and 6} \\
 = & (A'+AC)D+BCD && \text{rule 14} \\
 = & (A'+C)D+BCD && \text{rule 18} \\
 = & A'D+CD+BCD && \text{rule 14} \\
 = & A'D+CD(1+B) && \text{rule 14} \\
 = & A'D+CD && \text{rule 2 and 6} \\
 = & (A'+C)D && \text{rule 14}
 \end{aligned}$$

Does $XY+YZ+X'Z=XY+X'Z$?

$$\begin{aligned}
 & XY+YZ+X'Z \\
 = & XY \cdot 1 + YZ \cdot 1 + X'Z \cdot 1 && \text{rule 6} \\
 = & XY(Z+Z') + YZ(X+X') + X'Z(Y+Y') && \text{rule 4} \\
 = & XYZ+XYZ'+YZX+YZX'+X'ZY+X'ZY' && \text{rule 14} \\
 = & XYZ+XYZ'+XYZ+X'YZ+X'YZ+X'Y'Z && \text{rule 11} \\
 = & XYZ+XYZ+XYZ'+X'YZ+X'YZ+X'Y'Z && \text{rule 10} \\
 = & XYZ+XYZ'+X'YZ+X'Y'Z && \text{rule 3} \\
 = & XY(Z+Z') + X'Z(Y+Y') && \text{rule 14} \\
 = & XY \cdot 1 + X'Z \cdot 1 && \text{rule 4} \\
 = & XY+X'Z && \text{rule 6}
 \end{aligned}$$

This one is tricky

Does $XY+YZ+X'Z=XY+X'Z$? (done another way)

$XY+YZ+X'Z$	
$= XY+YZ \cdot 1+X'Z$	rule 6
$= XY+YZ(X+X')+X'Z$	rule 4
$= XY+YZX+YZX'+X'Z$	rule 14
$= XY+XYZ+X'ZY+X'Z$	rule 11
$= XY+XYZ+X'Z+X'ZY$	rule 10
$= XY \cdot 1+XYZ+X'Z \cdot 1+X'ZY$	rule 6
$= XY(1+Z)+X'Z(1+Y)$	rule 14
$= XY \cdot 1+X'Z \cdot 1$	rule 2
$= XY+X'Z$	rule 6

} rule 15
absorption