18-321
Homework #9
MOS ICs

Due: Friday, May 5, 2k
4:30pm
Lydia Corrado's Office

1. 5.72

2. 5.75

3. 5.80

4. 5.81

5. 6.80

6. 6.97

7. 7.26 It reads calculate f_H, but you should actually approximate f_H using the open circuit time constant approximation.

8. 7.78

Note that these are EXCELLENT practice problems for the final exam.